
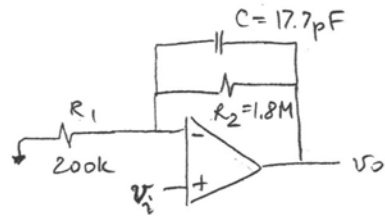


① For the following circuit

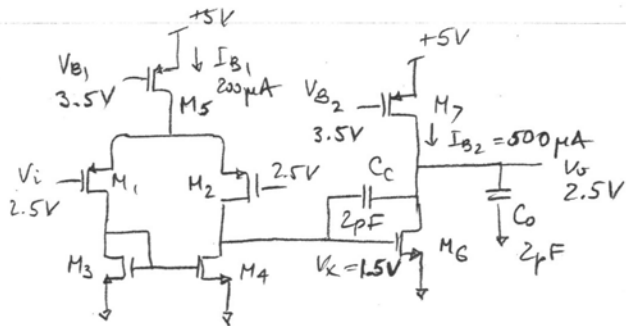

- (a) sketch the frequency response showing the low-frequency gain, the high-frequency gain, any poles and zeros, and slopes
- (b) if the unity GBW of the opamp is 10MHz, what is the gain error and the corrected gain of v_o/v_i at 200kHz?


② For the opamp shown



$$\begin{aligned}
 K_p &= 25 \mu A/V^2 \\
 \mu_n &= 50 \mu A/V^2 \\
 V_{thn} &= 0.5V \\
 V_{thp} &= -0.5V \\
 \lambda_p &= 0 \quad \lambda_n = 0.05 \\
 \delta_p &= 0 \quad \delta_n = 0
 \end{aligned}$$

- (a) With an opamp having a circuit as shown, and bias currents and other parameters as specified, pick and specify any transistor sizes to establish an internal bias voltage level v_x of 1.5V as shown and an output bias of 2.5V.
- (b) determine the DC magnitude gain of the two stages ($v_x/v_i, v_o, v_x$) and the overall DC gain in dB.
- (c) calculate the pole and zero frequencies and the unity GBW of the opamp in Hz. Determine if the opamp is stable. Explain your reasoning.
- (d) Find the positive and negative common-mode input range.

3. For the circuit shown

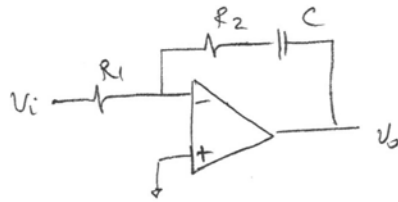

$$R_1 = 1\text{M}\Omega$$

$$R_2 = 2\text{K}\Omega$$

$$C = 5\text{pF}$$

- Find the transfer functions relating the noise due to R_1 and R_2 to the output
- Calculate the power spectral density at the output due to R_1 and R_2 at 100kHz
- Find the integrated output noise due to R_2 up to a bandwidth of 1MHz .
- The opamp has input referred thermal noise voltage v_n of $20\text{ nV}/\sqrt{\text{Hz}}$. Sketch the output noise density due to v_n from 1kHz to 1MHz .