

NETLIST STRUCTURE

TITLE

DESCRIPTION
OF SOURCES

DESCRIPTION
OF ELEMENTS

SOLUTION
CONTROL

OUTPUT
CONTROL

END
STATEMENT

CIRCUIT DESCRIPTION

- The first letter identifies the element type followed by a name limited to 7 characters

Rxx	Resistor
Cxx	Capacitor
Lxx	Inductor
Vxx	Voltage source
Ixx	Current source
Dxx	Diode
Qxx	BJT
Mxx	MOSFET

Node numbering

- All nodes numbered with nonnegative integers between 0 and 9999
- Ground node must be labeled 0
- SPICE allows to assign several numbers for the same node

PASSIVE ELEMENT STATEMENT

$X\langle name \rangle N+ N- value \langle IC=xx \rangle$

X is the reserved letter R , L , or C

$\langle name \rangle$ is number or string

$N+$ and $N-$ denote polarity of voltage across the element or current direction

$N+$ corresponds to more positive potential

$value$ is specified in Ohms [Ω], Henries [H] or Farads [F] correspondingly

$\langle IC (VC \text{ or } IL) = xx \rangle$ is the initial condition: capacitive voltage or inductive current at the time $t=0$


PASSIVE ELEMENTS

Resistor



$$V_R = R \cdot I_R, \quad R[\Omega]$$


Capacitor

 

$$V_C = \frac{1}{C} \int_0^{t_1} I_C \cdot dt \rightarrow V_C = \frac{1}{j\omega C} \cdot I_C$$

$$X_C = \frac{1}{j\omega C}, \quad C[F]$$

Inductor

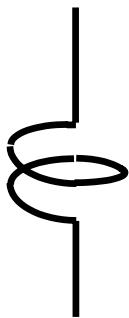


$$V_L = L \frac{d}{dt} I_L \rightarrow V_L = j\omega L \cdot I_L$$

$$X_L = j\omega L, \quad L[H]$$

POWER-OF-TEN NUMERICAL SUFFIXES IN PSPICE

Suffix	Factor
T	10^{12}
G	10^9
MEG	10^6
K	10^3
M	10^{-3}
U	10^{-6}
N	10^{-9}
P	10^{-12}
F	10^{-15}

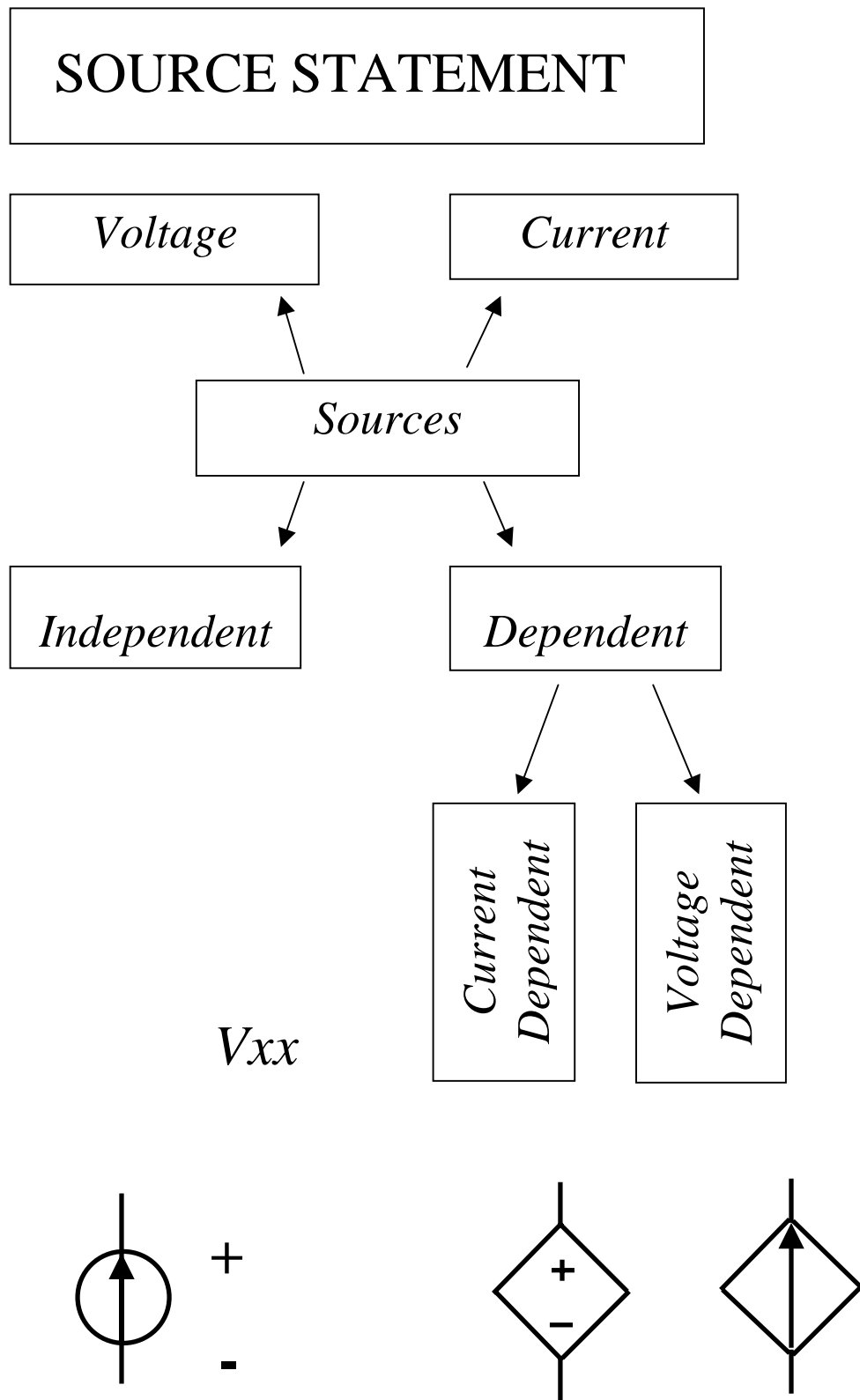

PARAMETERS OF VOLTAGE AND CURRENT SOURCES

DC sources

V <name> N+ N- DC <value>

I <name> N+ N- DC <value>




Voltage Source

Current Source

V1

V2

I1

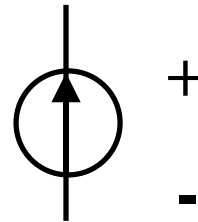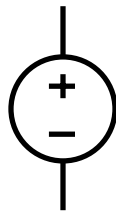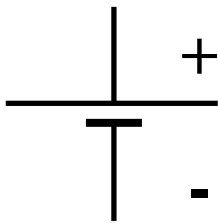


III. AC sources

For analysis in *time* domain

V<name> N+ N- SIN(Voff Vamp <freq> <TD> <damp>)

For analysis in *frequency* domain

V<name> N+ N- AC <Vamp>

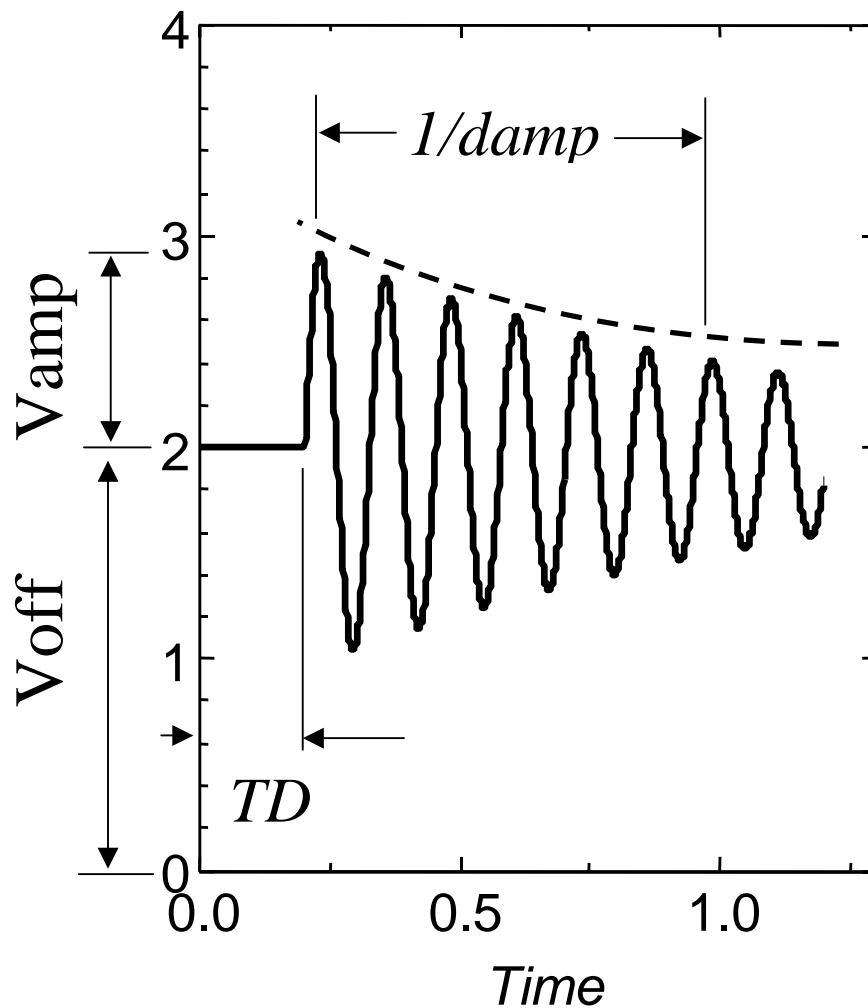

SOLUTION CONTROL

Operating Point Analysis

Determination of the Quiescent point (Q-point)

.OP

DC analysis

Circuit performance with DC sweeping

.DC *snm1 str1 stp1 inc1* <*snm2 str2 stp2 inc2*>

snm specify Voltage or Current source name

str, ***stp*** and ***inc***: Start, End and Increment values in Volts or Amps

AC analysis

Circuit performance in *frequency* domain

.AC *sweep num freq1 freq2*

sweep: **LINE** (linear), **DEC** (decade) or **OCT** (octave)

num: number of points per decade, octave or total

freq1, ***freq2***: Start and End frequencies in Hertz

Examples: .DC V1 0 10 0.1 I1 10u 100u 10u

.AC DEC 20 10K 100MEG

SOLUTION CONTROL

Transient analysis
Circuit performance in *time* domain

.TRAN *Tinc Tstop*

Tinc: Time increment in seconds

Tstop: Final time analyzed

Example: .TRAN 10n 2u

.PROBE

Store results of simulation in an *output file* for the future graphical representation

.END

Ends the SPICE *input file*. Can be placed in any part of file for debugging.

OUTPUT CONTROL

- The list of voltages and currents between nodes can be plotted using PROBE tool.
- The following suffix may be appended to variable names to extract specific parameters


Suffix	Meaning	Example
DB	Magnitude in <i>dB</i>	V1DB(1,0)
M	Magnitude V_m	IM(V1)
P	Phase ϕ	V1P(1,0)
R	Real part V_{Re}	V1R(1,0)
I	Imaginary part V_{Im}	V1I(1,0)

$$\text{Decibell: } V_m [\text{dB}] = 20 \lg V_m [\text{Volts}]$$

$$\text{Phasor: } V = V_m [\text{Volts}] e^{j\phi [\text{Degrees}]} = V_{Re} + jV_{Im}$$

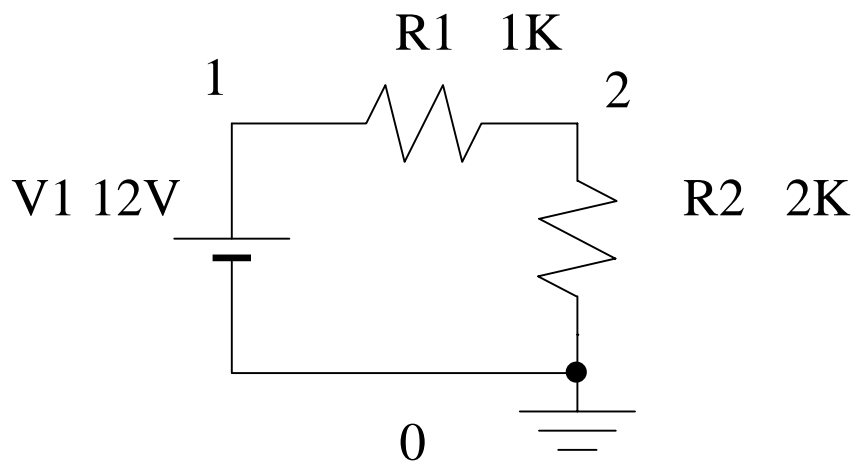EXAMPLE


Write down a PSPICE netlist to perform the operating point analysis for the circuit in Figure below:



The Input File (Netlist):

```
Voltage divider
V1 1 0 DC 12
R1 1 2 1K
R2 2 0 2K
.OP
.END
```

Kirchhoff Voltage Law

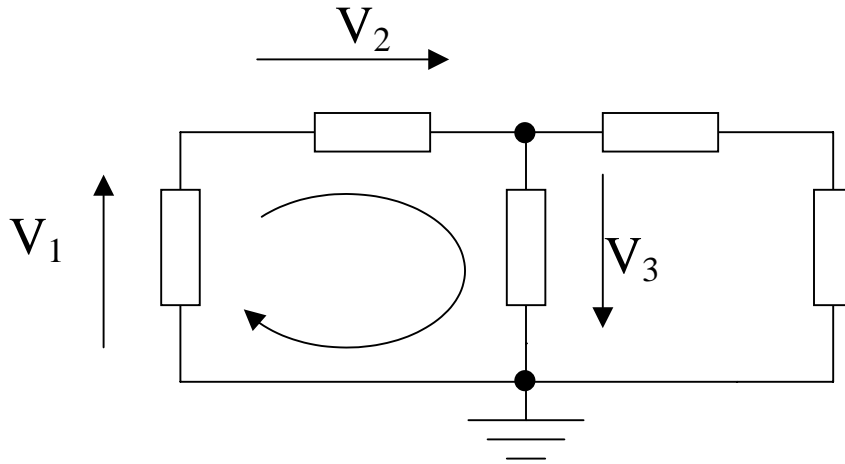


$$V_1 + V_2 + V_3 = 0$$

The algebraic sum of the voltage drops around closed path is zero

$$\sum_i V_i = 0$$

- The polarity of voltage across every element may be assigned *arbitrary*
- KVL is satisfied for AC signals

Kirchhoff Current Law

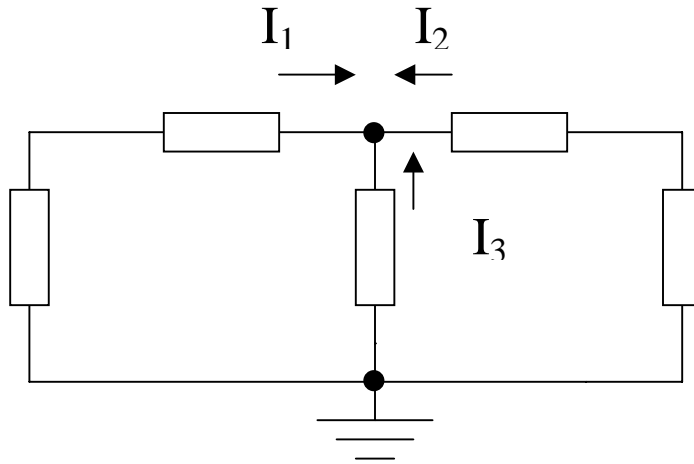

$$I_1 + I_2 + I_3 = 0$$


The algebraic sum of currents entering any node is zero

$$\sum_i I_i = 0$$


- Direction of current through every element can be chosen arbitrarily
- KCL is satisfied for AC signals

Analog Multimeter

Voltage Measurements

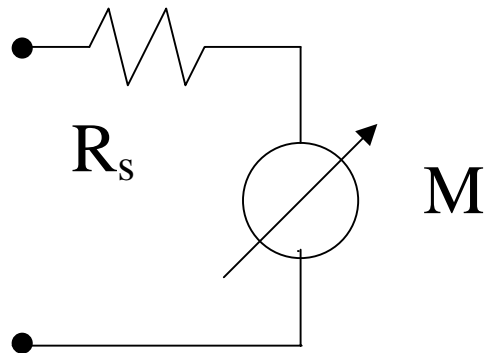


Current Measurements

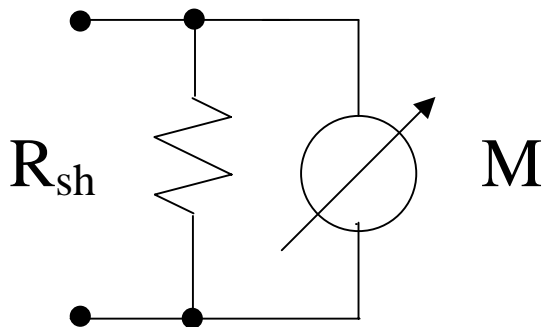


- *Floating nodes*: we can ignore the common mode voltage
- *Low accuracy*:
 - Low input resistance* for voltage measurements
 - Low input conductance* for current measurements
- *Needs to be calibrated* for resistance measurements *for every scale*

Digital Multimeter

Voltage Measurements

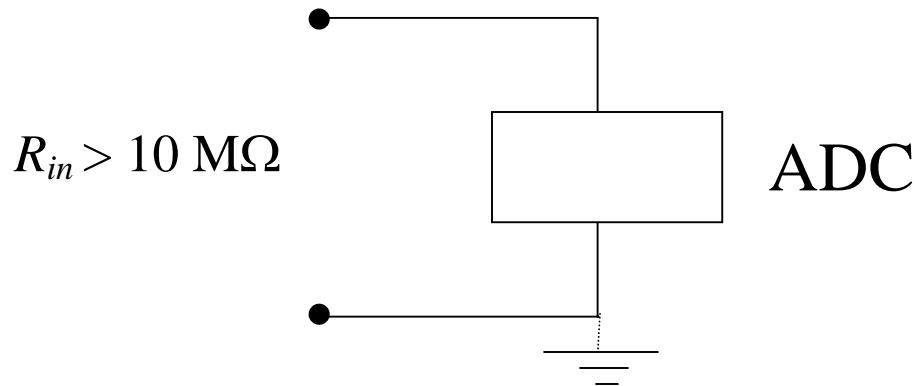


Current Measurements

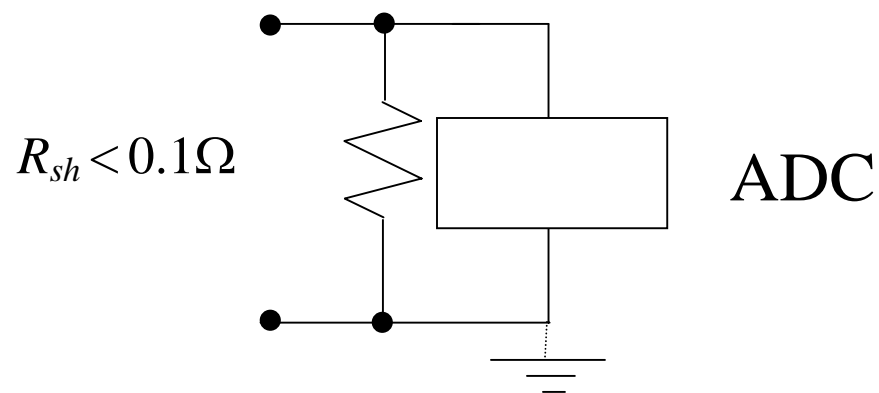

- *Virtually grounded*: the common mode voltage should be minimized!
- *High accuracy*:
 - High input resistance* for voltage measurements
 - High input conductance* for current measurements


Voltage and Current Measurements

Voltage Measurements

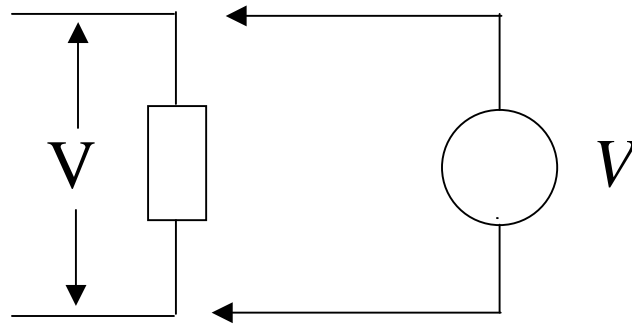

- Voltmeter V is connected *in parallel* to the element of the circuit

Current Measurements

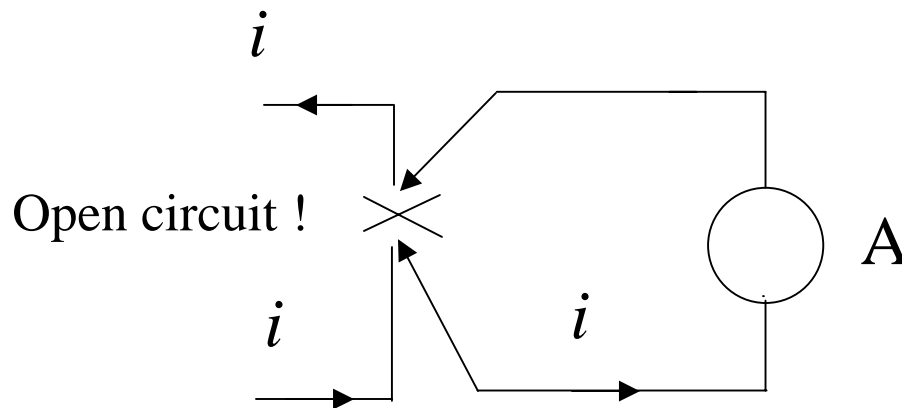

- The power must be *switched off* and the circuit must be *open* first
- Ammeter is *always* connected *in series* to the element of the circuit
- Then the power is switched on

Taking Measurements with DMM Fluke 45


- *Dual* display of Digital Multi Meter (DMM) *Fluke 45* allows one to take *two simultaneous* measurements which is very useful

Dual Display Applications

Primary Display	Secondary Display	Applications
Volts DC	Current DC	<ul style="list-style-type: none"> • Measurements of I-V characteristics • Check power supply load regulation
Volts AC	Current AC	<ul style="list-style-type: none"> • Power Line –Load test • Transformer (magnetic circuit) saturation test
Volts DC	Volts AC	<ul style="list-style-type: none"> • Monitor DC level and ripple of power supply
Volts AC	Current DC	<ul style="list-style-type: none"> • Check AC/DC or DC/AC converters
Volts AC	Frequency	<ul style="list-style-type: none"> • Frequency response
Volts dB	Frequency	<ul style="list-style-type: none"> • Quick Bode plots
Relative	Actual value	<ul style="list-style-type: none"> • Show actual measurements and the difference between this value and the relative base • Select and sort resistors
HOLD	Actual value	<ul style="list-style-type: none"> • Show actual value while holding a previous measurement

Oscilloscope

Voltage Measurements

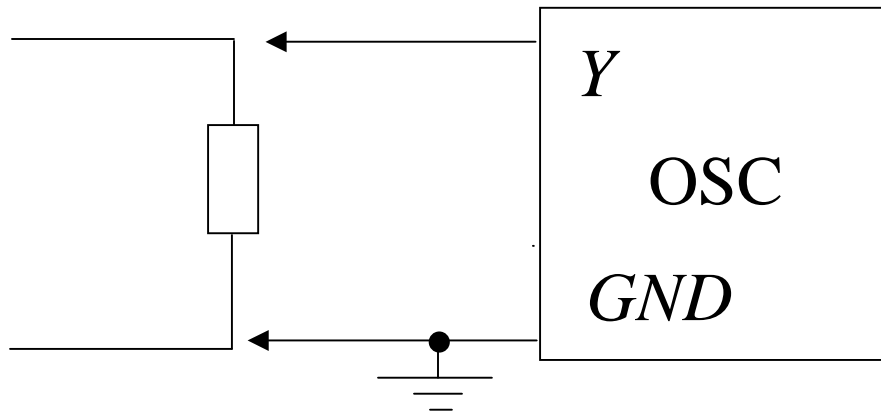


- Only *voltage measurements* can be taken
- One node is *always grounded*: the common mode voltage *must be zero*!

In order to measure the voltage across the element with both terminals hot: two terminals must be measured separately with respect to the ground and the results are subtracted

- Good accuracy: high input resistance

AC (periodical) signals

Determination of the Phase Shift

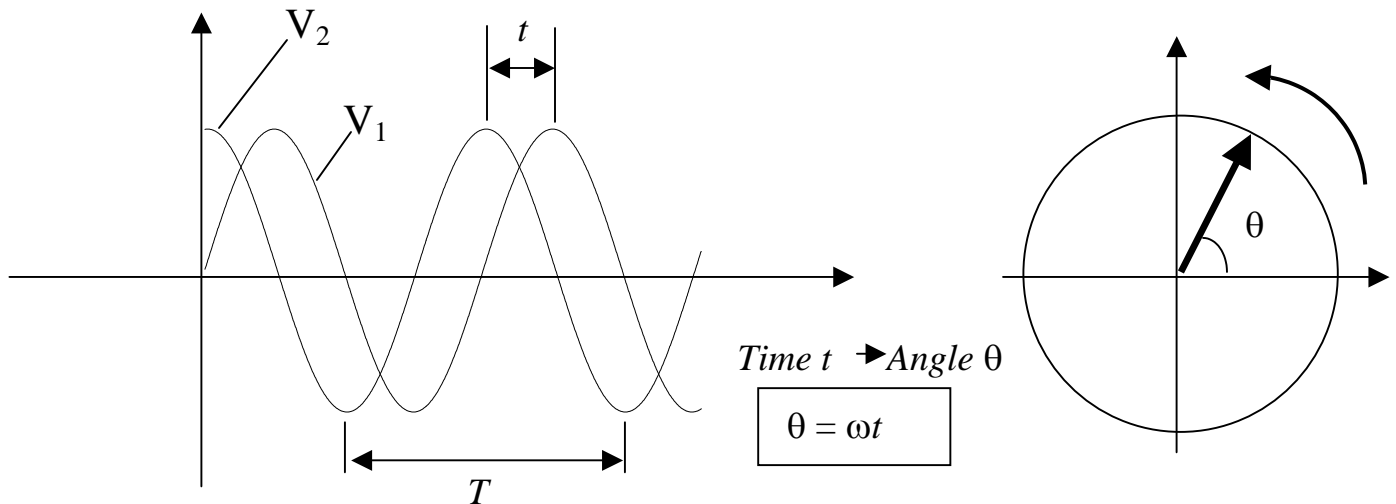

- *Period* is the shortest distance in time between two points with the same phase. It is convenient to measure the period between maxima or minima.
- *Frequency* is a value reciprocal to period: $f [\text{Hz}] = 1/T$
- *Angular frequency* shows the number of radians per sec: $\omega [\text{s}^{-1}] = 2\pi f$
- *Phase shift* is determined in the following way:

$$\Delta\Phi = \Phi_2 - \Phi_1 = \frac{t}{T} \cdot 2\pi [\text{rad}] = \frac{t}{T} \cdot 360 [\text{degrees}]$$

- *Phase shift* is determined with 2π accuracy
- Note the *sign* of the phase shift: in example above V_2 is *leading* V_1

Phasor Diagram

Exponential form of periodical *in time* signal:

$$V(t) = \text{Re}\{V_m \cdot e^{j(\omega t + \phi)}\} = \text{Re}\{\bar{V} \cdot e^{j\omega t}\}$$

$$\bar{V} = V_m \cdot e^{j\phi}$$


Phasor is a *complex number*

expressing the amplitude and the phase of a signal

- *Phasor* is a time-independent part of a signal
- The *amplitude* of sinusoid is the *magnitude* of its phasor
- The *phase angle* of the sinusoid is the *angle* of its phasor
- Phasor simplifies circuit analysis using *complex number* algebra

Properties of Complex Numbers

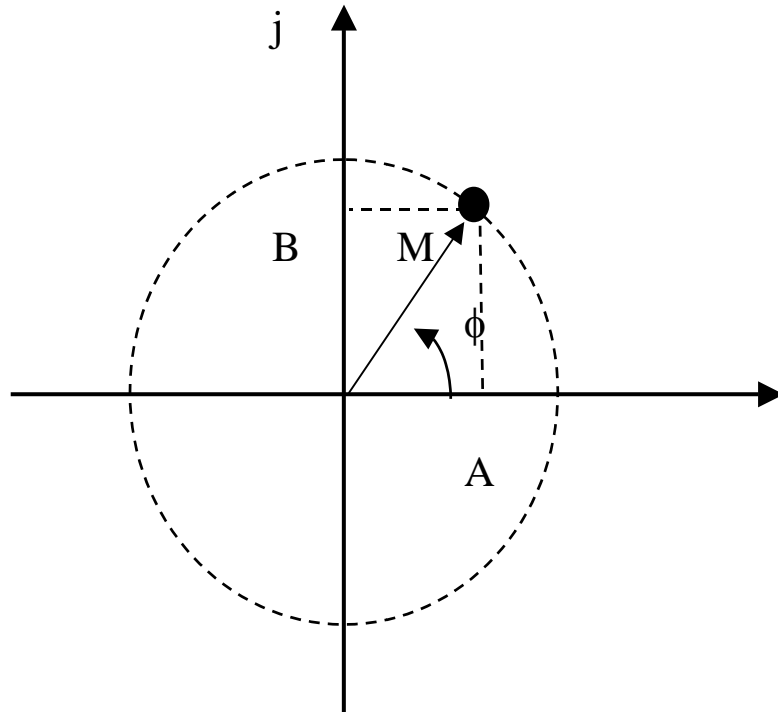- A complex number has a geometrical meaning and can be *uniquely* represented as a point on a *complex plane*



$$X = A + jB = M e^{j\phi}$$

- Euler equation: $e^{j\phi} = \cos \phi + j \sin \phi$

$$M = (A^2 + B^2)^{1/2}, \quad \phi = \arctan (B/A)$$

$$j^2 = -1, \quad j = e^{j\pi/2}$$

Operation with Complex Numbers

$$X_1 = A_1 + jB_1 = M_1 e^{j\varphi_1}$$

$$X_2 = A_2 + jB_2 = M_2 e^{j\varphi_2}$$

1) Sum of Complex Numbers:

$$X_1 + X_2 = (A_1 + A_2) + j(B_1 + B_2)$$

2) Product of Complex Numbers:

$$X_1 X_2 = M_1 M_2 e^{j(\varphi_1 + \varphi_2)}$$

$$X_1 X_2 = (A_1 A_2 - B_1 B_2) + j(A_1 B_2 + B_1 A_2)$$


3) Ratio of Complex Numbers:

$$X_1/X_2 = \{(A_1 A_2 + B_1 B_2) + j(A_2 B_1 - A_1 B_2)\} / (A_2^2 + B_2^2)$$


$$X_1/X_2 = (M_1/M_2) e^{j(\varphi_1 - \varphi_2)}$$

Voltage and Current Shift in Passive Elements


Resistor $V_R = R \cdot I,$

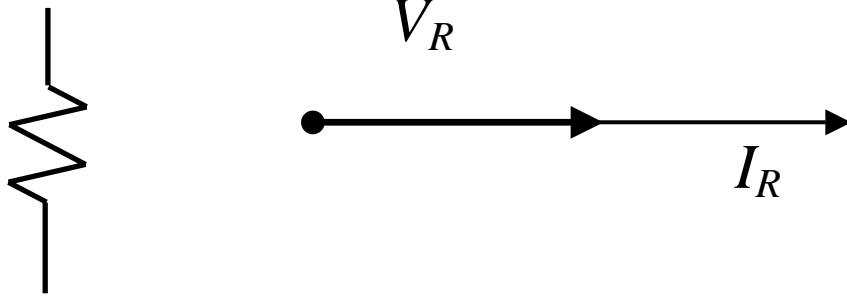

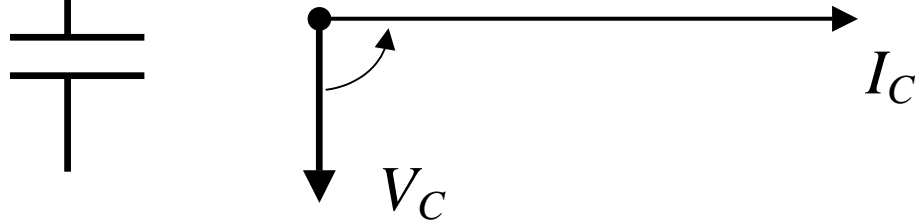Capacitor $V_C = \frac{1}{j\omega C} \cdot I_C$



Inductor $V_L = j\omega L \cdot I_L$

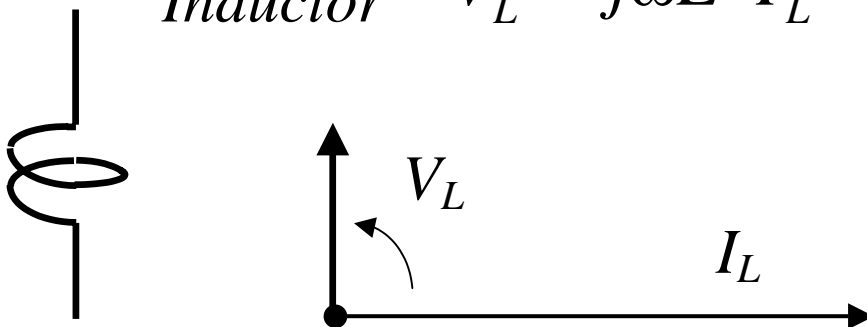

AC signals

Mean value

$$\langle V \rangle_T = \frac{1}{T} \int_0^T V(t) dt$$

Root Mean Square (RMS)

$$V_{RMS} = \sqrt{\langle V^2(t) \rangle}$$

Example: $V = V_m \sin(\omega t)$

$$\langle V \rangle = \frac{2V_m}{\pi} = 0.637V_m$$

$$V_{RMS} = V_m / \sqrt{2} = 0.707V_m$$

