

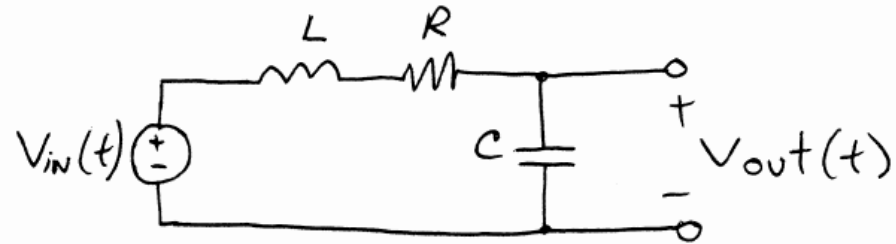


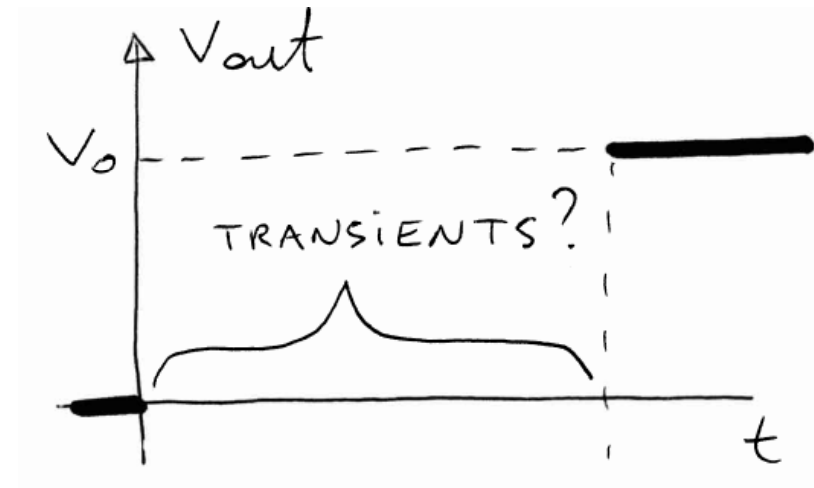Step response of series RLC circuit - output taken across capacitor.




$$V_{in}(t) = V_0 \cdot h(t)$$

$$V_{out}(t) = ?$$

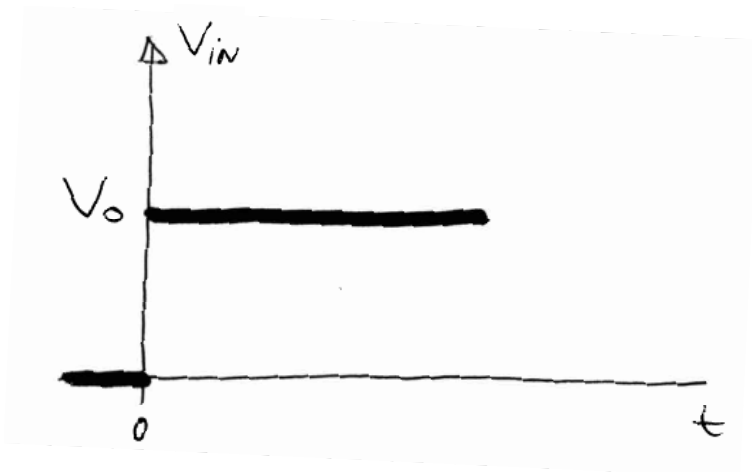

What happens during transient period from initial steady state to final steady state?

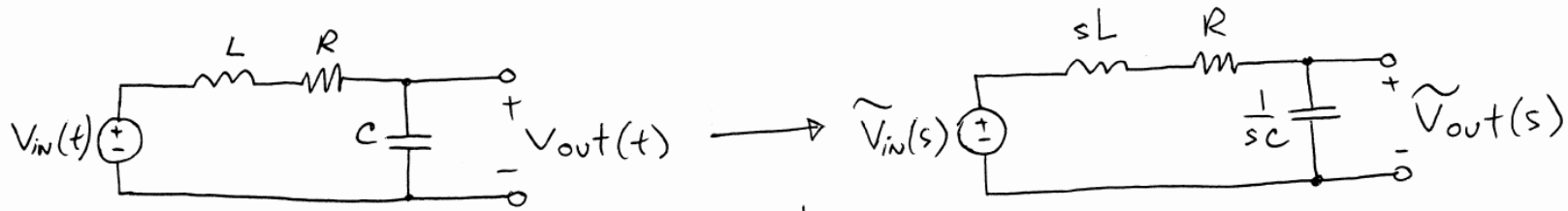Transfer function of series RLC - output taken across capacitor.



$$T(s) = \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} \Big|_{\substack{\text{ZERO} \\ \text{IC}}} = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{1}{LC} \cdot \frac{1}{s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}}$$

Poles: $s^2 + s \cdot \frac{R}{L} + \frac{1}{LC} = 0$ $p_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$

Case 1: $\frac{R^2}{4L^2} > \frac{1}{LC}$, i.e. $R > 2\sqrt{\frac{L}{C}}$ - two different real poles

Case 2: $\frac{R^2}{4L^2} = \frac{1}{LC}$, i.e. $p_1 = p_2 = -\frac{R}{2L}$ - two identical real poles


Case 3: $\frac{R^2}{4L^2} < \frac{1}{LC}$, i.e. $R < 2\sqrt{\frac{L}{C}}$ - complex conjugate poles

$$s^2 + \frac{R}{L} \cdot s + \frac{1}{LC} = s^2 + 2 \cdot \gamma \cdot \omega_n \cdot s + \omega_n^2$$

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \& \quad \gamma = \frac{R}{2} \sqrt{\frac{C}{L}} < 1$$

Case 1: two different real poles.

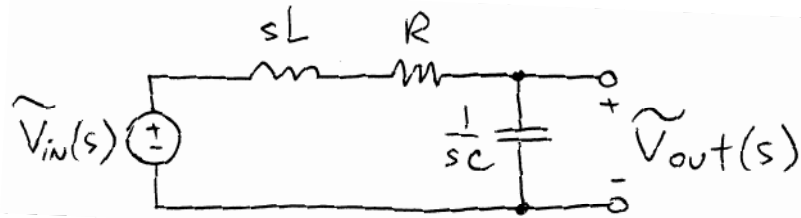Step response of series RLC - output taken across capacitor.



$$R > 2\sqrt{L/C}$$

$$p_1 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_1 < p_2 < 0 \text{ \& } |p_1| > |p_2|$$


$$T(s) = \frac{1}{LC} \cdot \frac{1}{(s-p_1)(s-p_2)}$$

$$\text{STEP}(t) = \mathcal{L}^{-1} \left[\frac{T(s)}{s} \right] = \frac{1}{LC} \cdot \mathcal{L}^{-1} \left[\frac{1}{s(s-p_1)(s-p_2)} \right]$$

$$\frac{1}{s(s-p_1)(s-p_2)} = \frac{A}{s} + \frac{B}{s-p_1} + \frac{C}{s-p_2}$$

$$A = \frac{1}{p_1 \cdot p_2} \quad ; \quad B = \frac{1}{p_1(p_1-p_2)} \quad ; \quad C = \frac{1}{p_2(p_2-p_1)}$$

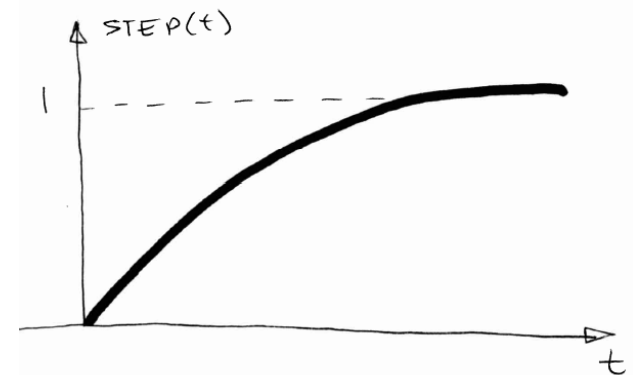
$$\text{STEP}(t) = \frac{1}{LC} \left[A \cdot h(t) + B \cdot e^{p_1 t} \cdot h(t) + C \cdot e^{p_2 t} \cdot h(t) \right]$$



Overdamped case – the circuit demonstrates relatively slow transient response.

Case 1: two different real poles.

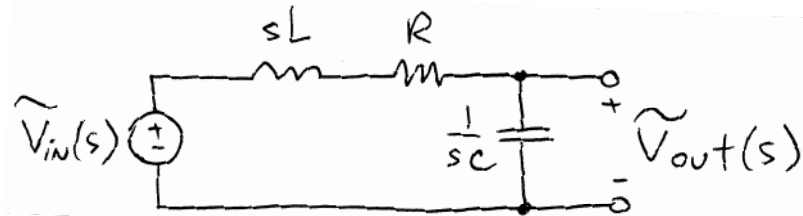Frequency response of series RLC - output taken across capacitor.



$$R > 2\sqrt{L/C}$$


$$p_1 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_1 < p_2 < 0 \text{ \& } |p_1| > |p_2|$$

$$T(j\omega) = \frac{1}{LC} \cdot \frac{1}{(j\omega - p_1)(j\omega - p_2)}$$


$$20 \log |T(j\omega)| = 20 \log \frac{1}{LC} - 20 \log \sqrt{\omega^2 + p_1^2} - 20 \log \sqrt{\omega^2 + p_2^2}$$

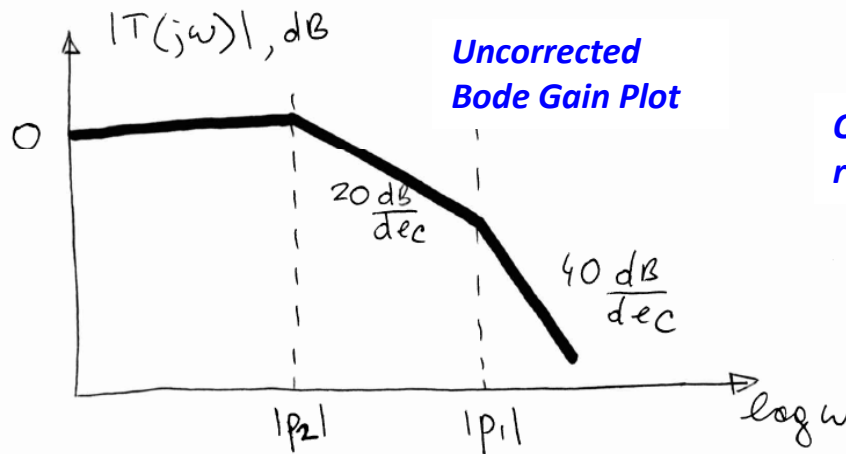

Overdamped case – the circuit demonstrates relatively limited bandwidth


Case 2: two identical real poles.

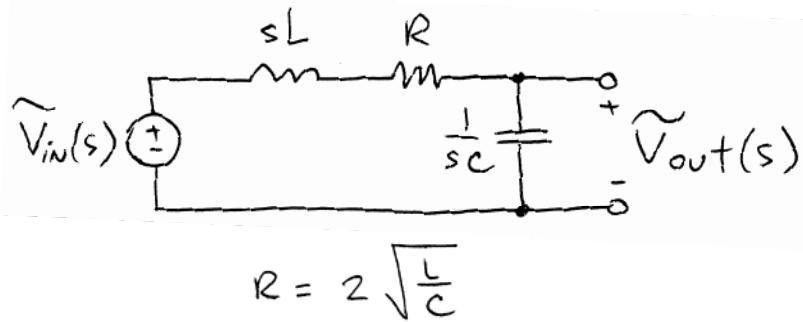Step response of series RLC - output taken across capacitor.



$$p = p_1 = p_2 = -\frac{R}{2L} < 0$$
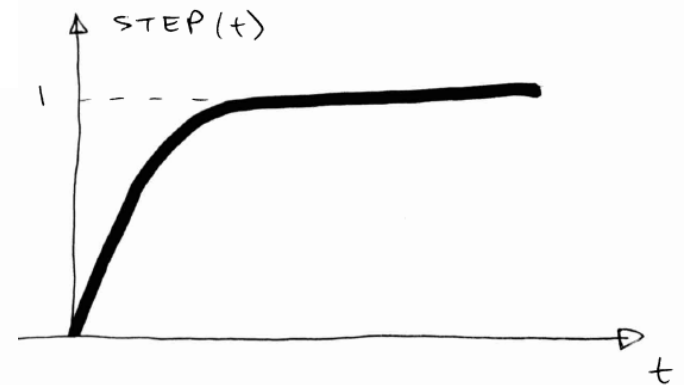
$$T(s) = \frac{1}{LC} \cdot \frac{1}{(s-p)^2}$$



$$\text{STEP}(t) = \mathcal{L}^{-1} \left[\frac{T(s)}{s} \right] = \frac{1}{LC} \mathcal{L}^{-1} \left[\frac{1}{s(s-p)^2} \right]$$

$$\frac{1}{s(s-p)^2} = \frac{A}{s} + \frac{B}{(s-p)^2} + \frac{C}{s-p}$$


$$A = \frac{1}{p^2}; \quad B = \frac{1}{p}; \quad C = -\frac{1}{p^2} \quad \& \quad p = -\frac{R}{2L} = -\frac{1}{\sqrt{LC}}$$

$$\begin{aligned} \text{STEP}(t) &= \frac{1}{LC} \left[A \cdot h(t) + B \cdot t e^{pt} \cdot h(t) + C \cdot e^{pt} \cdot h(t) \right] = \\ &= h(t) + \left(-\frac{t}{\sqrt{LC}} \right) e^{-\frac{t}{\sqrt{LC}}} \cdot h(t) - e^{-\frac{t}{\sqrt{LC}}} \cdot h(t) = \\ &= h(t) - \left[\frac{t}{\sqrt{LC}} + 1 \right] e^{-\frac{t}{\sqrt{LC}}} \cdot h(t) \end{aligned}$$

Critically damped case
 - the circuit demonstrates
 the shortest possible rise
 time without overshoot.

Case 2: two identical real poles.

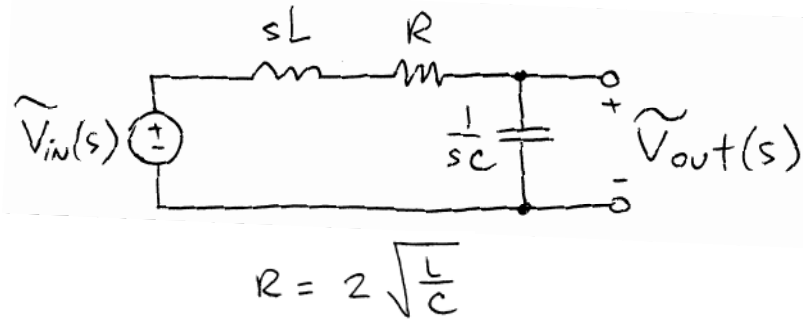Frequency response of series RLC - output taken across capacitor.




$$p = p_1 = p_2 = -\frac{R}{2L} < 0$$

$$T(s) = \frac{1}{LC} \cdot \frac{1}{(s-p)^2}$$

$$T(j\omega) = \frac{1}{LC} \cdot \frac{1}{(j\omega-p)^2} \quad ; \quad p = -\frac{1}{\sqrt{LC}}$$


$$20 \log |T(j\omega)| = 20 \log \frac{1}{LC} - 20 \cdot 2 \cdot \log \sqrt{\omega^2 + p^2}$$

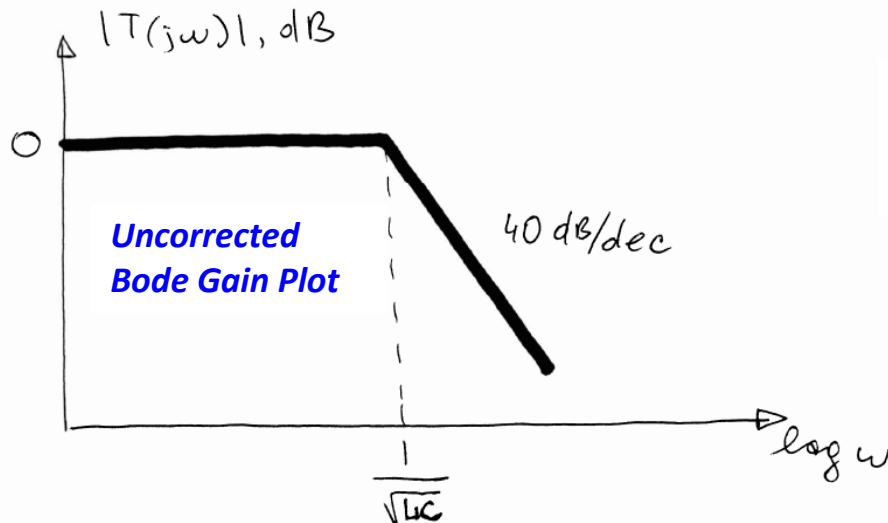

*Critically damped case
– the circuit demonstrates the widest
bandwidth without apparent resonance.*

Case 3: two complex poles.

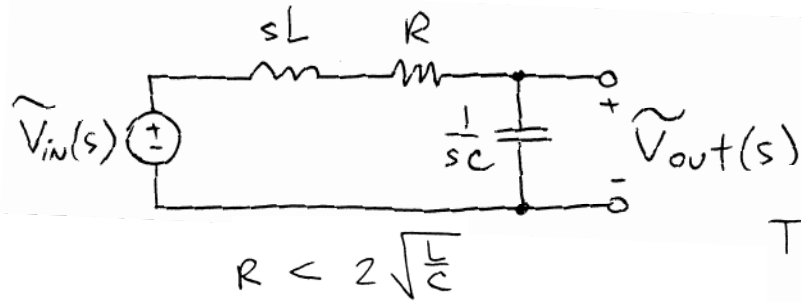Step response of series RLC - output taken across capacitor.



$$p_{1,2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$T(s) = \frac{1}{LC} \cdot \frac{1}{s^2 + 2\gamma\omega_n s + \omega_n^2} = \frac{1}{LC} \cdot \frac{1}{(s-p)(s-p^*)}$$

$$\text{STEP}(t) = L^{-1} \left[\frac{T(s)}{s} \right] = \frac{1}{LC} \cdot L^{-1} \left[\frac{1}{s(s-p)(s-p^*)} \right]$$


$$\frac{1}{s(s-p)(s-p^*)} = \frac{A}{s} + \frac{B}{s-p} + \frac{C}{s-p^*}$$

$$A = \frac{1}{p-p^*} = LC \quad ; \quad B = \frac{1}{p(p-p^*)} \quad ; \quad C = \frac{1}{p^*(p-p^*)} = B^*$$

$$\text{STEP}(t) = h(t) + h(t) \cdot \underbrace{2 \cdot \frac{|B|}{LC}}_{(\omega_n \sqrt{1-\gamma^2})^{-1}} \cdot e^{-\frac{R}{2L}t} \cdot \cos(\omega_n \sqrt{1-\gamma^2} \cdot t + \phi_B)$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

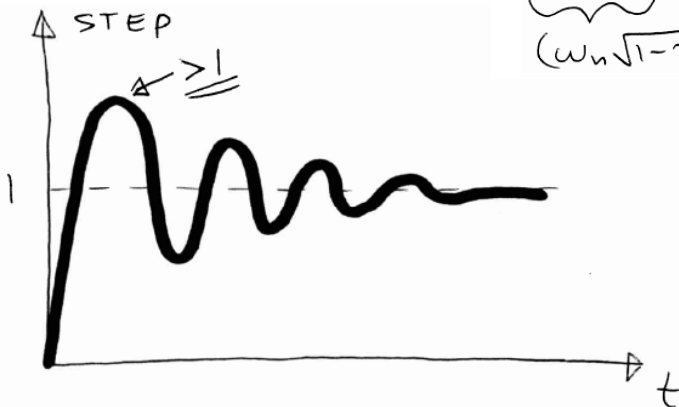
$$\gamma = \frac{R}{2} \sqrt{\frac{C}{L}} < 1$$



Underdamped case – the circuit oscillates.

Case 3: two complex poles.

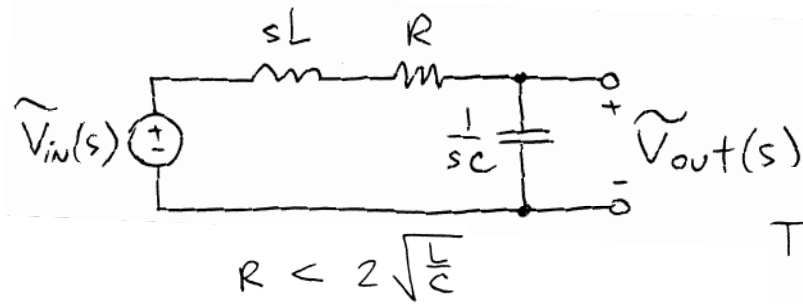Frequency response of series RLC - output taken across capacitor.




$$P_{1,2} = -\frac{R}{2L} \pm j\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$T(s) = \frac{1}{LC} \cdot \frac{1}{s^2 + 2\delta\omega_n s + \omega_n^2} = \frac{1}{LC} \cdot \frac{1}{(s-p)(s-p^*)}$$


$$T(j\omega) = \frac{1}{LC} \cdot \frac{1}{(j\omega)^2 + 2\delta\omega_n(j\omega) + \omega_n^2}$$

$$20 \log |T(j\omega)| = 20 \log \frac{1}{LC} - 20 \log \sqrt{(\omega_n^2 - \omega^2)^2 + (2\delta\omega_n\omega)^2}$$

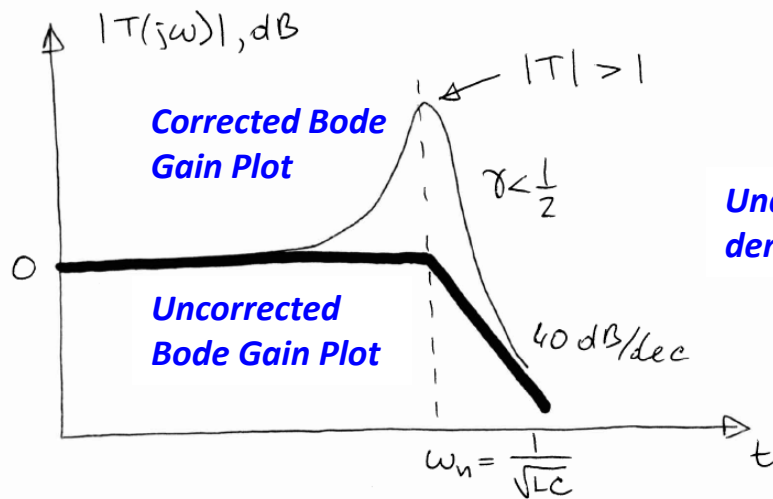

Underdamped case – the circuit can demonstrate apparent resonant behavior.

Series RLC resonance.

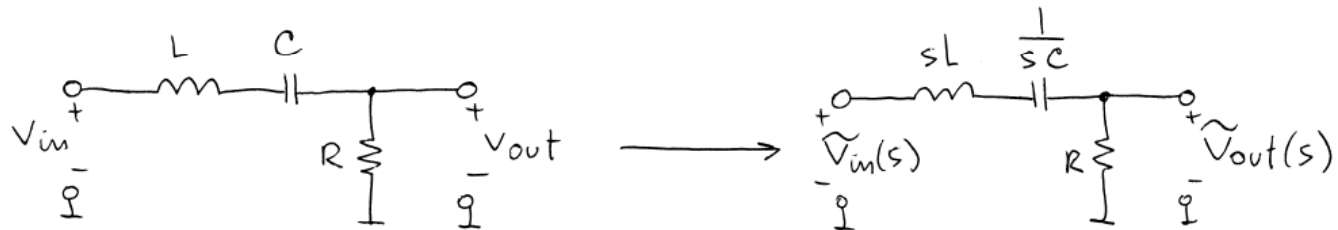

$$T(s) = \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} \Big|_{\text{ZERO IC}} = \frac{R}{sL + \frac{1}{sC} + R} = \frac{R}{L} \cdot \frac{s}{s^2 + \frac{R}{L} \cdot s + \frac{1}{LC}}$$

Zeros: $s = 0 = z$

Poles: $s_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} = p_{1,2}$

Case 1: $\frac{R^2}{4L^2} > \frac{1}{LC}$, i.e. $R > 2\sqrt{\frac{L}{C}}$ - two different real poles


Case 2: $\frac{R^2}{4L^2} = \frac{1}{LC}$, i.e. $p_1 = p_2 = -\frac{R}{2L}$ - two identical real poles

Case 3: $\frac{R^2}{4L^2} < \frac{1}{LC}$, i.e. $R < 2\sqrt{\frac{L}{C}}$ - complex poles

$$s^2 + \frac{R}{L} \cdot s + \frac{1}{LC} = s^2 + 2 \cdot \gamma \cdot \omega_n \cdot s + \omega_n^2$$

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \& \quad \gamma = \frac{R}{2} \sqrt{\frac{C}{L}} < 1$$

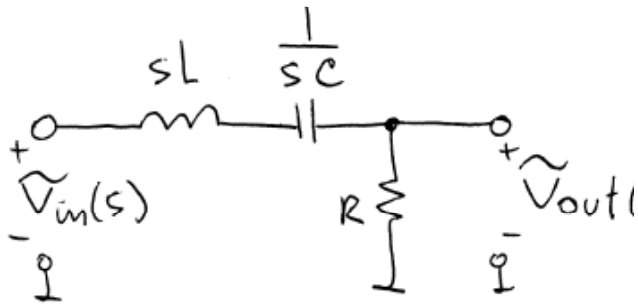Series RLC resonance: Case 1 – two different real poles.



$$R > 2\sqrt{L/C} \Rightarrow$$

$$p_1 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


$$p_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_1 < p_2 < 0 \text{ \& } |p_1| > |p_2|$$

$$T(s) = \frac{R}{L} \cdot \frac{s}{(s-p_1)(s-p_2)}$$


$$T(j\omega) = \frac{R}{L} \frac{j\omega}{(j\omega-p_1)(j\omega-p_2)}$$

$$20 \log |T(j\omega)| = 20 \log \frac{R}{L} + 20 \log \omega - 20 \log \sqrt{\omega^2 + p_1^2} - 20 \log \sqrt{\omega^2 + p_2^2}$$

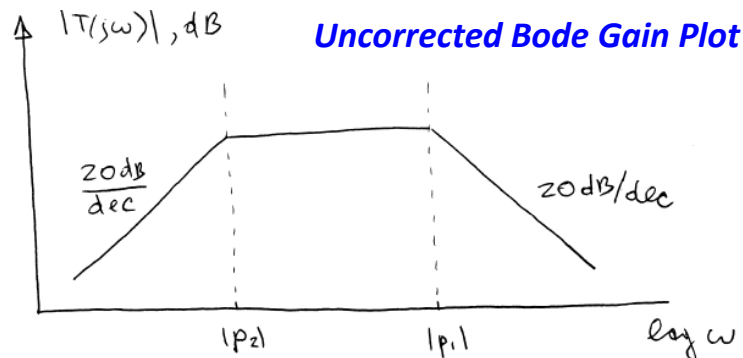

Underdamped case - Resonance is not sharp.

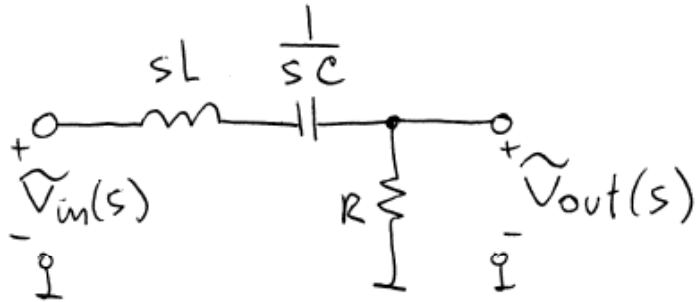Series RLC resonance: Case 2 – two identical real poles.




$$R = 2\sqrt{\frac{L}{C}}$$

$$p = p_1 = p_2 = -\frac{R}{2L} < 0$$

$$T(s) = \frac{R}{L} \cdot \frac{s}{(s-p)^2}$$


$$T(j\omega) = \frac{R}{L} \cdot \frac{j\omega}{(j\omega-p)^2}$$

$$20 \log |T(j\omega)| = 20 \log \frac{R}{L} + 20 \log \omega - 40 \log \sqrt{\omega^2 + p^2}$$

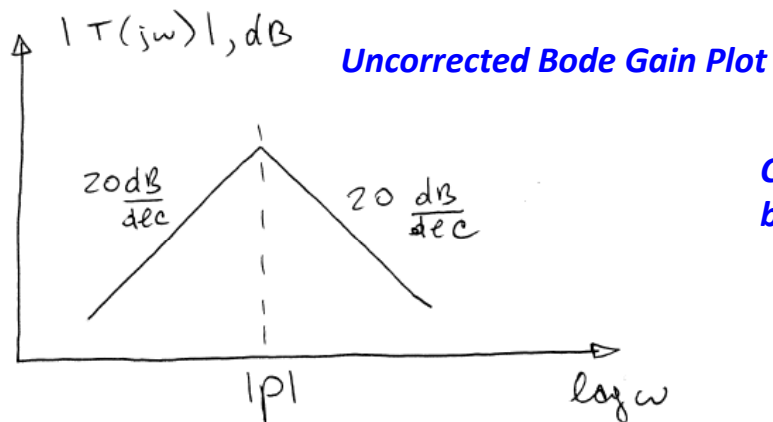

Critically damped case - Resonance is apparent but still not sharp enough.

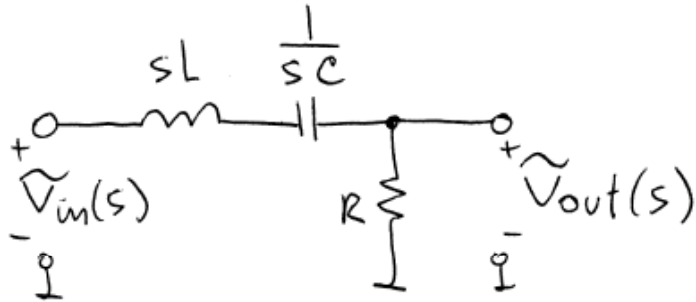Series RLC resonance: Case 3 – complex poles.



$$R < 2\sqrt{\frac{L}{C}}$$


$$P_{1,2} = -\frac{R}{2L} \pm j\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$T(s) = \frac{R}{L} \cdot \frac{s}{s^2 + 2\delta\omega_n s + \omega_n^2}$$

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \delta = \frac{R}{2}\sqrt{\frac{C}{L}} < 1$$

$$T(j\omega) = \frac{R}{L} \cdot \frac{j\omega}{(j\omega)^2 + 2\delta\omega_n j\omega + \omega_n^2}$$

$$20 \log |T(j\omega)| = 20 \log \frac{R}{L} + 20 \log \omega - 20 \log \sqrt{(\omega_n^2 - \omega^2)^2 + (2\delta\omega_n\omega)^2}$$

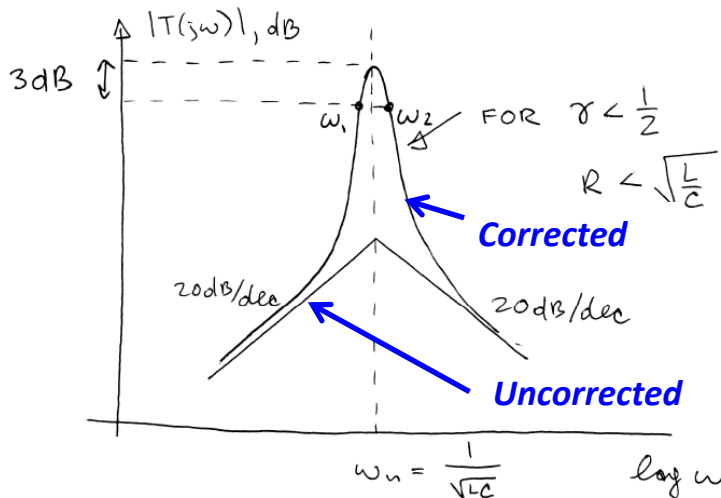


Half power bandwidth: $|T(j\omega)|_{\omega=\omega_1 \text{ or } \omega_2} = \frac{1}{\sqrt{2}}$

$$BW = R/L$$


Quality factor: $Q = \frac{\omega_n}{BW} = \frac{1}{R}\sqrt{\frac{L}{C}}$

Another look at Series RLC resonance.

Bandwidth.

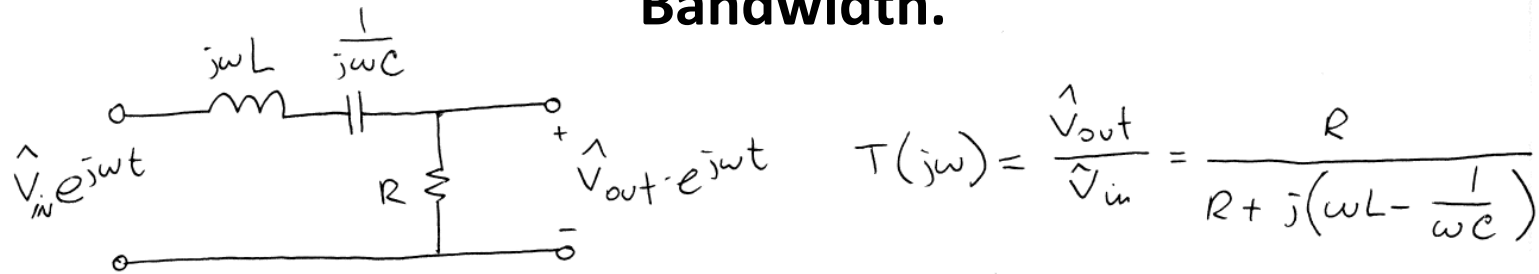

$$|T(j\omega)| = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad ; \quad |T(j\omega_n)| = 1 \quad ; \quad \omega_n = \frac{1}{\sqrt{LC}}$$

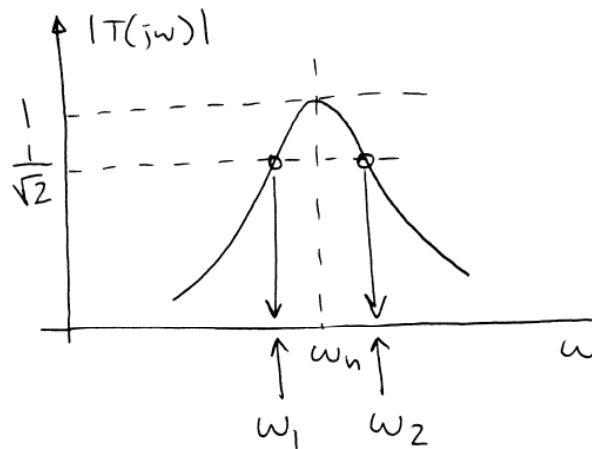

Half power bandwidth:

$$BW = \omega_2 - \omega_1 = \frac{R}{L}$$

$$|T(j\omega)| = \frac{1}{\sqrt{2}} \quad \text{when} \quad R^2 = (\omega L - \frac{1}{\omega C})^2$$

$$(\omega L - \frac{1}{\omega C}) = \pm R$$


$$\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


Another look at Series RLC resonance.

Quality factor.

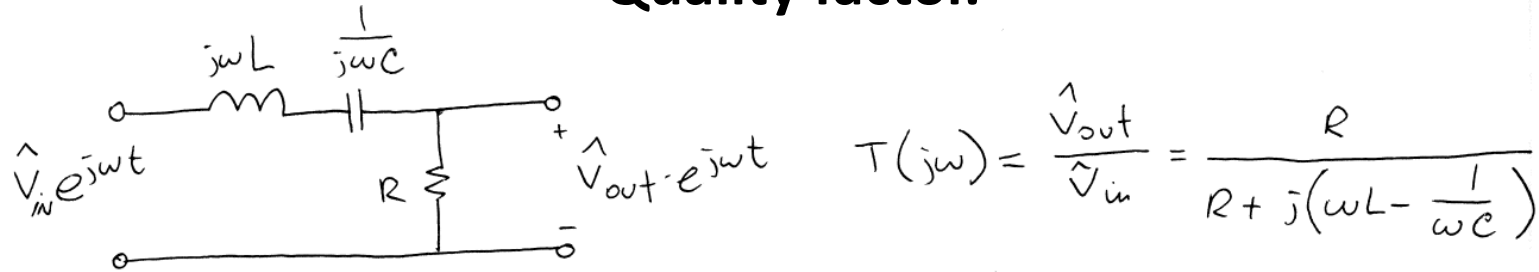

$$|T(j\omega)| = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad ; \quad |T(j\omega_n)| = 1 \quad ; \quad \omega_n = \frac{1}{\sqrt{LC}}$$

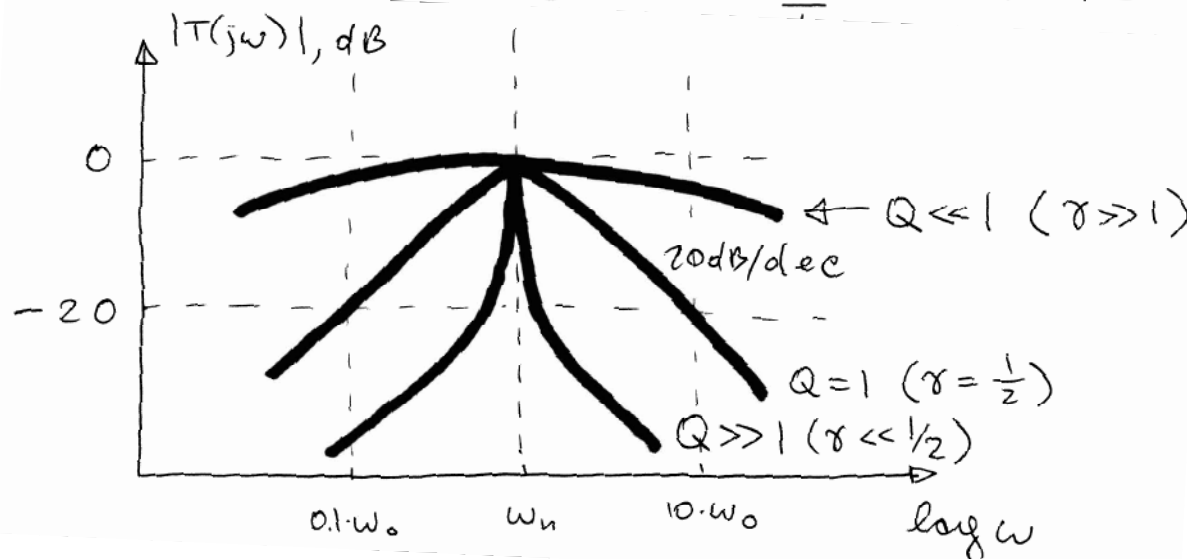Quality factor: $Q = \frac{\omega_n}{BW} = \frac{\frac{1}{\sqrt{LC}}}{\frac{R}{L}} = \frac{1}{R} \cdot \sqrt{\frac{L}{C}} = \frac{1}{2 \cdot \gamma} \quad ; \quad \gamma = \frac{R}{2} \sqrt{\frac{C}{L}}$



High values of Quality factor ensure sharp resonance peak.

Example 1.

Design series RLC circuit with resonant frequency of 1 kHz and quality factor of 100.

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \& \quad Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

ASSUME $C = 1 \mu\text{F}$

$$\Rightarrow L = \frac{1}{(2\pi f_n)^2 \cdot C} = 25.3 \text{ mH}$$

$$\Rightarrow R = \frac{1}{100} \cdot \sqrt{\frac{L}{C}} \approx 1.6 \Omega$$

BUT : L is COIL OF WIRE $\Rightarrow R_L \neq 0$!!!

Inductors have series resistance that is often characterized by inductor Q-factor:


Usual values of inductor Q-factor are 50-200.

Series resistance of the inductor has to be taken into account when calculating R.

$$Q_L = \frac{\omega \cdot L}{r_s}$$

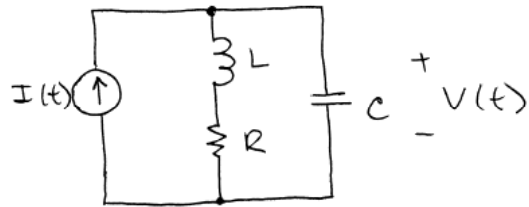Example.

Sketch the Bode Gain Plot of the following circuit:



$$T(s) = \frac{\tilde{V}(s)}{\tilde{I}(s)} = \frac{\frac{1}{sC} \cdot (sL + R)}{\frac{1}{sC} + sL + R}$$

ASSUME $L = 10\text{H}$; $R = 1\Omega$; $C = 0.1\text{F}$


$$T(s) = \frac{\frac{10}{s}(10s + 1)}{\frac{10}{s} + 10s + 1} = 10 \cdot \frac{(s + \frac{1}{10})}{s^2 + \frac{1}{10}s + 1}$$

$$\begin{cases} \text{ZERO:} & z = -\frac{1}{10} \\ \text{poles:} & p_{1,2} = -\frac{1}{20} \pm \sqrt{\frac{1}{400} - 1} = -\frac{1}{20} \pm j\sqrt{1 - \frac{1}{400}} \quad \text{- COMPLEX (UNDER DAMPED)} \end{cases}$$


$$s^2 + \frac{1}{10}s + 1 = s^2 + 2 \cdot \gamma \cdot \omega_n \cdot s + \omega_n^2$$

$$\Rightarrow \omega_n = 1 \text{ RAD/S}$$


$$\gamma = \frac{1}{20}$$

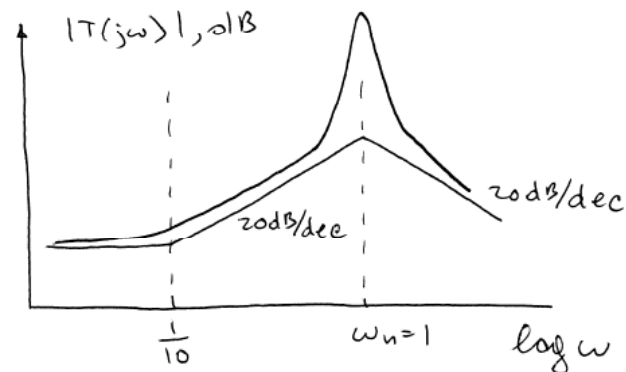

RLC band stop circuit – notch filter.

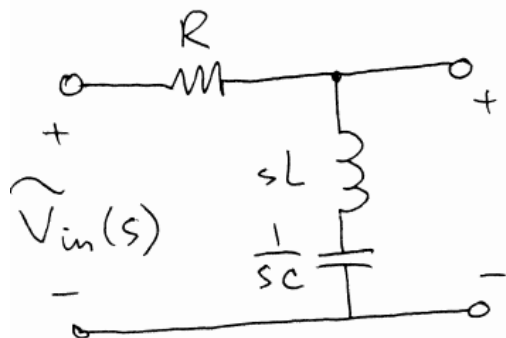
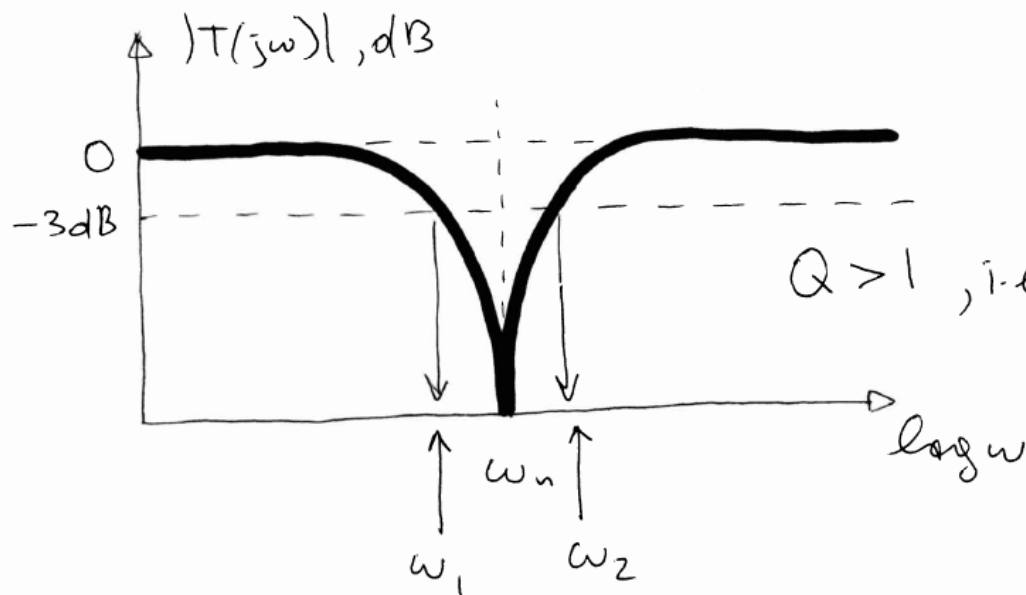
$$T(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}}$$



$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$Q > 1, \text{ i.e. } \gamma = \frac{R}{2} \sqrt{\frac{C}{L}} < \frac{1}{2}$$

$$BW = \omega_2 - \omega_1 = R/L \quad ; \quad Q = \frac{\omega_n}{BW}$$