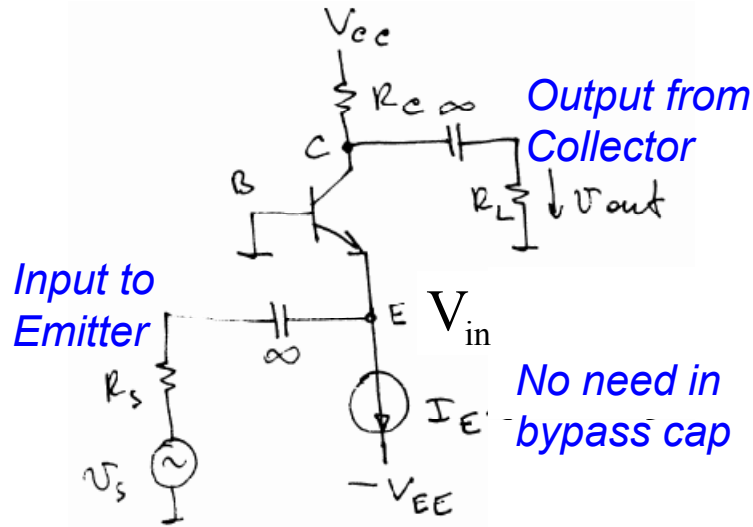


Common Base  
Biased by current source



Start with bias DC analysis – make sure BJT is in FA, then calculate small signal parameters for AC analysis.

\*ignore  $r_o$  for simplicity, then:

$$A_v = \frac{v_{out}}{v_{in}} = g_m (R_L \parallel R_c) \quad \text{noninverting}$$

$$A_{v0} = A_v |_{R_L = \infty} = g_m R_c$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{r_{\pi}}{\beta + 1} \quad \text{Small!}$$


$$R_{out} = \frac{v_{out}}{i_{out}} \Big|_{v_s = 0} = R_c$$

$$G_v = \frac{v_{out}}{v_s} = \frac{R_{in}}{R_{in} + R_s} \cdot A_v \approx \frac{R_L \parallel R_c}{R_s}$$

Short circuit current gain

$$\frac{i_{out}}{i_{in}} \Big|_{R_L = 0} = \alpha \approx 1$$

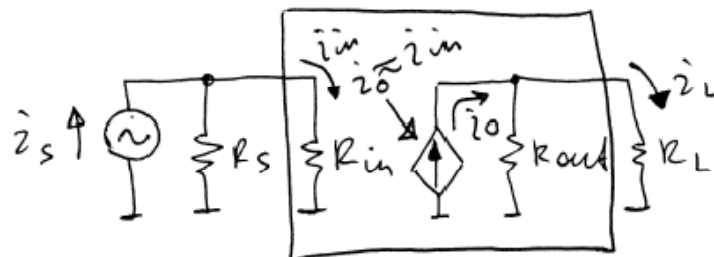
The circuit is current buffer: delivers current from source to load




\* when BJT output impedance  $r_o$  can not be neglected – the circuit is said to perform an impedance transformation.

# Common Collector amplifier

Again.  
No need for  $C_E$ !

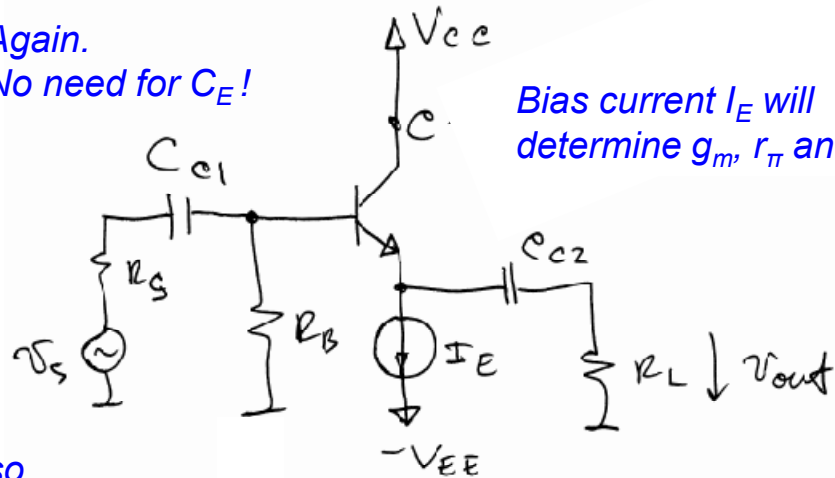


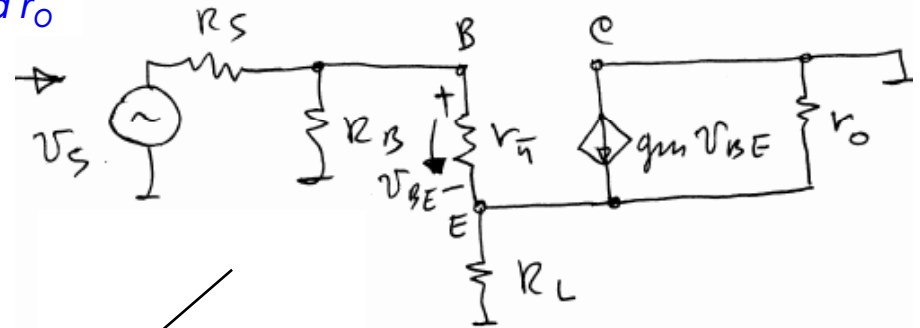Bias current  $I_E$  will determine  $g_m$ ,  $r_\pi$  and  $r_o$




Also  
 $R_B$  and  $C_{C1}$  can be eliminated

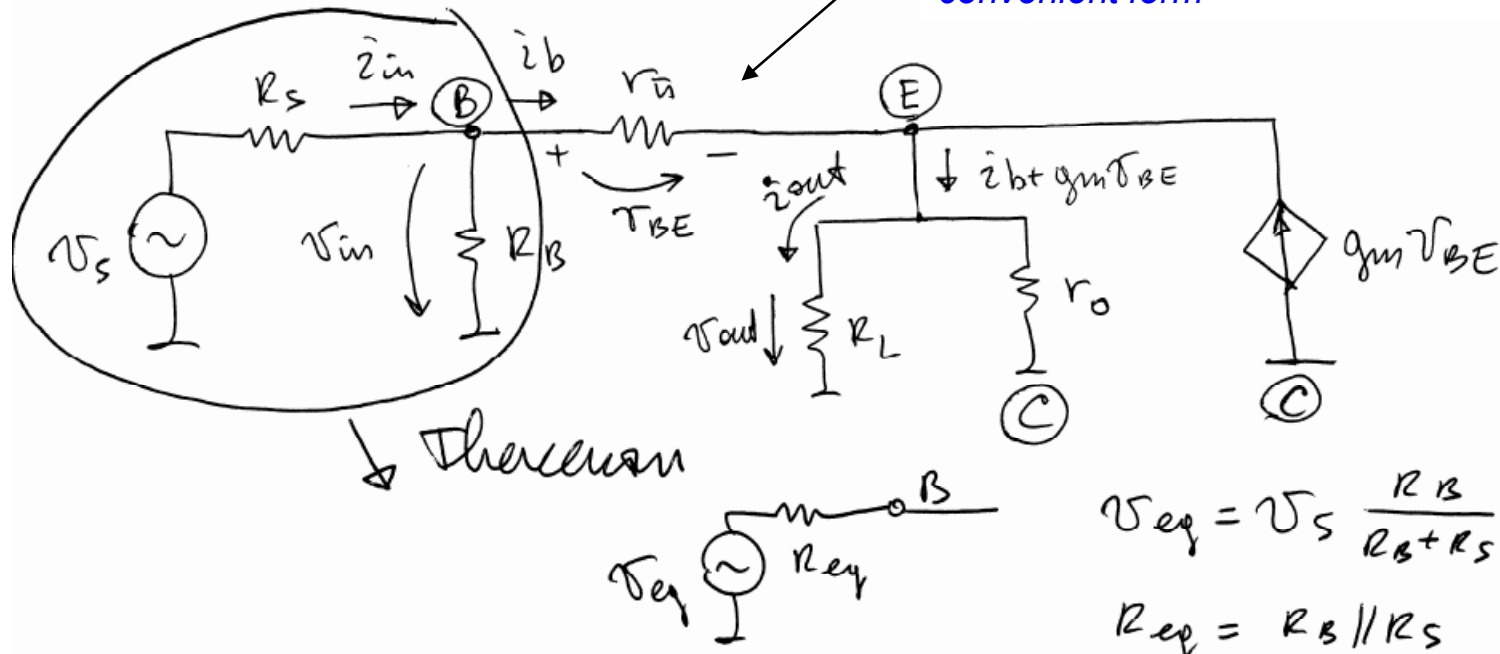Redraw equivalent circuit in more convenient form



## Common Collector amplifier

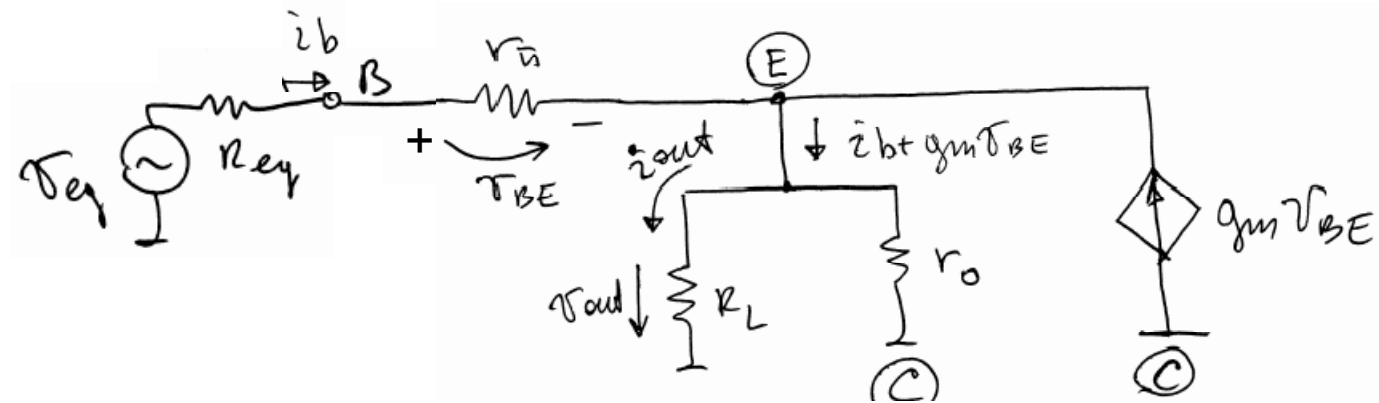

$$v_{eq} = v_s \frac{R_B}{R_B + R_S} = i_b (r_{\pi} + R_{eq}) + v_{out}$$

$$v_{out} = (i_b + g_m v_{BE}) \cdot (R_L \parallel r_o) = i_b \underbrace{(1 + \beta)}_{g_m r_{\pi}} (R_L \parallel r_o)$$


$$G_V = \frac{v_{out}}{v_s} = \frac{v_{out}}{v_{eq}} \cdot \frac{v_{eq}}{v_s} = \frac{R_B}{R_S + R_B} \cdot \frac{(\beta + 1) (R_L \parallel r_o)}{\underbrace{(r_{\pi} + R_B \parallel R_S) + (\beta + 1) (R_L \parallel r_o)}_{< 1}} < 1$$

When  
 $R_B \gg R_S$   
 $r_o \gg R_L$

$$G_V = \frac{(\beta + 1) R_L}{\underbrace{[R_S + r_{\pi}]_{k\Omega}} + R_L \underbrace{(\beta + 1)}_{\substack{\downarrow \\ k\Omega \\ 100}} \approx 1$$

i.e. no voltage gain !

## Common Collector amplifier

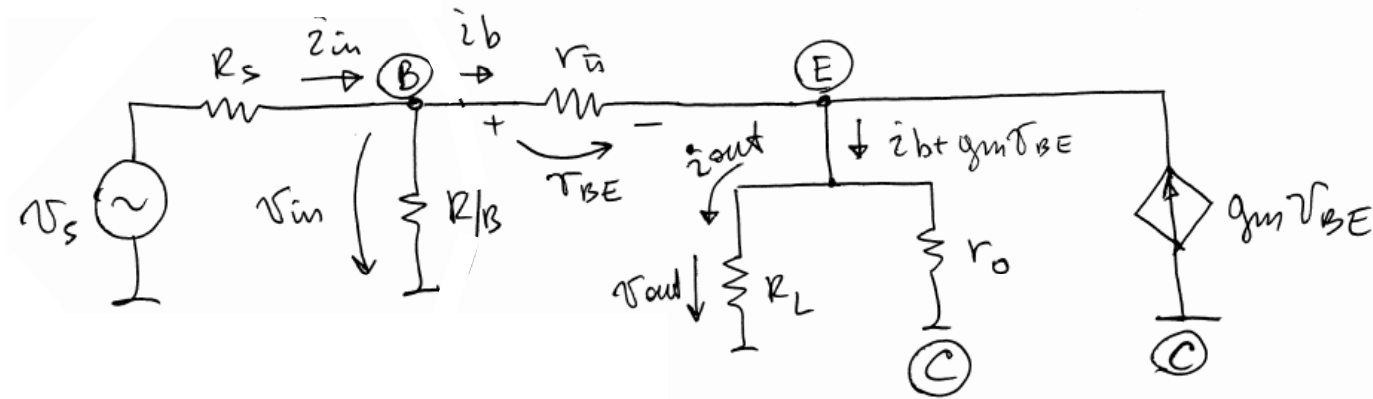

Input impedance

$$R_{in} = \frac{v_{in}}{i_{in}}$$

$$v_{in} = i_b \cdot r_{\pi} + \overbrace{(\beta+1)(R_L \parallel r_o)}^{v_{out}} \cdot i_b$$

$$i_{in} = v_{in}/R_B + i_b = i_b \left( \frac{r_{\pi}}{R_B} + 1 + \frac{\beta+1}{R_B} (R_L \parallel r_o) \right)$$

$$R_{in} = \frac{[r_{\pi} + (\beta+1)(R_L \parallel r_o)] \cdot R_B}{R_B + [r_{\pi} + (\beta+1)(R_L \parallel r_o)]} = R_B \parallel (r_{\pi} + (\beta+1)(R_L \parallel r_o))$$


can be  $\infty$ 
 $\downarrow$   $\approx R_B$ 
 $\downarrow$   $\approx R_B$ 
 $\downarrow$   $100 \Omega$ 
 $\downarrow$   $100 \Omega$

$$R_{in} \approx (\beta+1) \cdot R_L, \text{ for } R_L \ll r_o$$

Impedance transformation

## Common Collector amplifier

Output impedance

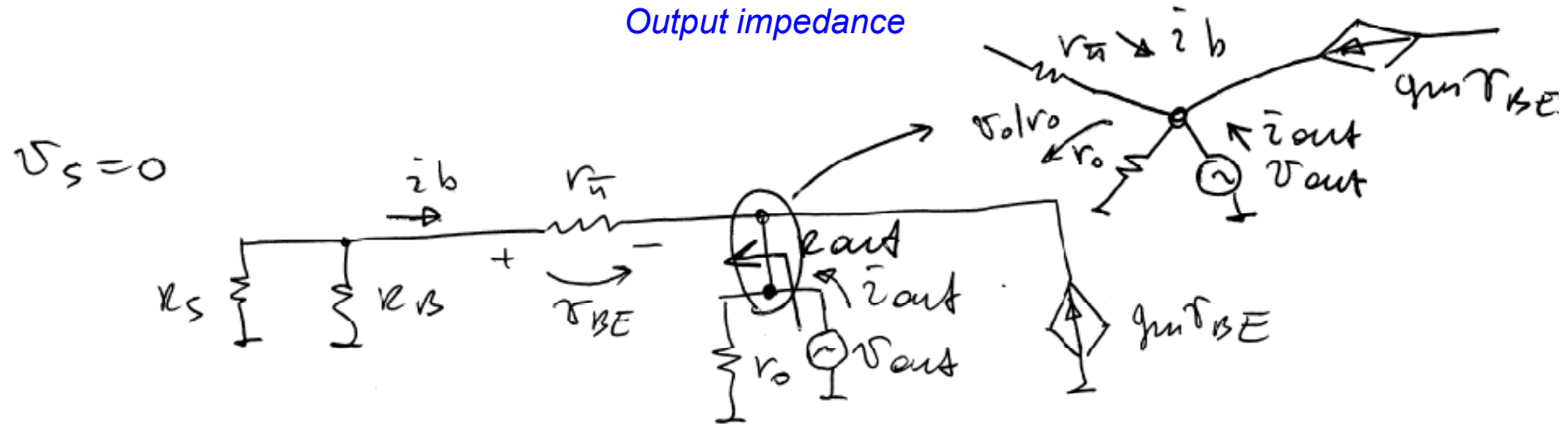

$$V_{out} = -\dot{i}_b (R_s \parallel R_B) - V_{BE} = -\dot{i}_b (R_s \parallel R_B + r_{\pi})$$

$$\begin{aligned} \dot{i}_{out} &= \frac{V_{out}}{r_o} - \dot{i}_b - g_m V_{BE} = \\ &= -\dot{i}_b \frac{R_s \parallel R_B + r_{\pi}}{r_o} - \dot{i}_b - \dot{i}_b \cdot \beta \end{aligned}$$


$$R_{out} = \frac{r_{\pi} + R_s \parallel R_B}{(\beta + 1) + \frac{r_{\pi} + R_s \parallel R_B}{r_o}} = \left( r_o \parallel \frac{r_{\pi} + (R_s \parallel R_B)}{\beta + 1} \right)$$

$$R_B \gg R_s \text{ \& } r_o \gg \text{all then } R_{out} \approx \frac{R_s}{\beta + 1}$$

$R_s \gg r_{\pi}$

Impedance transformation
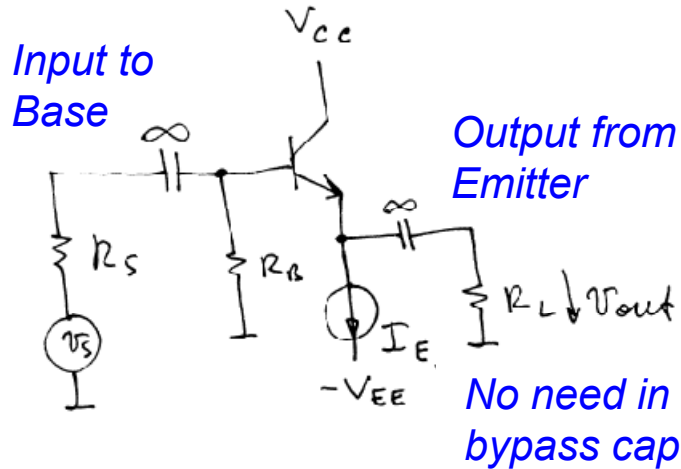
## Common Collector (Emitter follower) Biased by current source



Start with bias DC analysis – make sure BJT is in FA, then calculate small signal parameters for AC analysis.

$$G_v = \frac{v_{out}}{v_s} = \frac{R_B}{R_s + R_B} \cdot \frac{(\beta + 1)(R_L \parallel r_o)}{[(R_s \parallel R_B) + r_{\pi}] + (\beta + 1)(R_L + r_o)} < 1$$

Often  $R_B \gg R_s$  and  $r_o \gg R_L$ , then

$$G_v \approx \frac{(\beta + 1) \cdot R_L}{(R_s + r_{\pi}) + R_L(\beta + 1)} \approx 1$$


Short circuit current gain is almost the same as in case of CE amp, namely  $\beta + 1$ .

$$R_{in} = \frac{v_{in}}{i_{in}} = \left[ \underbrace{R_B}_{\infty} \parallel \left( \underbrace{r_{\pi}}_{\sim 1k\Omega} + (\beta + 1) \left( \underbrace{R_L}_{\sim 100} \parallel \underbrace{r_o}_{\sim 100k\Omega} \right) \right) \right] \approx (\beta + 1) \cdot R_L$$

*Impedances transformed*

$$R_{out} = \frac{v_{out}}{i_{out}} \Big|_{v_s=0} = r_o \parallel \frac{r_{\pi} + (R_s \parallel R_B)}{\beta + 1} \approx \frac{R_s}{\beta + 1}$$

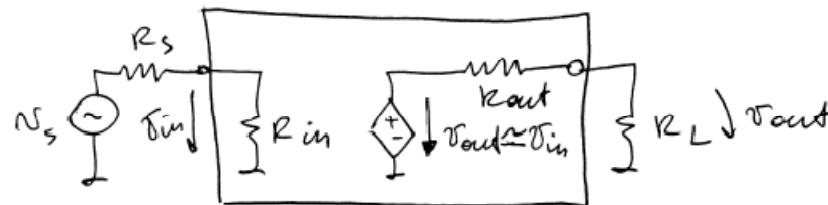The circuit is voltage buffer: delivers voltage from source to load





## Frequency response of Common Emitter amplifier

Low frequencies, i.e. BJT itself is fast enough

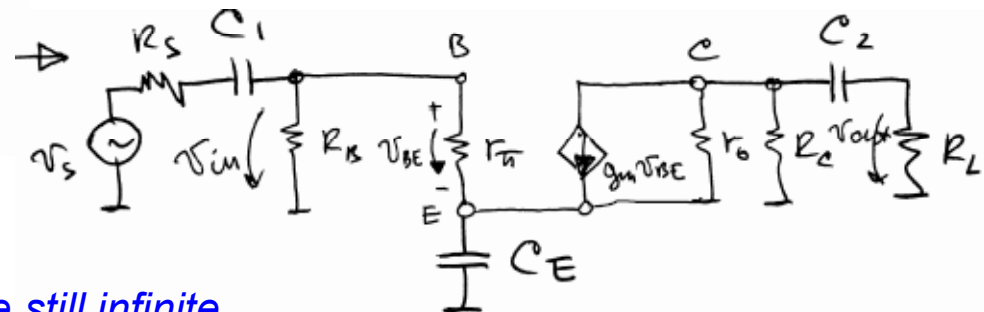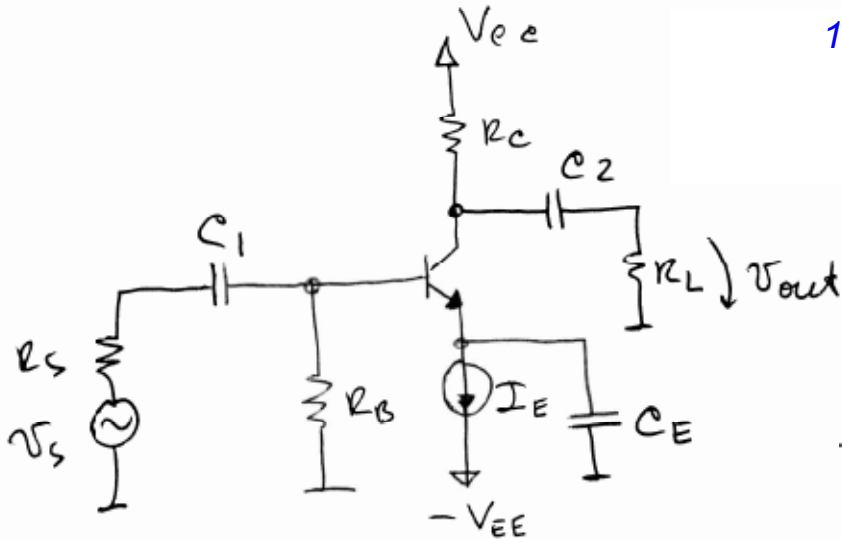
1. DC bias – make sure BJT is in FA - AC analysis.

**Before** – assumed coupling caps are big enough to act as a short circuit for any frequency of AC signal.

**Now** – assume they have finite values.



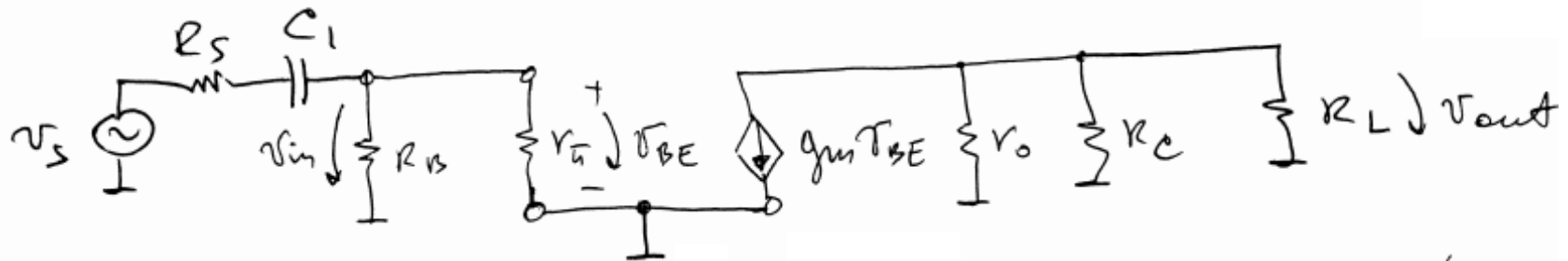
1. Assume  $C_1$  is finite while  $C_2$  and  $C_E$  are still infinite.



$$G_v(f) = \frac{v_{out}(f)}{v_s(f)} = \underbrace{\frac{v_{out}(f)}{v_{in}(f)}}_{\text{Frequency independent}} \cdot \underbrace{\frac{v_{in}(f)}{v_s(f)}}_{\text{Depends on frequency}}$$


Frequency independent.
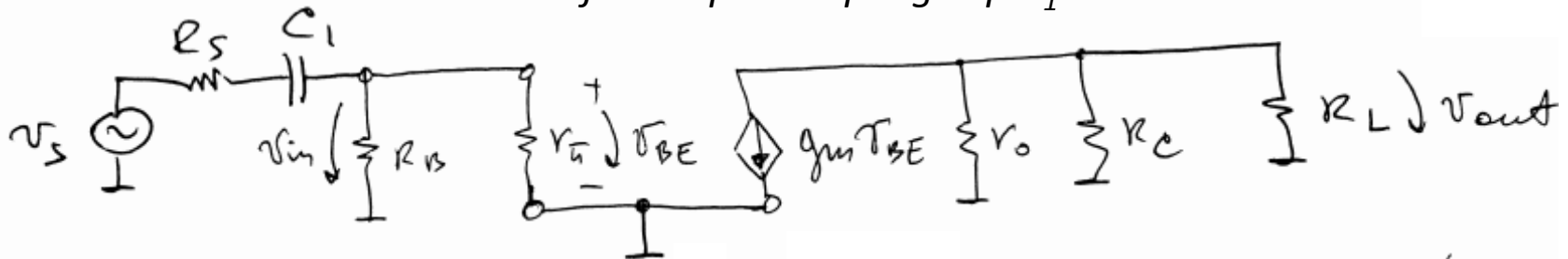
## Frequency response of Common Emitter amplifier Role of the input coupling cap $C_1$



$$G_V(f) = \frac{v_{out}(f)}{v_s(f)} = \underbrace{\frac{v_{out}(f)}{v_{in}(f)}}_{\text{Voltage gain found before}} \cdot \underbrace{\frac{v_{in}(f)}{v_s(f)}}_{\text{Depends on frequency.}}$$


Voltage gain found before  $(-g_m)(r_o || R_C || R_L) = A_V$

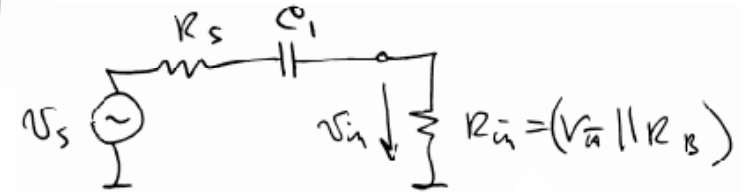


$$\frac{v_{in}}{v_s} = \frac{R_{in}}{R_s + R_{in} + \frac{1}{j\omega C_1}} = \frac{R_{in}}{R_s + R_{in}} \cdot \frac{j f / f_{L1}}{1 + j f / f_{L1}}$$

Input voltage divider found before.

High Pass Filter

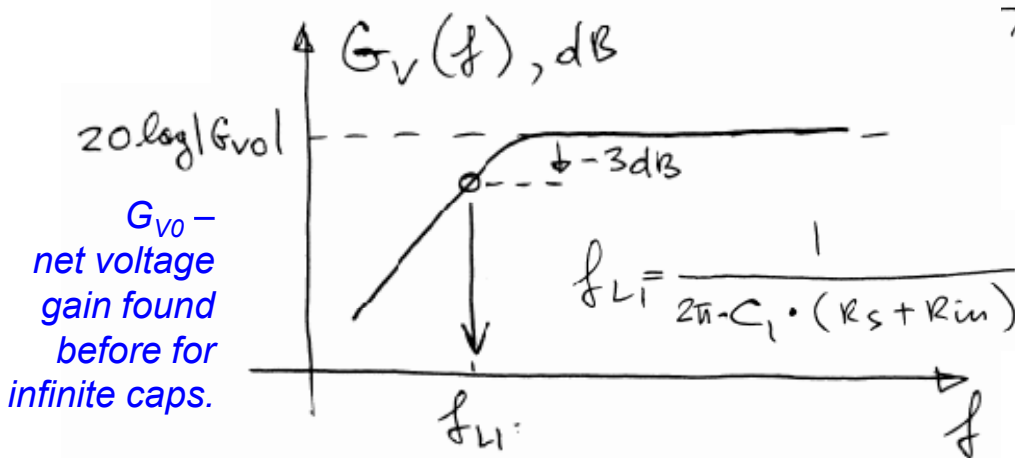

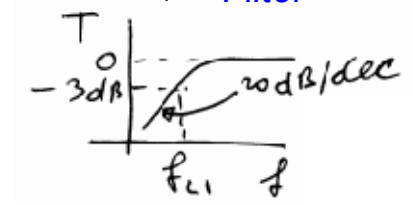
$G_{V0}$  - net voltage gain found before for infinite caps.





## Frequency response of Common Emitter amplifier Role of the output coupling cap $C_2$

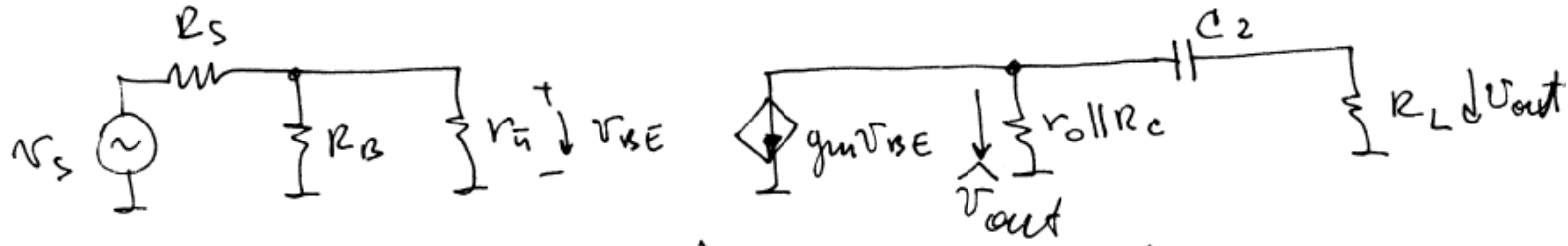2. Assume  $C_2$  is finite while  $C_1$  and  $C_E$  are still infinite.



$$G_v(f) = \frac{v_{out}(f)}{v_s(f)} = \frac{\hat{v}_{out}(f)}{v_s(f)} \cdot \frac{v_{out}(f)}{\hat{v}_{out}(f)}$$

$$G_v(f) = \frac{R_{in}}{R_{in} + R_s} \cdot A_{v0} \cdot \frac{R_L}{R_{out} + R_L + \frac{1}{j\omega C_2}}$$

$$G_v(f) = \underbrace{\frac{R_{in}}{R_{in} + R_s} \cdot A_{v0} \cdot \frac{R_L}{R_L + R_{out}}}_{G_{v0}} \cdot \underbrace{\frac{R_L + R_{out}}{R_L + R_{out} + \frac{1}{j\omega C_2}}}_{\text{High Pass Filter}}$$


Again High Pass Filter but with 3dB frequency defined by  $C_2$

$G_{v0}$  – net voltage gain found before for infinite caps.

$$= \frac{j f / f_{L2}}{1 + j f / f_{L2}}, \quad f_{L2} = \frac{1}{2\pi (R_L + R_{out}) \cdot C_2}$$

## Frequency response of Common Emitter amplifier Role of the bypass cap $C_E$

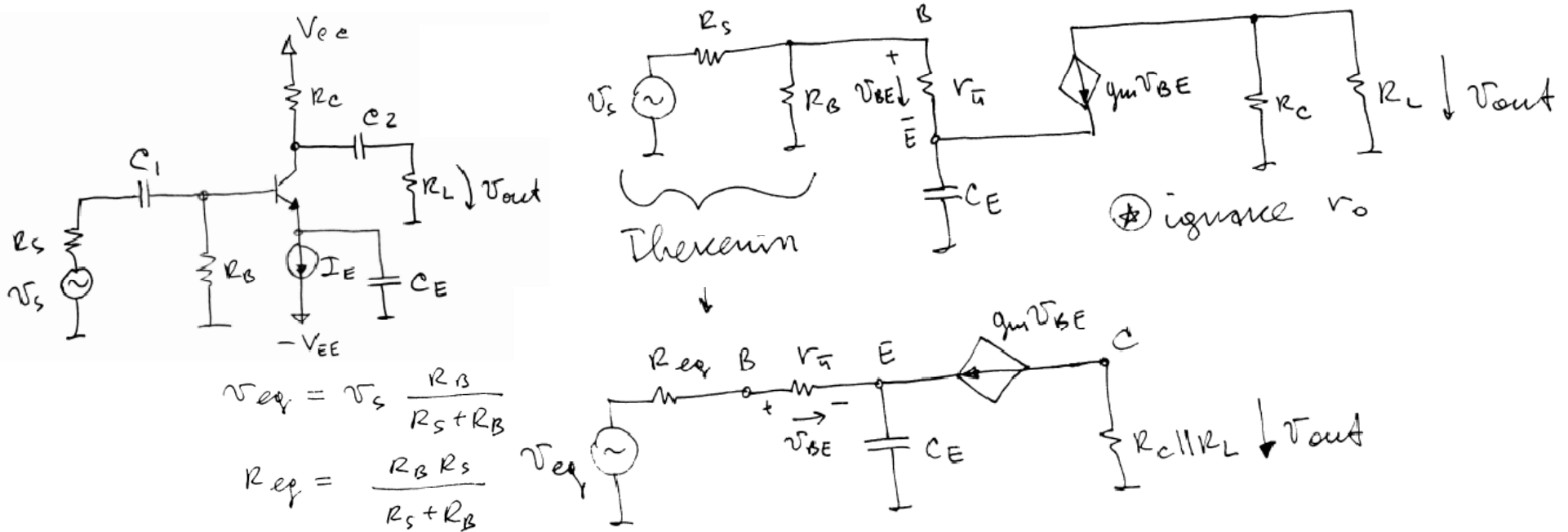3. Assume  $C_E$  is finite while  $C_1$  and  $C_2$  are still infinite.



$$v_{eq} = v_s \frac{R_B}{R_s + R_B}$$

$$R_{eq} = \frac{R_B R_s}{R_s + R_B}$$



$$G_v(f) = \frac{v_{out}}{v_s} = \frac{-g_m v_{BE} (R_C \parallel R_L)}{\frac{R_s + R_B}{R_B} \cdot v_{eq}} \propto \frac{v_{BE}}{v_{eq}}$$

$$\frac{v_{BE}}{v_{eq}} = \frac{z_b \cdot r_{\pi}}{(r_{\pi} + R_{eq})z_b + z_b(\beta + 1) \frac{1}{j\omega C_E}} = \frac{r_{\pi}}{r_{\pi} + R_{eq}} \cdot \frac{j\omega(r_{\pi} + R_{eq}) \frac{C_E}{\beta + 1}}{j\omega(r_{\pi} + R_{eq}) \frac{C_E}{\beta + 1} + 1}$$

$$\text{Hence: } G_v = G_{v0} \cdot \frac{jf/f_{L3}}{1 + jf/f_{L3}} ; f_{L3} = \frac{1}{2\pi (r_{\pi} + R_{eq}) \frac{C_E}{\beta + 1}}$$

## Frequency response of Common Emitter amplifier

### Low frequency

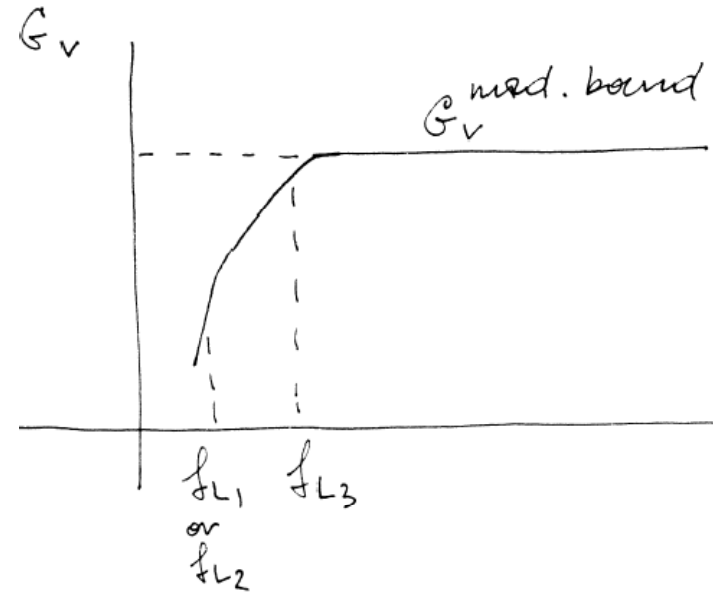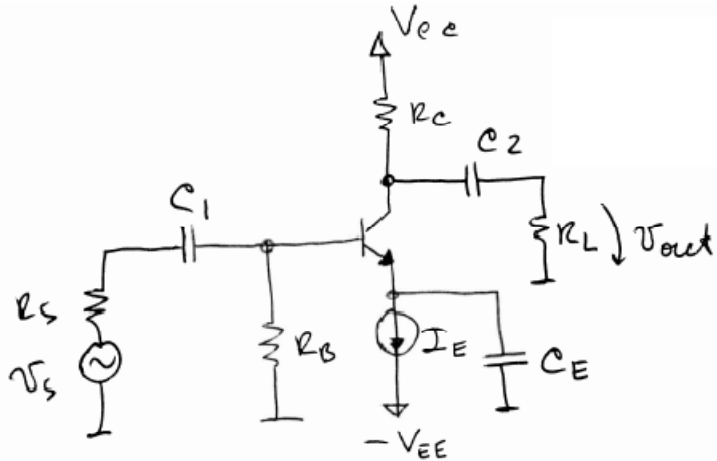

We have identified three HPF.

$$T_i(f) = \frac{j \cdot f / f_{L1}}{1 + j \cdot f / f_{L1}}$$

$$f_{L1} = \frac{1}{2 \cdot \pi \cdot C_1 \cdot (R_{in} + R_S)}$$

$$f_{L2} = \frac{1}{2 \cdot \pi \cdot C_2 \cdot (R_{out} + R_L)}$$

$$f_{L3} = \frac{1}{2 \cdot \pi \cdot \frac{C_E}{\beta + 1} \cdot (r_\pi + R_S \parallel R_B)}$$

$$C_1 = C_2 = C_E = 1 \mu$$


$$R_{in} + R_S \sim k\Omega \rightarrow f_{L1} < 200\text{Hz}$$

$$R_{out} + R_L \sim 10k\Omega \rightarrow f_{L2} < 20\text{Hz}$$



$$r_\pi + R_S \parallel R_B \sim k\Omega \rightarrow f_{L3} > k\text{Hz}$$

Low frequency cutoff is determined by  $C_E$
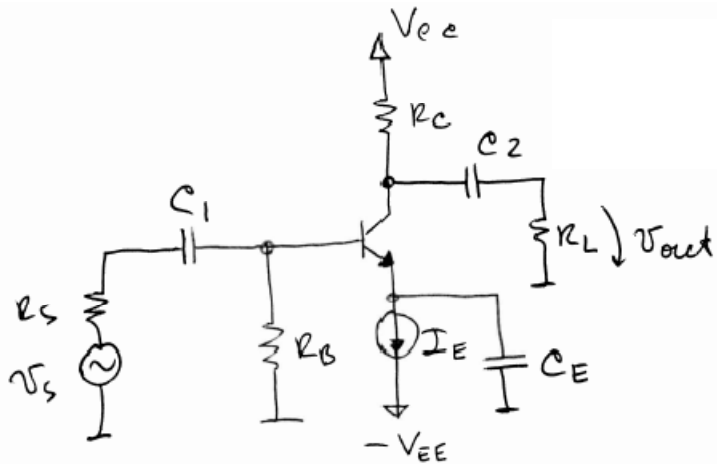
## Frequency response of Common Emitter amplifier Bandwidth




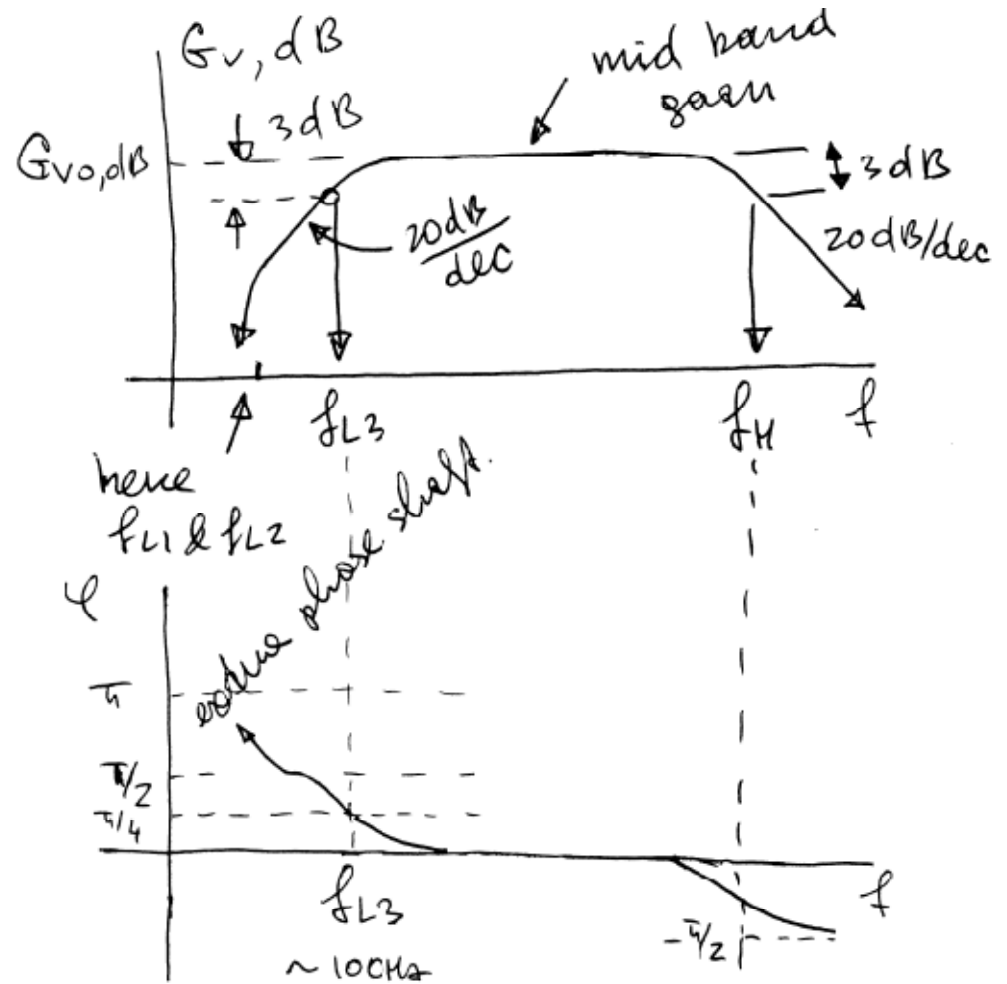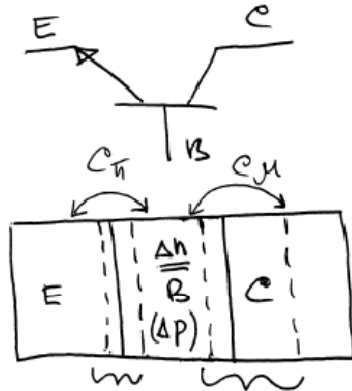High frequency 3dB determines amplifier bandwidth.



Amplifier bandwidth is determined by BJT high frequency capabilities – determined by internal parasitic capacitances  $C_{\pi}$  and  $C_{\mu}$ .
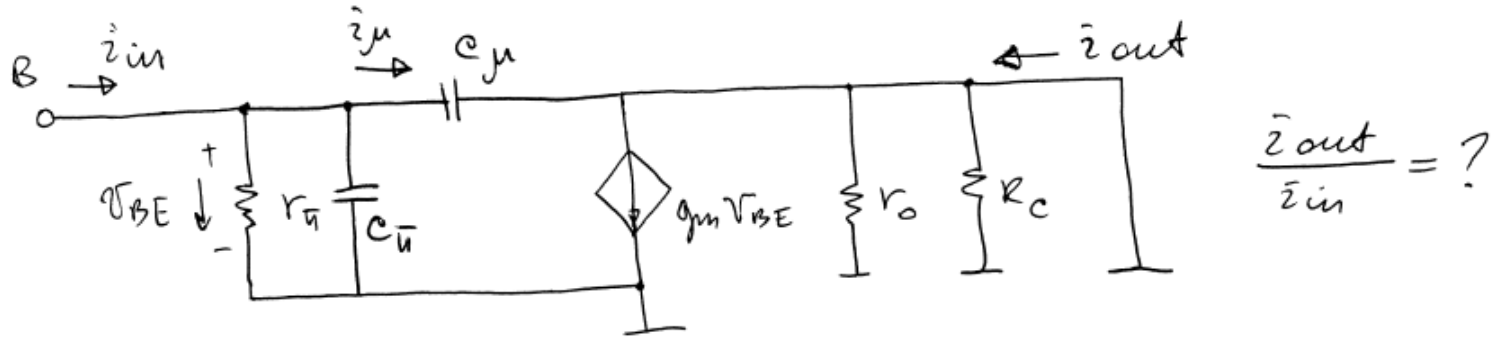
## Frequency response of Common Emitter amplifier Short circuit current gain at high frequencies



$$\frac{\bar{i}_{out}}{\bar{i}_{in}} = ?$$

①.  $C_{\pi} = C_{\mu} = 0 \quad \left( \frac{\bar{i}_{out}}{\bar{i}_{in}} \right) = \frac{g_m v_{BE}}{i_b} = g_m \cdot r_{\pi} = \beta_0$   
↑ Common emitter current gain defined earlier.

②  $C_{\pi} \& C_{\mu} \neq 0$

$$\bar{i}_{out} = g_m v_{BE} - \bar{i}_{\mu} = g_m v_{BE} - \frac{v_{BE}}{\frac{1}{j\omega C_{\mu}}} = (g_m - j\omega C_{\mu}) \cdot v_{BE}$$

$$\bar{i}_{in} = \frac{v_{BE}}{r_{\pi}} + \frac{v_{BE}}{\frac{1}{j\omega C_{\pi}}} + \frac{v_{BE}}{\frac{1}{j\omega C_{\mu}}}$$

*Negligible since  $\ll \beta_0$  for not extreme frequencies.*


⊛  $C_{\pi} \sim 1 \text{ pF}$   
 $C_{\mu} \sim 0.1 \text{ pF}$   
 $f_{\beta} \sim 10 \text{ MHz}$

$$\frac{\bar{i}_{out}(\omega)}{\bar{i}_{in}(\omega)} = \frac{g_m - j\omega C_{\mu}}{\frac{1}{r_{\pi}} + j\omega(C_{\pi} + C_{\mu})} = \frac{\beta_0 - j f (2\pi r_{\pi} \cdot C_{\mu})}{1 + j f / f_{\beta}} \quad f_{\beta} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$
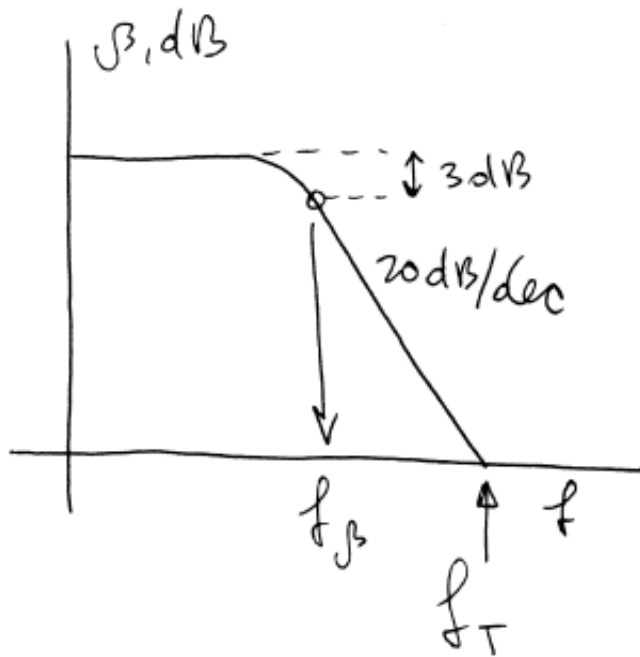
## Frequency response of Common Emitter amplifier Short circuit current gain at high frequencies

$$\beta(f) \approx \frac{\beta_0}{1 + j f / f_{\beta}}$$

$$f_{\beta} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$




Unity gain bandwidth  $f_T$ .

$$\beta(f_T) = 1 = \left| \frac{\beta_0}{1 + j f_T / f_{\beta}} \right| \approx \frac{\beta_0 \cdot f_{\beta}}{f_T}$$

$$f_T = \beta_0 \cdot f_{\beta} = \frac{\beta_0}{r_{\pi}} \cdot \frac{1}{2\pi (C_{\pi} + C_{\mu})} = \frac{g_m}{2\pi (C_{\pi} + C_{\mu})}$$

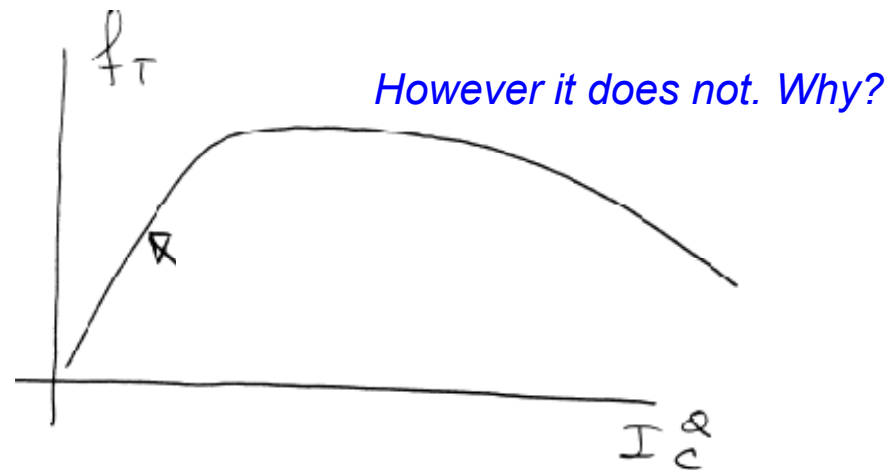Looks like it is supposed to improve with bias current because  $g_m = \frac{I_C}{V_{th}}$




However it does not. Why?

Frequency response of Common Emitter amplifier  
 Frequency dependence of common base current gain


$$\alpha(f) = \frac{\beta(f)}{\beta(f) + 1}$$

$$\alpha(f) = \frac{\beta_0}{1 + \beta_0 + j f / f_\beta} = \frac{\alpha_0}{1 + j f / (f_\beta (1 + \beta_0))} \approx \frac{\alpha_0}{1 + j f / f_T}$$

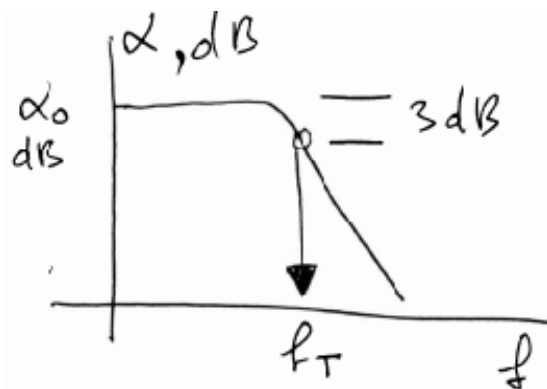3dB frequency for  $\alpha$  is equal to  $f_T$ .



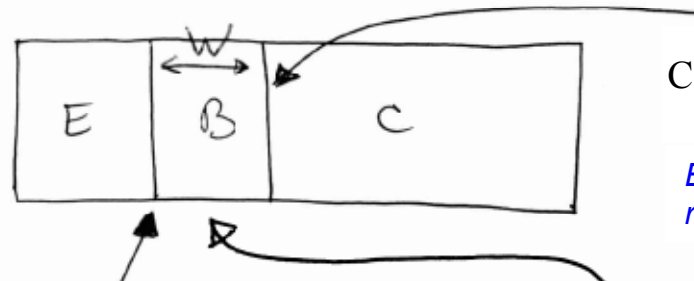Hence at  $f_T$  electrons from emitter can not reach collector.



$$C_{BC}(V_{CB}) = \frac{C_{BC0}}{(1 + V_{CB}/V_{bi})^{1/2}}$$

BC-junction depletion region capacitance

$$C_{BE}(V_{BE}) = \frac{C_{BE0}}{(1 - V_{BE}/V_{bi})^{1/2}}$$


EB-junction depletion region capacitance

Base transport time – time of flight of electrons from emitter to collector.

\*There are also several parasitic caps associated with technology limitations

## Frequency response of Common Emitter amplifier
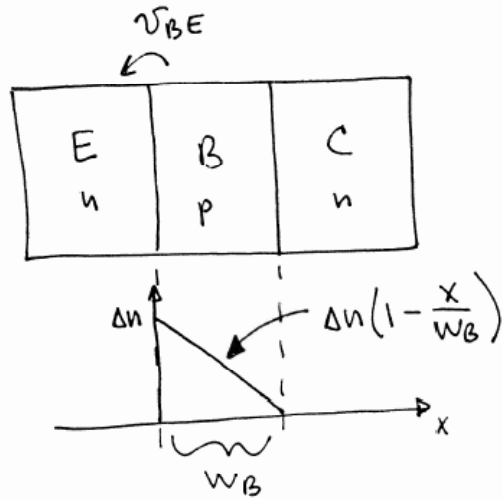
### *Base transport time and associated diffusion capacitance*



*time of flight of electrons from emitter to collector.*

$$\tau_{TF} = \frac{W_B}{v_{diff}} \approx \frac{W_B^2}{2D_n}$$

*\*Need thin base for high speed operation*


$$J_{diff} = q \cdot D_n \cdot \frac{dn}{dx} = q \cdot n \cdot \underbrace{\left( \frac{D_n}{n} \cdot \frac{dn}{dx} \right)}$$

*Effective velocity of diffusion electrons* →  $v_{diff}$ .



## Frequency response of Common Emitter amplifier
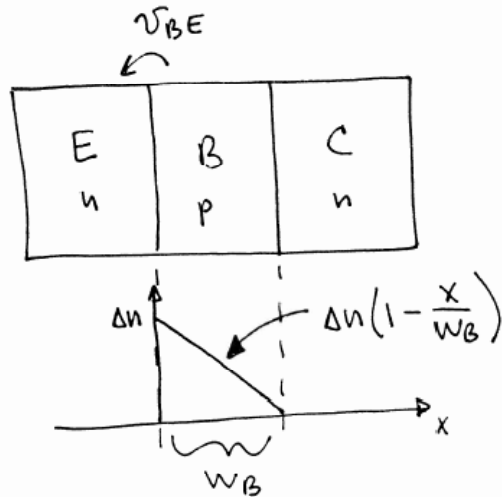
### *Base transport time and associated diffusion capacitance*



*time of flight of electrons from emitter to collector.*

$$\tau_{TF} = \frac{W_B}{v_{diff}} \approx \frac{W_B^2}{2D_n}$$

*\*Need thin base for high speed operation*

*Electron charge stored in base when current  $I_C$  is flowing*

$$Q_{TF} = I_c \cdot \tau_{TF} \approx q \frac{\Delta n}{2} \cdot W_B$$

$$C_{TF} = \left. \frac{dQ_{TF}}{dV_{BE}} \right|_{I_c^Q} = \tau_{TF} \cdot \left. \frac{dI_c}{dV_{BE}} \right|_{I_c^Q} = \tau_{TF} \cdot g_m$$

$$C_{\pi} = \underbrace{C_{TF}} + \underbrace{C_{BEj}} \quad ; \quad C_{\mu} = \underbrace{C_{CBj}}$$

*Charge storage capacitance*

*Pn-junction depletion region capacitances and other parasitic caps*

## Frequency response of Common Emitter amplifier Unity gain bandwidth

$$C_{\pi} = C_{TF} + C_{BEj} \quad \& \quad C_{\mu} = C_{CBj}$$

$$= \tau_{TF} \cdot g_m$$

$$f_T = \frac{g_m}{2\pi (C_{BEj} + C_{CBj}) + 2\pi \cdot g_m \cdot \tau_{TF}} = \frac{1}{2\pi \tau_T}$$

Total time delay

$$\tau_T = \tau_{TF} + \frac{C_{BEj} + C_{CBj}}{g_m} \quad \& \quad g_m \sim I_c^{\alpha}$$

Minimum possible time delay

Ultimate limit for BJT speed

