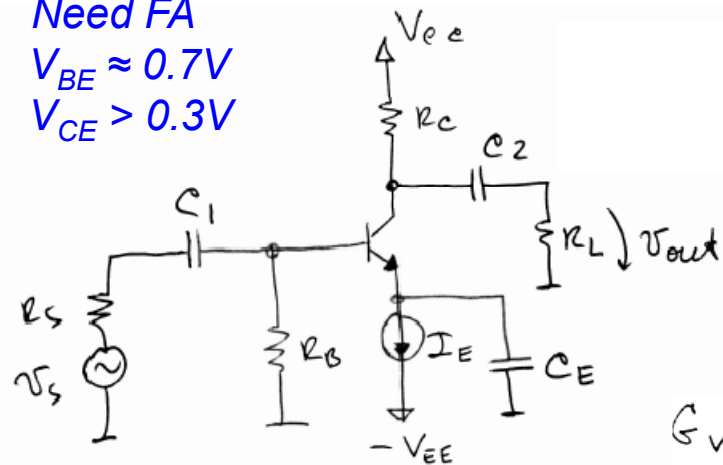


Last time: BJT CE low frequency response


Need FA

$$V_{BE} \approx 0.7V$$

$$V_{CE} > 0.3V$$



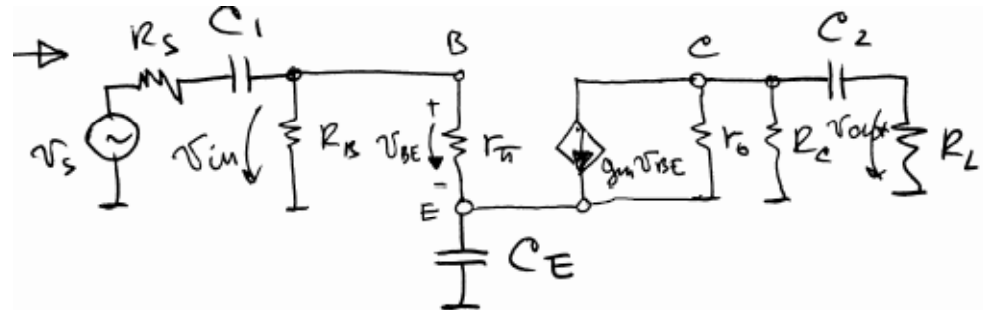
Equivalent circuit for low frequency small signal analysis



$$g_m = \left(\frac{dI_E}{dV_{BE}} \right)_{I_C^Q} = \frac{I_C^Q}{V_{th}}$$

$$r_\pi = \frac{dV_{BE}}{dI_B} \bigg|_{I_B^Q} = \frac{\beta}{g_m}$$

$$r_o = \frac{dV_{CE}}{dI_C} \bigg|_{I_C^Q} = \frac{V_A}{I_C^Q}$$

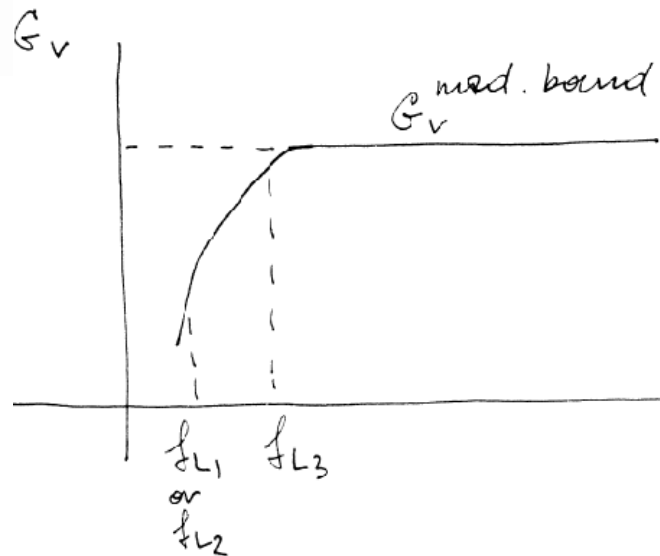

$$T_i(f) = \frac{j \cdot f / f_{L1}}{1 + j \cdot f / f_{L1}}$$

$$f_{L1} = \frac{1}{2 \cdot \pi \cdot C_1 \cdot (R_{in} + R_s)}$$


$$f_{L2} = \frac{1}{2 \cdot \pi \cdot C_2 \cdot (R_{out} + R_L)}$$

$$f_{L3} = \frac{1}{2 \cdot \pi \cdot \frac{C_E}{\beta + 1} \cdot (r_\pi + R_s \parallel R_B)}$$

Coupling and bypass capacitors result into high pass filters (as could be expected).

Role of the bypass cap C_E

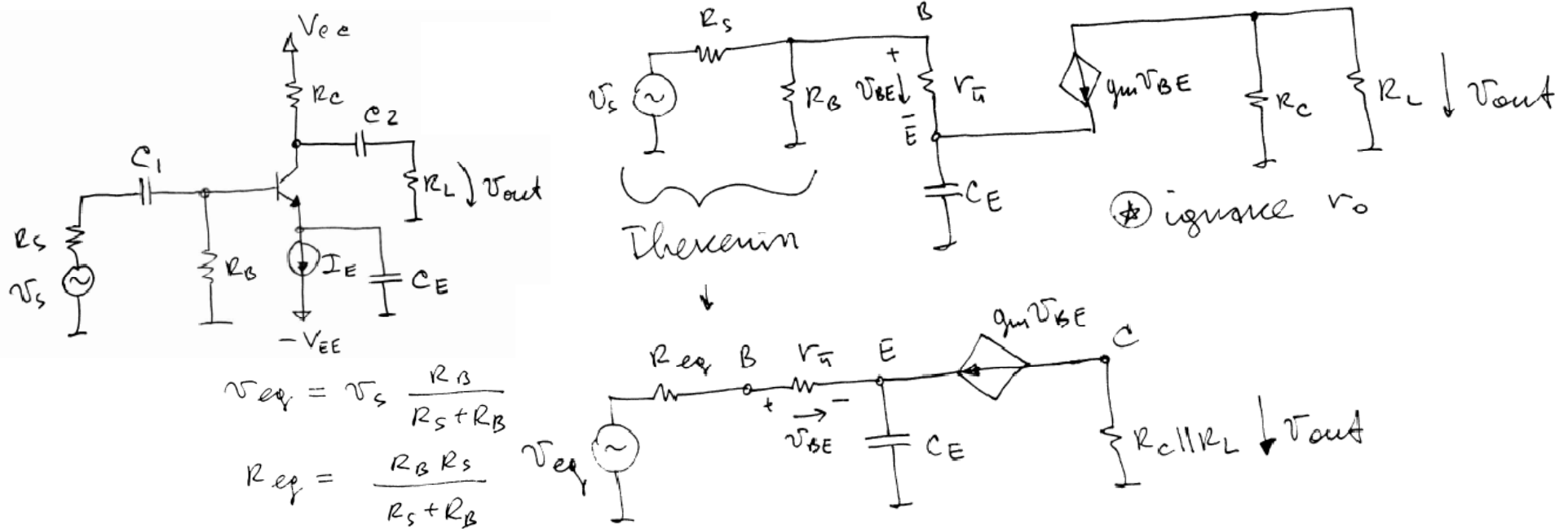3. Assume C_E is finite while C_1 and C_2 are still infinite.



$$V_{eq} = V_s \frac{R_B}{R_s + R_B}$$


$$R_{eq} = \frac{R_B R_s}{R_s + R_B}$$

$$G_v(f) = \frac{V_{out}}{V_s} = \frac{-g_m V_{BE} (R_C \parallel R_L)}{\frac{R_s + R_B}{R_B} \cdot V_{eq}} \propto \frac{V_{BE}}{V_{eq}}$$



$$\frac{V_{BE}}{V_{eq}} = \frac{\cancel{z_b} \cdot r_\pi}{(r_\pi + R_{eq}) \cancel{z_b} + \cancel{z_b} (\beta + 1) \frac{1}{j\omega C_E}} = \frac{r_\pi}{r_\pi + R_{eq}} \cdot \frac{j\omega (r_\pi + R_{eq}) \frac{C_E}{\beta + 1}}{j\omega (r_\pi + R_{eq}) \frac{C_E}{\beta + 1} + 1}$$

$$\text{Hence: } G_v = G_{v0} \cdot \frac{j f / f_{L3}}{1 + j f / f_{L3}} ; f_{L3} = \frac{1}{2\pi (r_\pi + R_{eq}) \frac{C_E}{\beta + 1}}$$

Bandwidth of Common Emitter amplifier

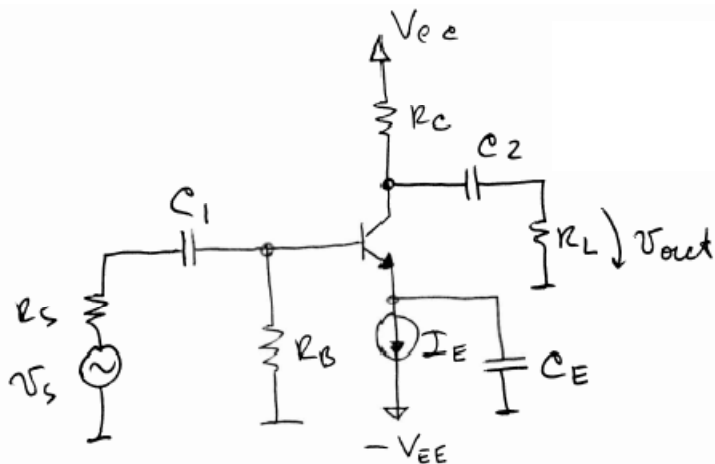


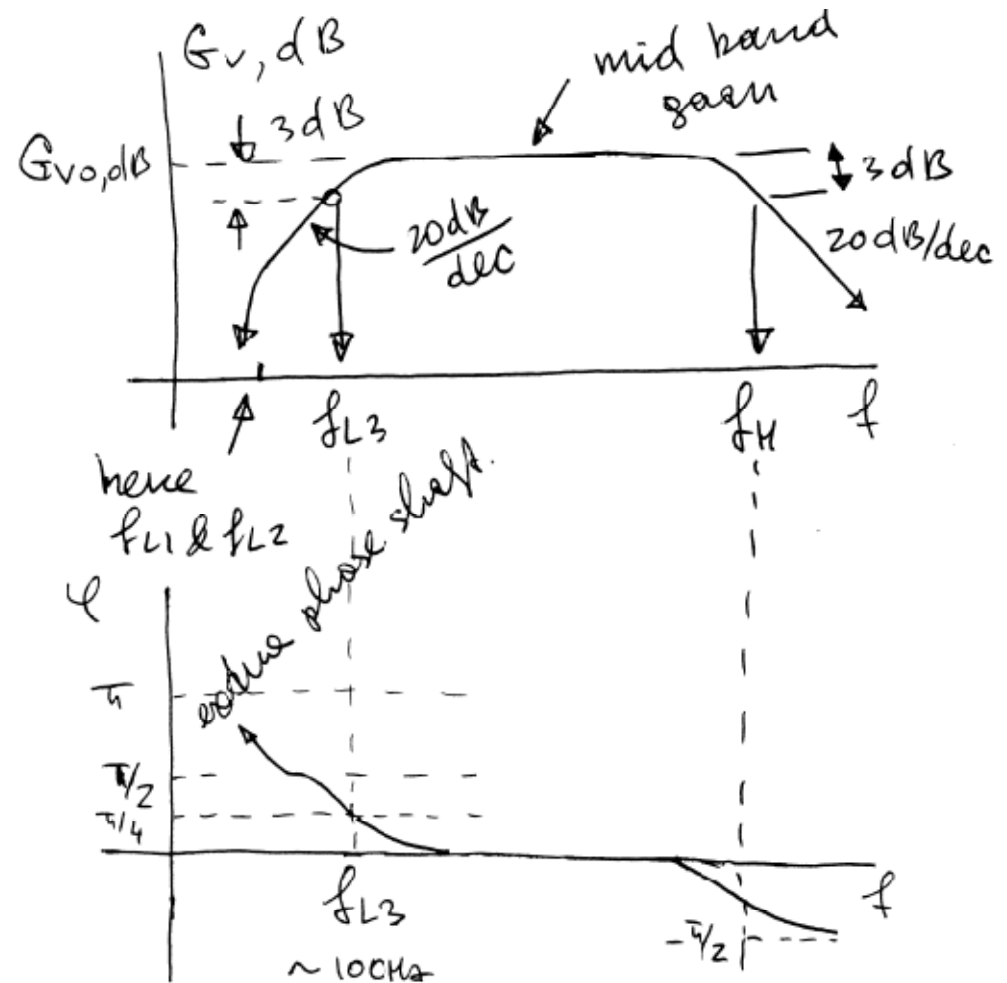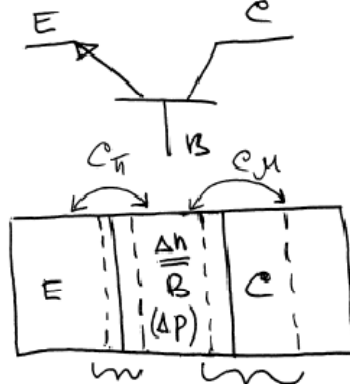High frequency 3dB determines amplifier bandwidth.



Amplifier bandwidth is determined by BJT high frequency capabilities – determined by internal parasitic capacitances C_{π} and C_{μ} .

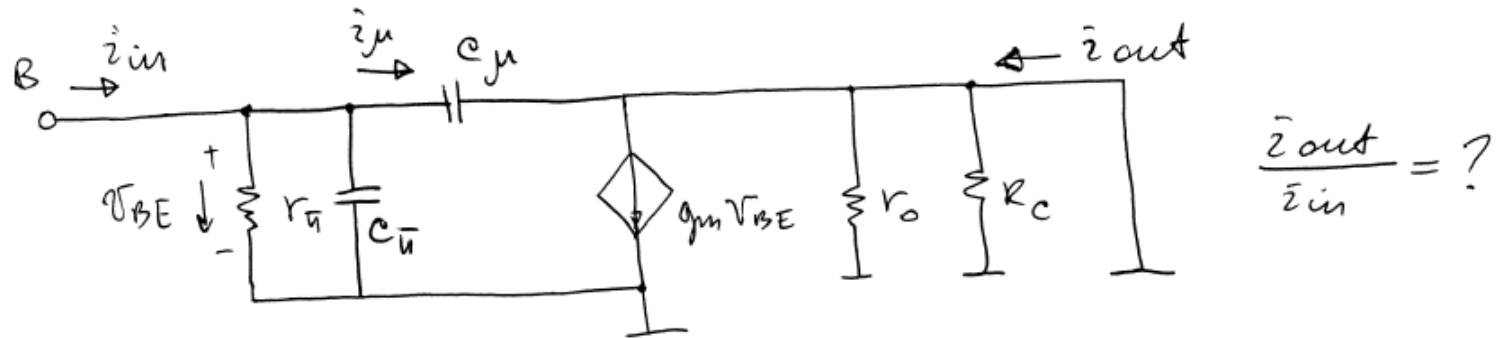Frequency dependence of short circuit current gain



①. $C_{\pi} = C_{\mu} = 0 \quad \left(\frac{i_{out}}{i_{in}} \right) = \frac{g_m v_{BE}}{i_b} = g_m \cdot r_{\pi} = \beta_0$
 ↑ Common emitter current gain defined earlier.

② $C_{\pi} \& C_{\mu} \neq 0$

$$i_{out} = g_m v_{BE} - i_{\mu} = g_m v_{BE} - \frac{v_{BE}}{\frac{1}{j\omega C_{\mu}}} = (g_m - j\omega C_{\mu}) \cdot v_{BE}$$

$$i_{in} = \frac{v_{BE}}{r_{\pi}} + \frac{v_{BE}}{\frac{1}{j\omega C_{\pi}}} + \frac{v_{BE}}{\frac{1}{j\omega C_{\mu}}}$$

Negligible since $\ll \beta_0$ for not extreme frequencies.


④ $C_{\pi} \sim 1 \text{ pF}$
 $C_{\mu} \sim 0.1 \text{ pF}$
 $f_{\beta} \sim 10 \text{ MHz}$

$$\frac{i_{out}(\omega)}{i_{in}(\omega)} = \frac{g_m - j\omega C_{\mu}}{\frac{1}{r_{\pi}} + j\omega(C_{\pi} + C_{\mu})} = \frac{\beta_0 - jf(2\pi r_{\pi} \cdot C_{\mu})}{1 + jf/f_{\beta}} \quad f_{\beta} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$

Frequency dependence of short circuit current gain

$$\beta(f) \approx \frac{\beta_0}{1 + j f / f_\beta}$$
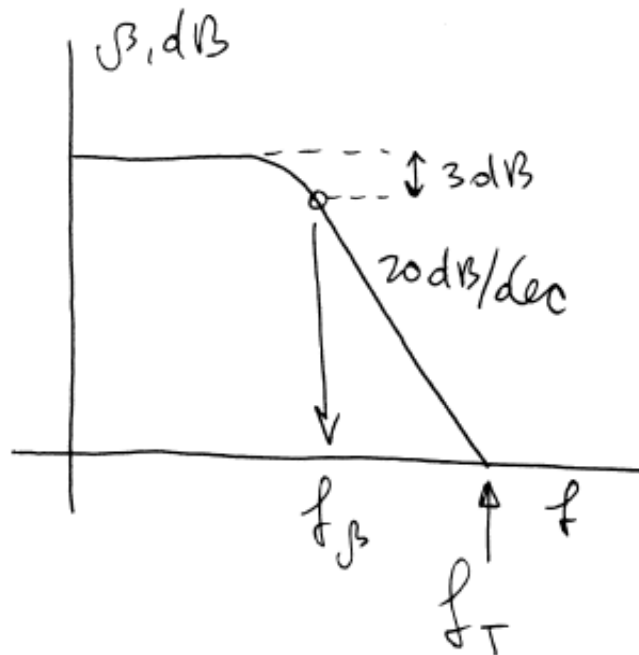
$$f_\beta = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$



Unity gain bandwidth f_T .

$$\beta(f_T) = 1 = \left| \frac{\beta_0}{1 + j f_T / f_\beta} \right| \approx \frac{\beta_0 \cdot f_\beta}{f_T}$$

$$f_T = \beta_0 \cdot f_\beta = \frac{\beta_0}{r_{\pi}} \cdot \frac{1}{2\pi (C_{\pi} + C_{\mu})} = \frac{g_m}{2\pi (C_{\pi} + C_{\mu})}$$


Looks like it is supposed to improve with bias current because

$$g_m = \frac{I_C}{V_{th}}$$

Frequency dependence of short circuit current gain

$$\beta(f) \approx \frac{\beta_0}{1 + j f / f_\beta}$$
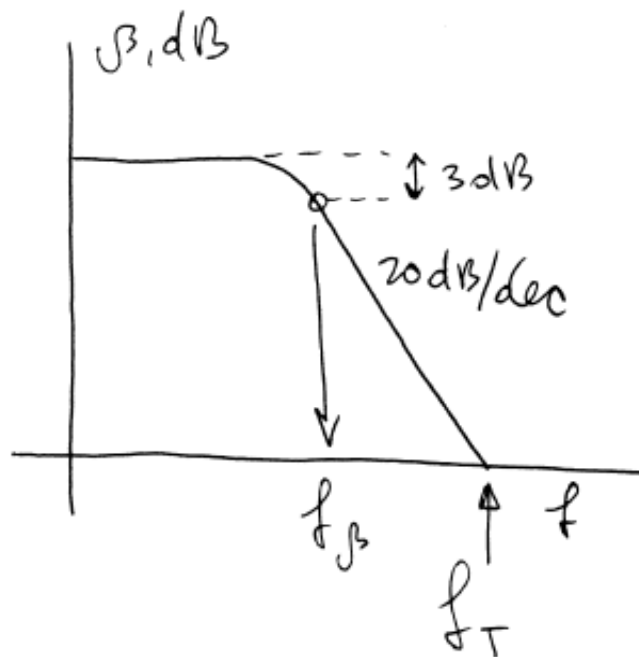
$$f_\beta = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$




Unity gain bandwidth f_T .

$$\beta(f_T) = 1 = \left| \frac{\beta_0}{1 + j f_T / f_\beta} \right| \approx \frac{\beta_0 \cdot f_\beta}{f_T}$$

$$f_T = \beta_0 \cdot f_\beta = \frac{\beta_0}{r_{\pi}} \cdot \frac{1}{2\pi (C_{\pi} + C_{\mu})} = \frac{g_m}{2\pi (C_{\pi} + C_{\mu})}$$

Looks like it is supposed to improve with bias current because

$$g_m = \frac{I_C}{V_{th}}$$

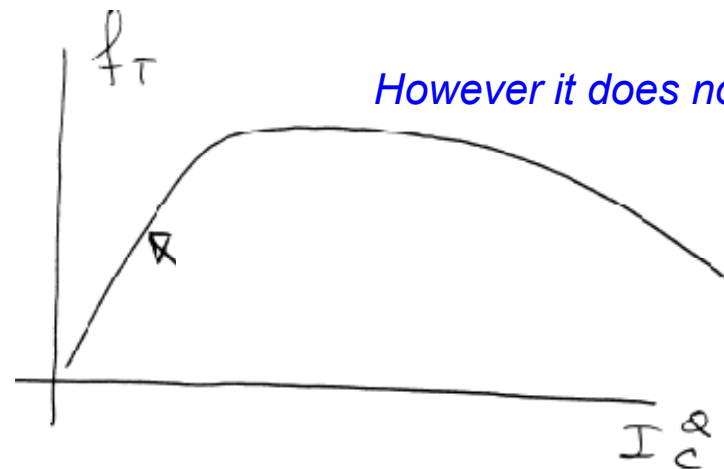


However it does not. Why?

Frequency dependence of common base current gain

$$\alpha(f) = \frac{\beta(f)}{\beta(f) + 1}$$

$$\alpha(f) = \frac{\beta_0}{1 + \beta_0 + j f / f_\beta} = \frac{\alpha_0}{1 + j f / (f_\beta (1 + \beta_0))} \approx \frac{\alpha_0}{1 + j f / f_T}$$

3dB frequency for α is equal to f_T .

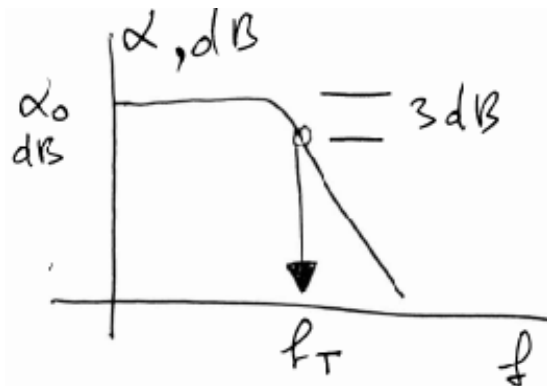


Hence at f_T electrons from emitter can not reach collector.

Frequency dependence of common base current gain


$$\alpha(f) = \frac{\beta(f)}{\beta(f) + 1}$$

$$\alpha(f) = \frac{\beta_0}{1 + \beta_0 + j f / f_\beta} = \frac{\alpha_0}{1 + j f / (f_\beta (1 + \beta_0))} \approx \frac{\alpha_0}{1 + j f / f_T}$$

3dB frequency for α is equal to f_T .

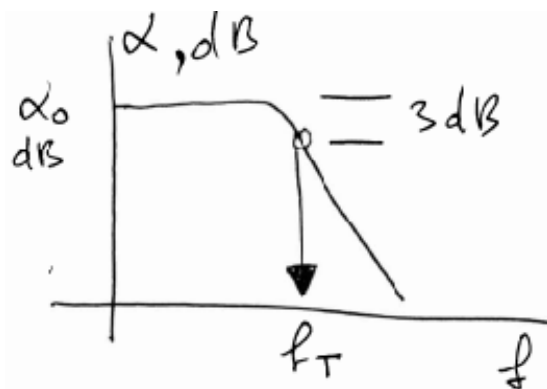

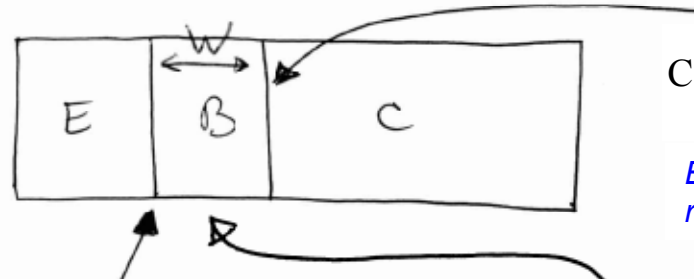Hence at f_T electrons from emitter can not reach collector.



$$C_{BE}(V_{BE}) = \frac{C_{BE0}}{(1 - V_{BE}/V_{bi})^{1/2}}$$

EB-junction depletion region capacitance


$$C_{BC}(V_{CB}) = \frac{C_{BC0}}{(1 + V_{CB}/V_{bi})^{1/2}}$$

BC-junction depletion region capacitance

Base transport time – time of flight of electrons from emitter to collector.

*There are also several parasitic caps associated with technology limitations

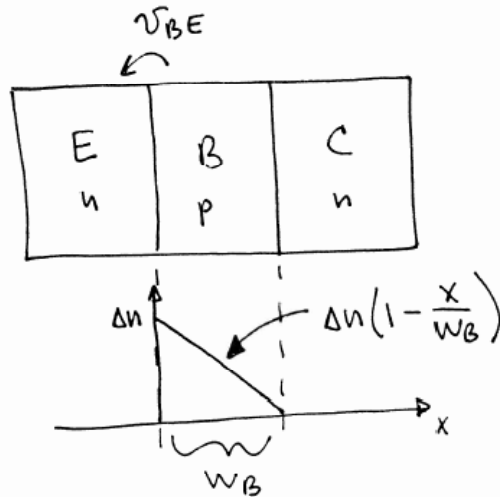Base transport time and diffusion capacitance



$$J_{diff} = q \cdot D_n \cdot \frac{dn}{dx} = q \cdot n \cdot \underbrace{\left(\frac{D_n}{n} \cdot \frac{dn}{dx} \right)}_{\rightarrow v_{diff}}$$


Effective velocity of diffusion electrons $\rightarrow v_{diff}$.

time of flight of electrons from emitter to collector.

$$\tau_{TF} = \frac{w_B}{v_{diff}} \approx \frac{w_B^2}{2 D_n}$$

*Need thin base for high speed operation

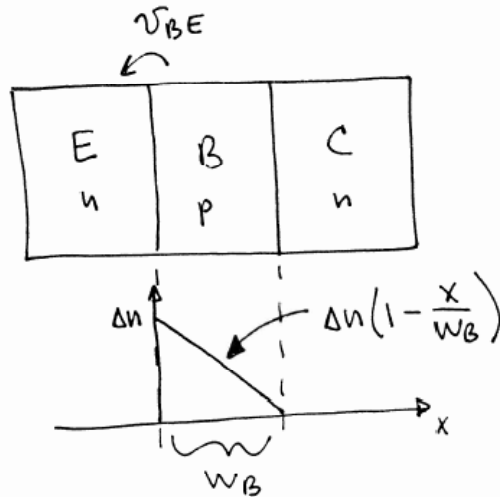Base transport time and diffusion capacitance



time of flight of electrons from emitter to collector.

$$\tau_{TF} = \frac{w_B}{v_{diff}} \approx \frac{w_B^2}{2D_n}$$

*Need thin base for high speed operation

Electron charge stored in base when current I_C is flowing

$$Q_{TF} = I_C \cdot \tau_{TF} \approx q \frac{\Delta n}{2} \cdot w_B$$

$$C_{TF} = \left. \frac{dQ_{TF}}{dV_{BE}} \right|_{I_C^Q} = \tau_{TF} \cdot \left. \frac{dI_C}{dV_{BE}} \right|_{I_C^Q} = \tau_{TF} \cdot g_m$$

$$C_{\pi} = C_{TF} + C_{BEj} \quad ; \quad C_{\mu} = C_{CBj}$$

Charge storage capacitance

Pn-junction depletion region capacitances and other parasitic caps

Unity gain bandwidth

$$C_{\pi} = \underbrace{C_{TF} + C_{BEj}}_{= \tau_{TF} \cdot g_m} \quad \& \quad C_{\mu} = C_{CBj}$$

$$f_T = \frac{g_m}{2\pi (C_{BEj} + C_{CBj}) + 2\pi \cdot g_m \cdot \tau_{TF}} = \frac{1}{2\pi \tau_T}$$

Total time delay



$$\tau_T = \underbrace{\tau_{TF}}_{\text{Minimum possible time delay}} + \frac{C_{BEj} + C_{CBj}}{g_m} \quad \& \quad g_m \sim I_c^{\alpha}$$

Minimum possible time delay


Ultimate limit for BJT speed



Bandwidth of Common Emitter amplifier

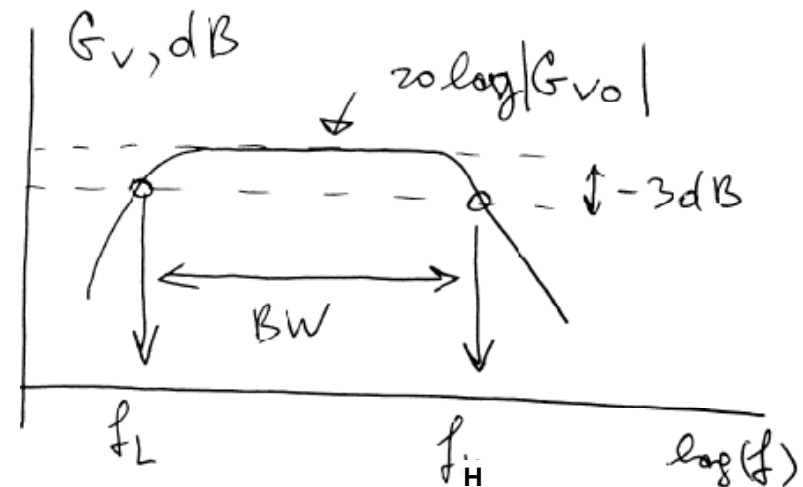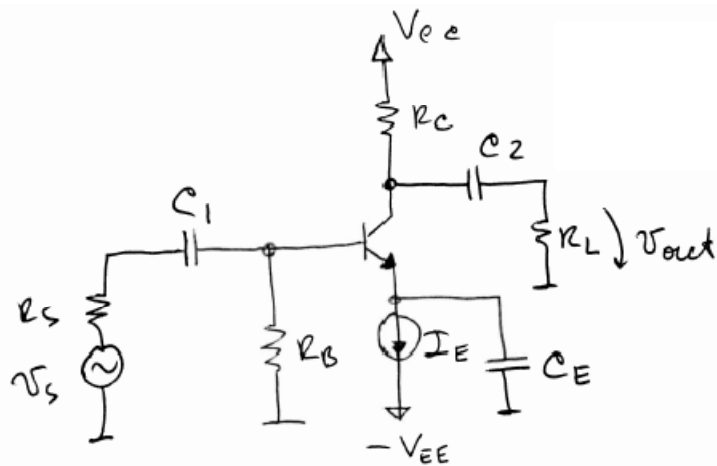

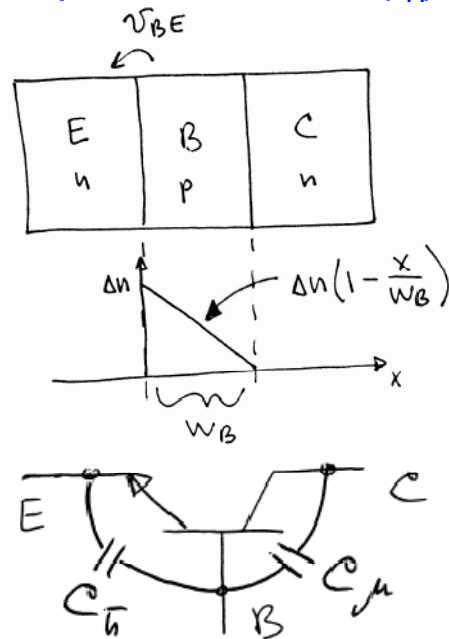Amplifier bandwidth (f_H) is determined by BJT internal parasitic capacitances C_π and C_μ .



$$Q_{TF} = I_C \cdot \tau_{TF} \approx q \frac{\Delta n}{2} \cdot W_B$$

$$\tau_{TF} = \frac{W_B}{v_{diff}} \approx \frac{W_B^2}{2 D_n}$$


$$C_{TF} = \left. \frac{dQ_{TF}}{dV_{BE}} \right|_{I_C^Q} = \tau_{TF} \cdot \left. \frac{dI_C}{dV_{BE}} \right|_{I_C^Q} = \tau_{TF} \cdot g_m$$

$$C_\pi = C_{TF} + C_{BEj} \quad ; \quad C_\mu = C_{CBj}$$


Charge storage
capacitance

Pn-junction depletion region
capacitances and other parasitic caps

Unity gain bandwidth

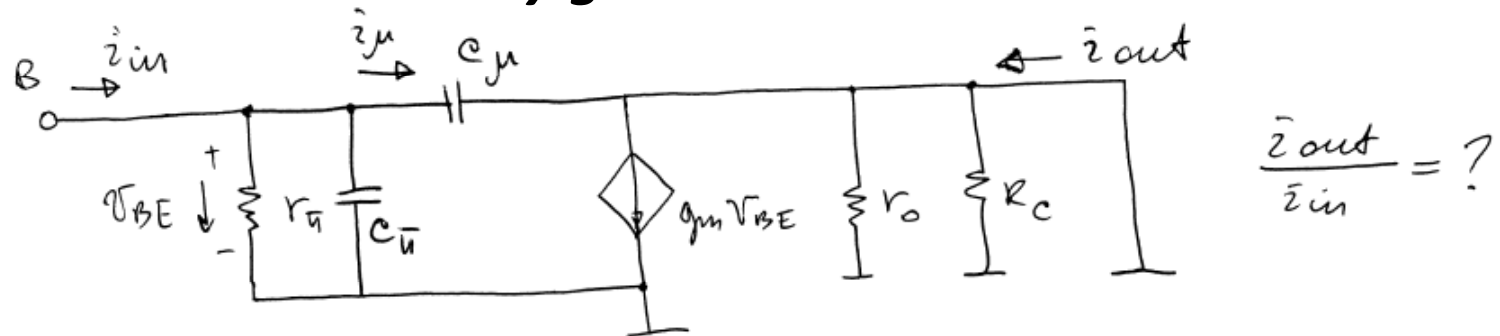
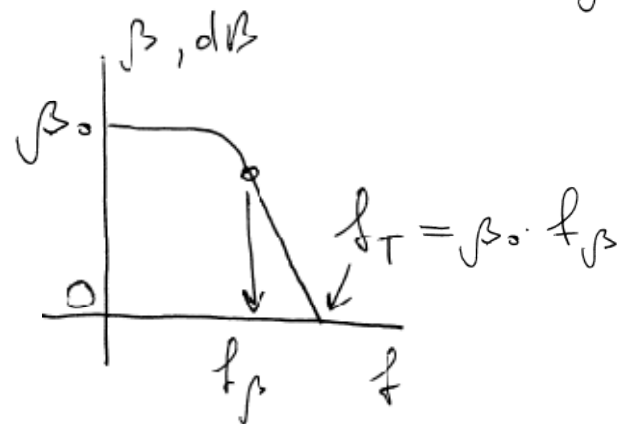
$$\beta(f) = \frac{i_{out}}{i_{in}} \approx \frac{\beta_0}{1 + jf/f_\beta}$$




$$f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$


Unity gain bandwidth f_T

$$C_\pi + C_\mu = C_{\text{junctions}} + \frac{\tau_{TF}}{V_{th}} \cdot I_C^Q$$
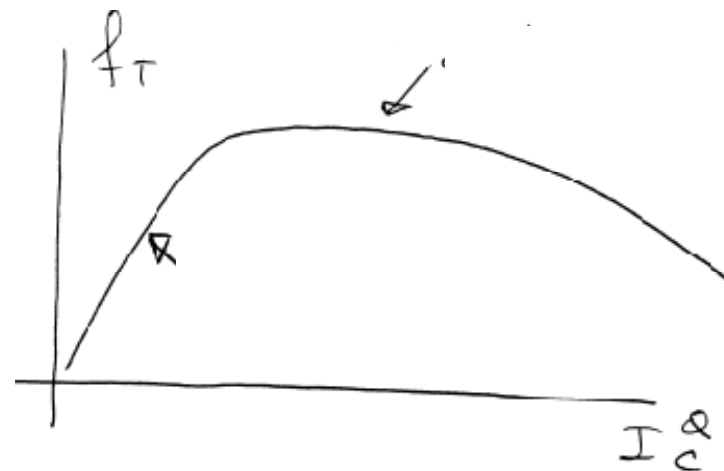
$$f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)} \approx \frac{I_C^Q / V_{th}}{2\pi (C_{\text{junctions}} + \frac{\tau_{TF}}{V_{th}} \cdot I_C^Q)}$$



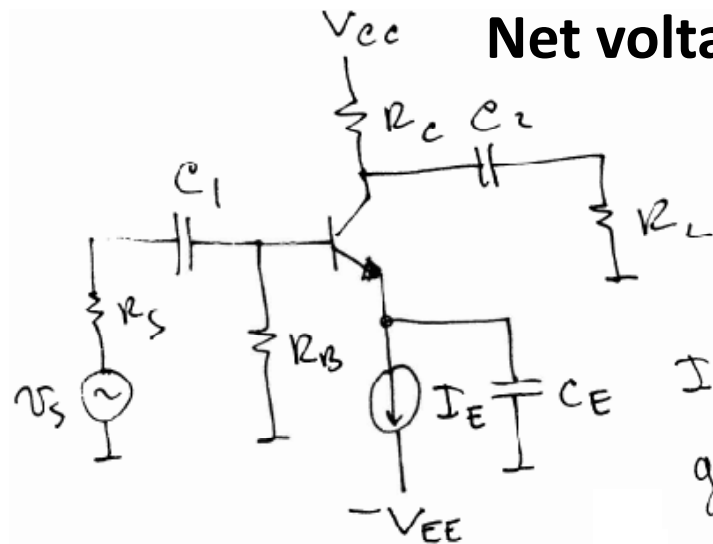
Net voltage gain bandwidth of CE BJT amplifier




We are interested in high frequency cutoff, i.e. coupling and bypass capacitors can be replaced by short circuit for frequencies $\gg f_L$.

I_E determines:
 g_m , r_π , r_o & c_π .

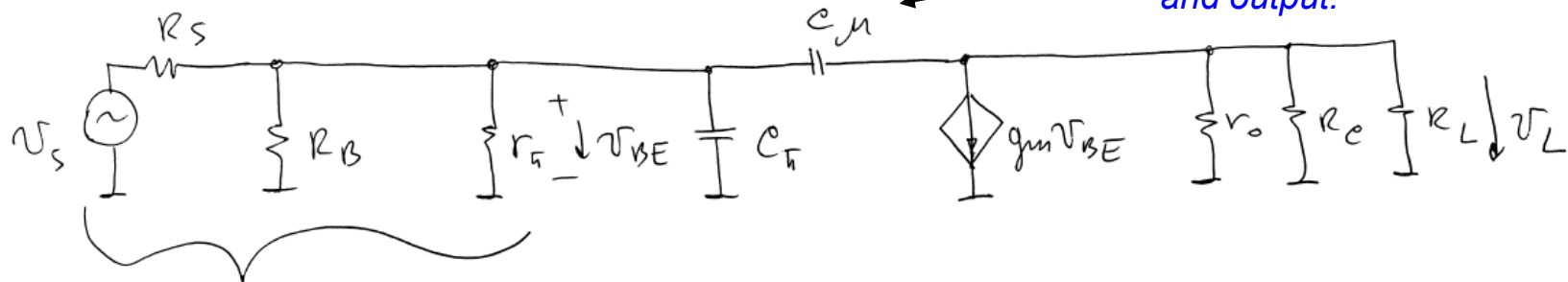We have got capacitive coupling between input and output.




Therefore

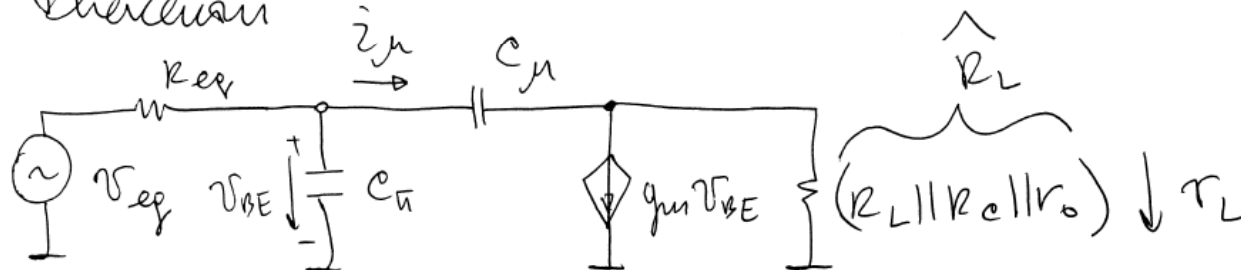

$$v_{eq} = v_s \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} ; R_{eq} = (r_\pi \parallel R_B \parallel R_S)$$

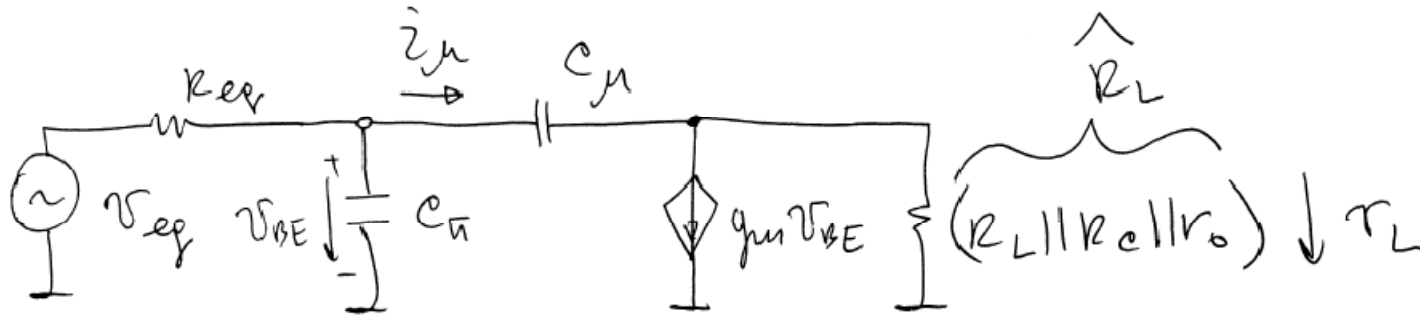Net voltage gain bandwidth of CE BJT amplifier




$$v_L = \hat{R}_L (i_{\mu} - g_m v_{BE}) = v_{BE} - \frac{i_{\mu}}{j\omega C_{\mu}}, \text{ hence}$$

$$i_{\mu} = v_{BE} \frac{1 + g_m \hat{R}_L}{\hat{R}_L + \frac{1}{j\omega C_{\mu}}} = v_{BE} \frac{(1 + g_m \hat{R}_L) \cdot j\omega C_{\mu}}{1 + j\omega C_{\mu} \cdot \hat{R}_L}$$

Observe increase of i_{μ} with transconductance g_m .

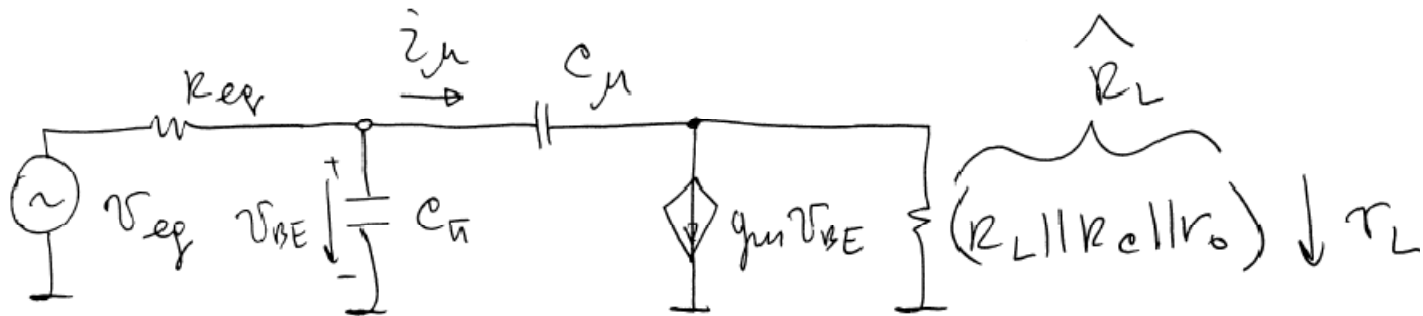Net voltage gain bandwidth of CE BJT amplifier




$$v_L = v_{BE} - \hat{i}_{\mu} \frac{1}{j\omega C_{\mu}} = v_{BE} \frac{j\omega C_{\mu} \hat{R}_L - g_m \hat{R}_L}{1 + j\omega C_{\mu} \hat{R}_L}$$

$$v_{eq} = v_{BE} + R_{eq} (\hat{i}_{\mu} + j\omega C_{\pi} v_{BE})$$


$$\frac{v_L}{v_{eq}} = \frac{j\omega C_{\mu} \hat{R}_L - g_m \hat{R}_L}{(1 + j\omega C_{\pi} R_{eq})(1 + j\omega C_{\mu} \hat{R}_L) + (1 + g_m \hat{R}_L) j\omega C_{\mu} R_{eq}}$$

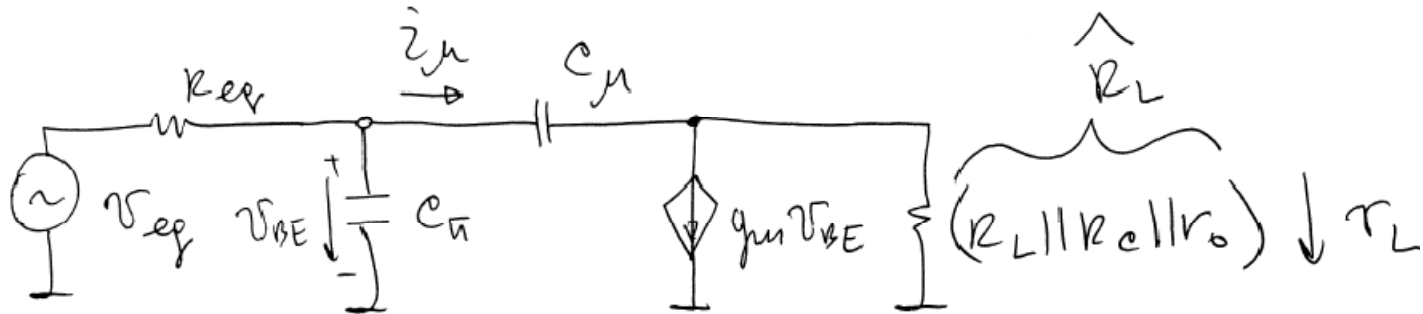Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} = \frac{j\omega C_{\mu} \hat{R}_L - g_m \hat{R}_L}{(1 + j\omega C_{\pi} R_{eq})(1 + j\omega C_{\mu} \hat{R}_L) + (1 + g_m \hat{R}_L) j\omega C_{\mu} R_{eq}}$$

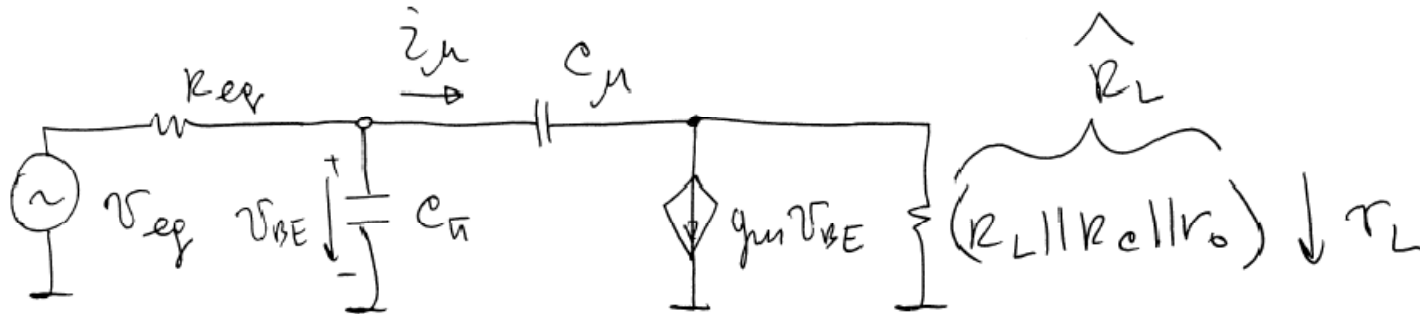Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} = \frac{j\omega C_\mu \hat{R}_L - g_m \hat{R}_L}{(1 + j\omega C_\pi R_{eq})(1 + j\omega C_\mu \hat{R}_L) + (1 + g_m \hat{R}_L)j\omega C_\mu R_{eq}}$$


nominator

$$f_T \approx \frac{1}{2 \cdot \pi \cdot \tau_{TF}} \approx 1 \text{GHz}, \quad C_\mu \approx 0.1 \text{pF}$$

$$\omega \cdot C_\mu \leq 0.001 \Omega^{-1}$$

$$g_m \approx 0.04$$

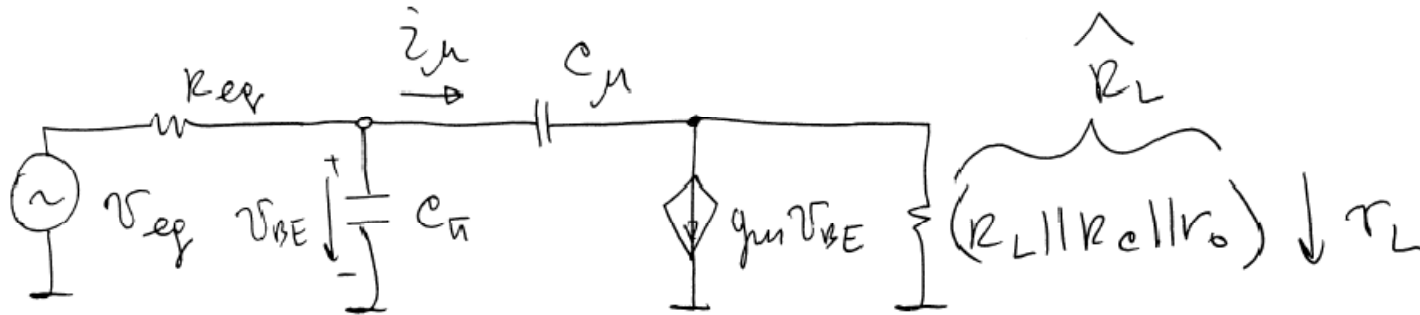Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} = \frac{\cancel{j\omega C_{\mu} \hat{R}_L} - g_m \hat{R}_L}{(1 + j\omega C_{\pi} R_{eq})(1 + j\omega C_{\mu} \hat{R}_L) + (1 + g_m \hat{R}_L) j\omega C_{\mu} R_{eq}}$$


nominator

$$f_T \approx \frac{1}{2 \cdot \pi \cdot \tau_{TF}} \approx 1 \text{GHz}, \quad C_{\mu} \approx 0.1 \text{pF}$$

$$\omega \cdot C_{\mu} \leq 0.001 \Omega^{-1}$$

$$g_m \approx 0.04$$

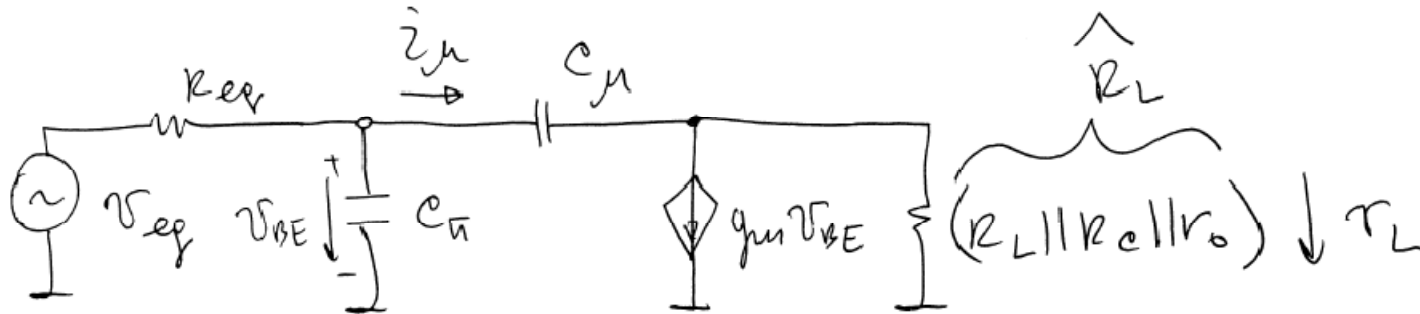Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} = \frac{j\omega C_\mu \hat{R}_L - g_m \hat{R}_L}{(1 + j\omega C_\pi R_{eq})(1 + j\omega C_\mu \hat{R}_L) + (1 + g_m \hat{R}_L)j\omega C_\mu R_{eq}}$$

nominator

$$f_T \approx \frac{1}{2 \cdot \pi \cdot \tau_{TF}} \approx 1 \text{GHz}, \quad C_\mu \approx 0.1 \text{pF}$$

$$\omega \cdot C_\mu \ll 0.001 \Omega^{-1}$$

$$g_m \approx 0.04 \Omega^{-1}$$

denominator


for

$$C_\mu \approx C_\pi / 10$$

$$\text{and } f \ll f_T$$

$$\omega \cdot C_\mu \cdot \hat{R}_L \ll 1$$

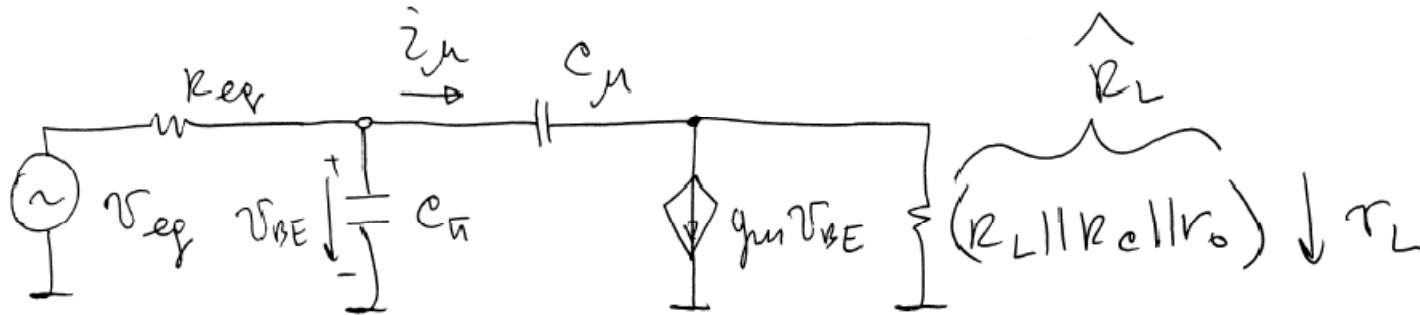Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} = \frac{j\omega C_\mu \hat{R}_L - g_m \hat{R}_L}{(1 + j\omega C_\pi R_{eq})(1 + j\omega C_\mu \hat{R}_L) + (1 + g_m \hat{R}_L)j\omega C_\mu R_{eq}}$$

nominator

$$f_T \approx \frac{1}{2 \cdot \pi \cdot \tau_{TF}} \approx 1 \text{GHz}, \quad C_\mu \approx 0.1 \text{pF}$$

$$\omega \cdot C_\mu \ll 0.001 \Omega^{-1}$$

$$g_m \approx 0.04 \Omega^{-1}$$

denominator


for

$$C_\mu \approx C_\pi / 10$$

$$\text{and } f \ll f_T$$

$$\omega \cdot C_\mu \cdot \hat{R}_L \ll 1$$

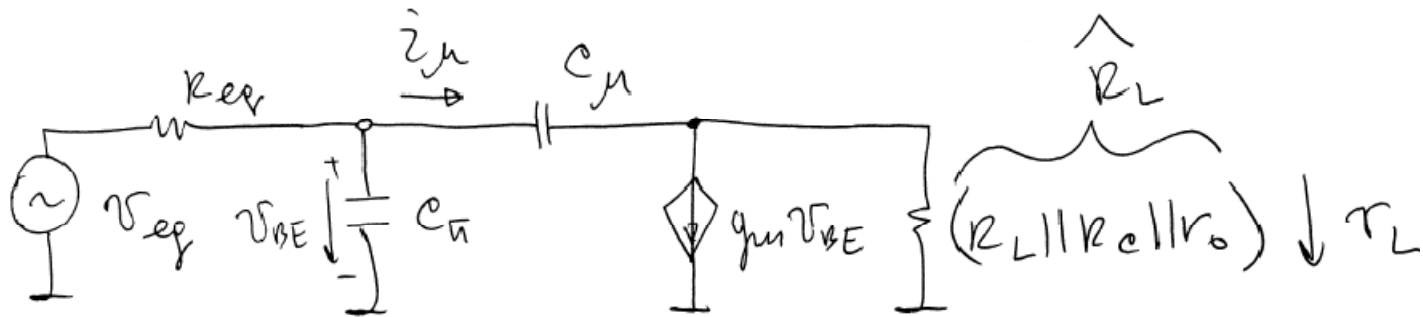Net voltage gain bandwidth of CE BJT amplifier



$$\frac{v_L}{v_{eq}} \approx \frac{-g_m \hat{R}_L}{1 + j\omega R_{eq} (C_{\pi} + (1 + g_m \hat{R}_L) \cdot C_{\mu})}$$



$$\frac{v_L(f)}{v_S(f)} = G_V(f) \propto \frac{-g_m (R_L \parallel R_c \parallel r_o)}{1 + j f / f_H}$$

$$f_H = \frac{1}{2\pi R_{eq} (C_{\pi} + (1 + g_m \hat{R}_L) C_{\mu})}$$

Resistor in series
with input cap

equivalent input cap

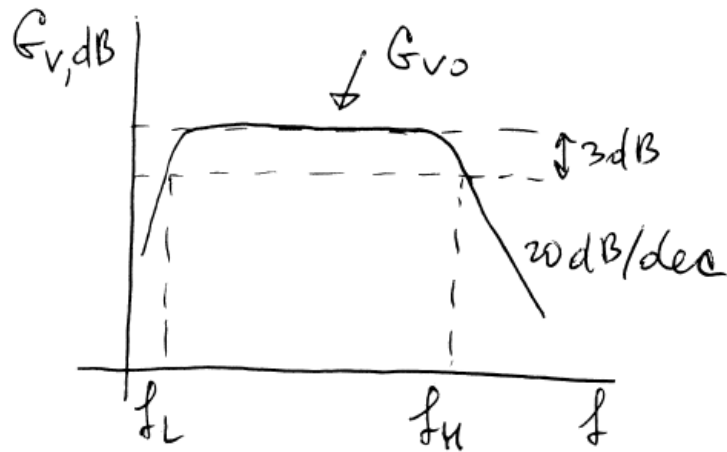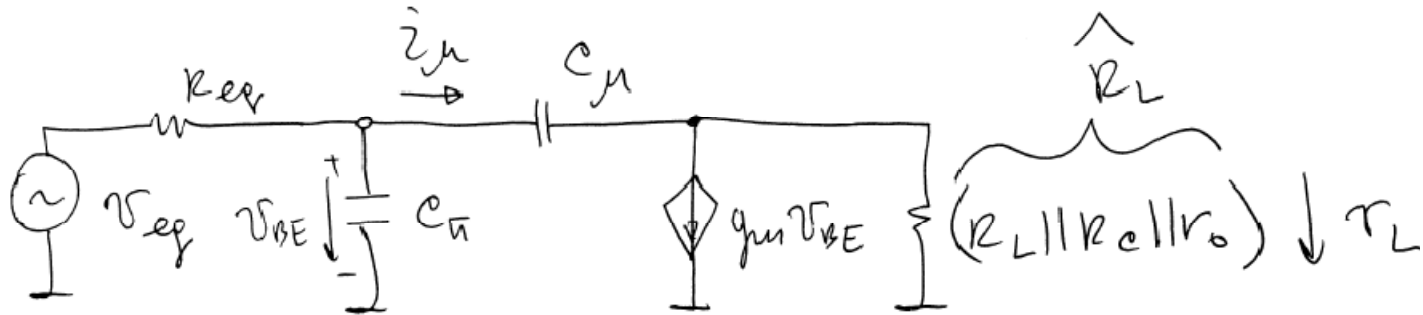Net voltage gain bandwidth of CE BJT amplifier



$$f_H = \frac{1}{2\pi R_{eq} (C_{\pi} + \underbrace{C_{\mu}(1 + g_m(R_L \parallel R_C \parallel r_o))}_{A_v})}$$

$$C_{\mu}(1 + A_v) = C_M$$

"Miller" capacitor

$$G_{v_o} = \frac{R_{in}}{R_{in} + R_S} \cdot A_{v_o} \cdot \frac{R_L}{R_{out} + R_L}$$

$$A_{v_o} = -g_m(R_C \parallel r_o)$$


Example

$$V_{CC} = V_{EE} = 10V ; I_E = 1mA ; R_B = 100k\Omega$$

$$\beta_o = 100 ; C_{\mu} = 1pF ; f_T = 800MHz ; R_C = 8k\Omega$$

$$V_A = 100V ; R_S = R_L = 5k\Omega$$

* confirm FA regime first ...

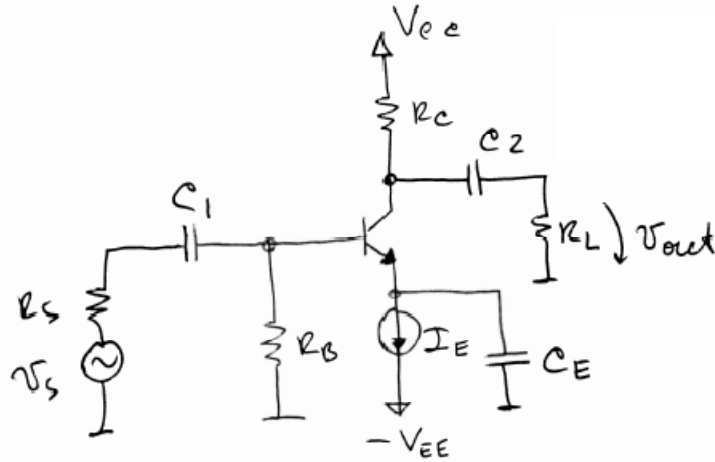

$$\textcircled{1} \quad g_m = \frac{1mA}{25mV} = 40 \frac{mA}{V}$$

$$r_{\pi} = \frac{100}{g_m} = 2.5k\Omega$$

$$r_o = \frac{100V}{1mA} = 100k\Omega$$

$$\textcircled{2} \quad C_{\pi} + C_{\mu} = \frac{g_m}{\omega_T} = \frac{40 \cdot 10^{-3}}{2\pi \cdot 800 \cdot 10^6} = 8pF$$


$$C_{\mu} = 1pF \text{ hence } C_{\pi} = 7pF$$

$$\textcircled{*} R_L || R_C || r_o \approx 3k\Omega$$

$$\textcircled{3} \quad G_V = \frac{R_B || r_{\pi}}{R_B || r_{\pi} + R_S} \cdot (-g_m (R_L || R_C || r_o)) = - \frac{40 \cdot 10^{-3} \cdot 3 \cdot 10^3}{(100k || 2.5k) + 5k} \cdot (100k || 8k || 100k)$$

$$G_V \approx -121 \frac{V}{V} \cdot \frac{1}{3} \approx -40 \frac{V}{V} \quad \textcircled{*} g_m \cdot \hat{R}_L = 121 \frac{V}{V}$$

Example – cont.

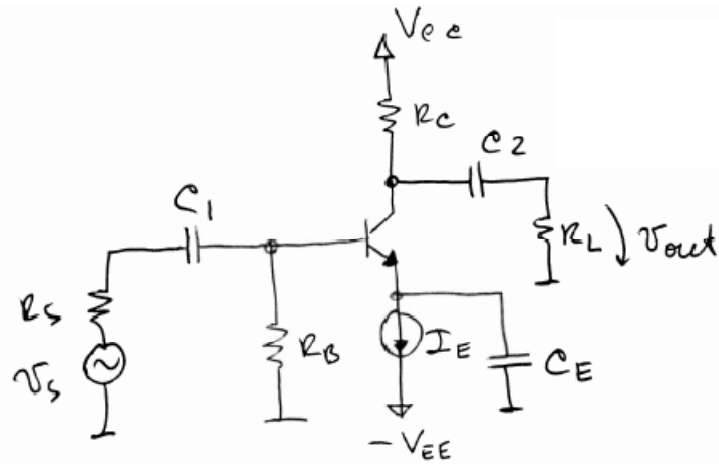

$$V_{CC} = V_{EE} = 10V ; I_E = 1mA ; R_B = 100k\Omega$$

$$\beta_o = 100 ; C_{\mu} = 1pF ; f_T = 800MHz$$

$$V_A = 100V ; R_C = 8k\Omega ; R_S = R_L = 5k\Omega$$

$$G_v \approx -121 \frac{V}{V} \cdot \frac{1}{3} \approx -40 \frac{V}{V}$$

$$\textcircled{4} R_{eq} = (r_{\pi} \parallel R_B) \parallel R_S = 1.7k\Omega$$

$$C_{in} = 7pF + 121 \cdot 1pF = 128pF \gg C_{\pi}$$

$$f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{eq}} \approx 750kHz \ll f_T$$

Even $\ll f_{\beta} = 8MHz$


$$Gain \cdot BW \approx 3 \cdot 10^7$$

Reduced gain – improved BW

$$R_L = 2k\Omega ; \hat{g_m R_L} \approx 64 \frac{V}{V}$$

$$f_H \approx 1.4MHz$$


Miller Effect

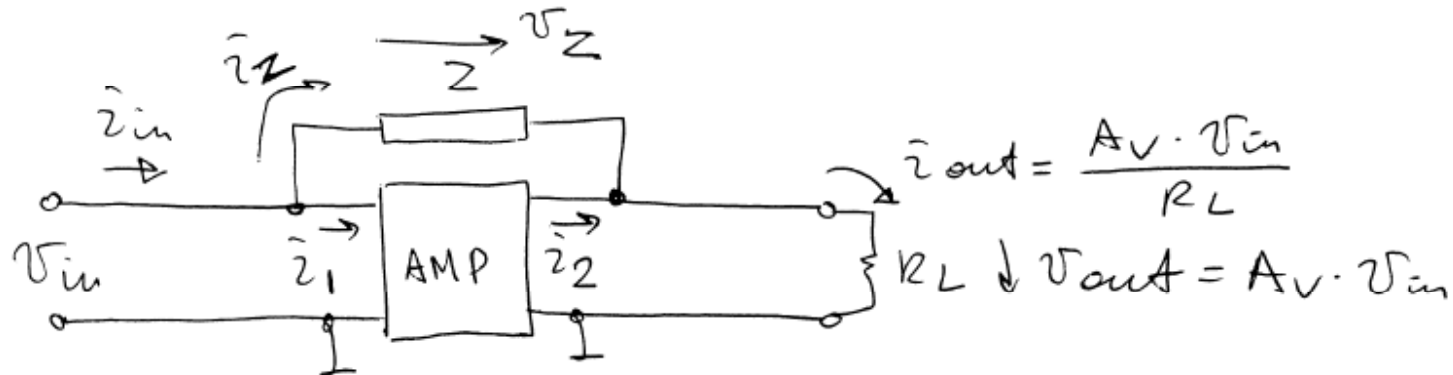

$$v_Z = v_{in} - A_v \cdot v_{in} = v_{in}(1 - A_v)$$

$$i_Z = \frac{v_Z}{Z} = \frac{v_{in}(1 - A_v)}{Z} = v_{in} / \left(\frac{Z}{1 - A_v} \right)$$

Miller transformation

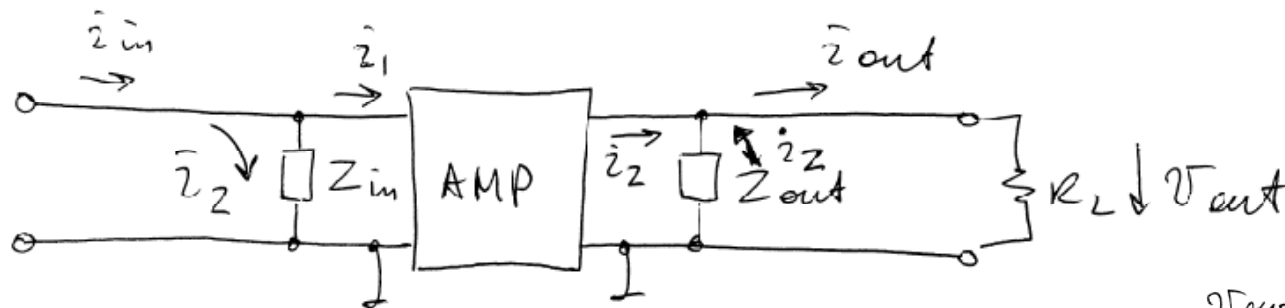


$$Z_{in} = \frac{Z}{1 - A_v}$$

$$Z_{out} = \frac{Z}{A_v - 1}$$

$$\frac{v_{out}}{i_{out}} = - \frac{v_{in}(1 - A_v)}{Z}$$

Miller Effect in CE amplifier

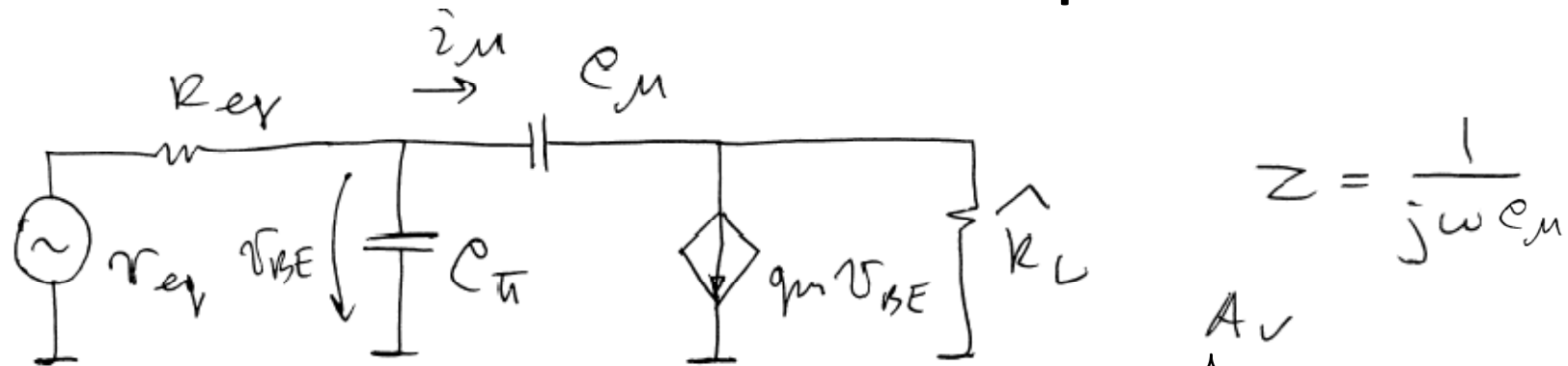

If i_{μ} is not very high (small C_{μ}), then


$$Z_{in} = \frac{1}{j\omega C_{\mu}(1 - A_v)}$$

$$Z_{out} = \frac{1}{j\omega C_{\mu} A_v - 1}$$


$$v_{out} \approx (-g_m \hat{R}_L) \cdot v_{BE}$$

$$C_M^{in} = C_{\mu} (1 + g_m \hat{R}_L)$$


$$C_M^{out} = C_{\mu}$$

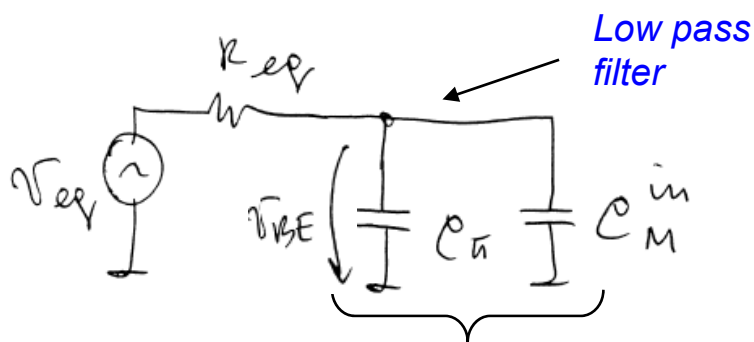

Total equivalent input cap

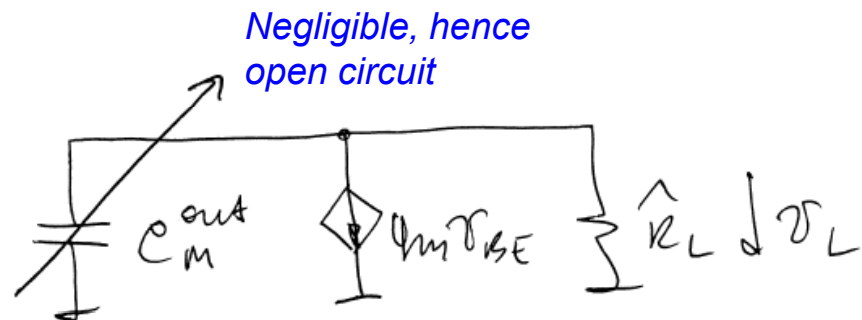

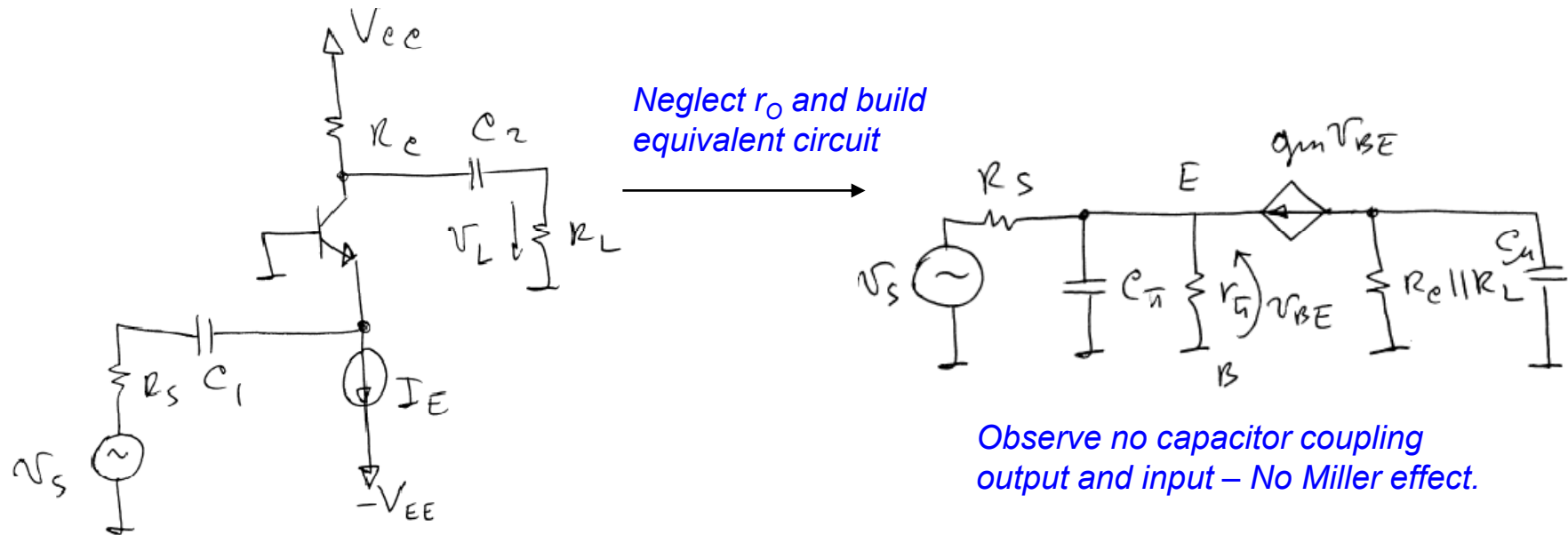CB amplifier does not suffer from Miller effect




$$v_L = (-g_m v_{BE}) (R_c \parallel R_L \parallel C_\mu)$$

$$-v_{BE} = v_s + R_s \left(g_m v_{BE} + \frac{v_{BE}}{(r_\pi \parallel C_\pi)} \right)$$

$$\frac{v_L}{v_s} = \frac{g_m (R_c \parallel R_L \parallel C_\mu)}{1 + R_s \left(g_m + \frac{r_\pi + \frac{1}{j\omega C_\pi}}{r_\pi - \frac{1}{j\omega C_\pi}} \right)}$$

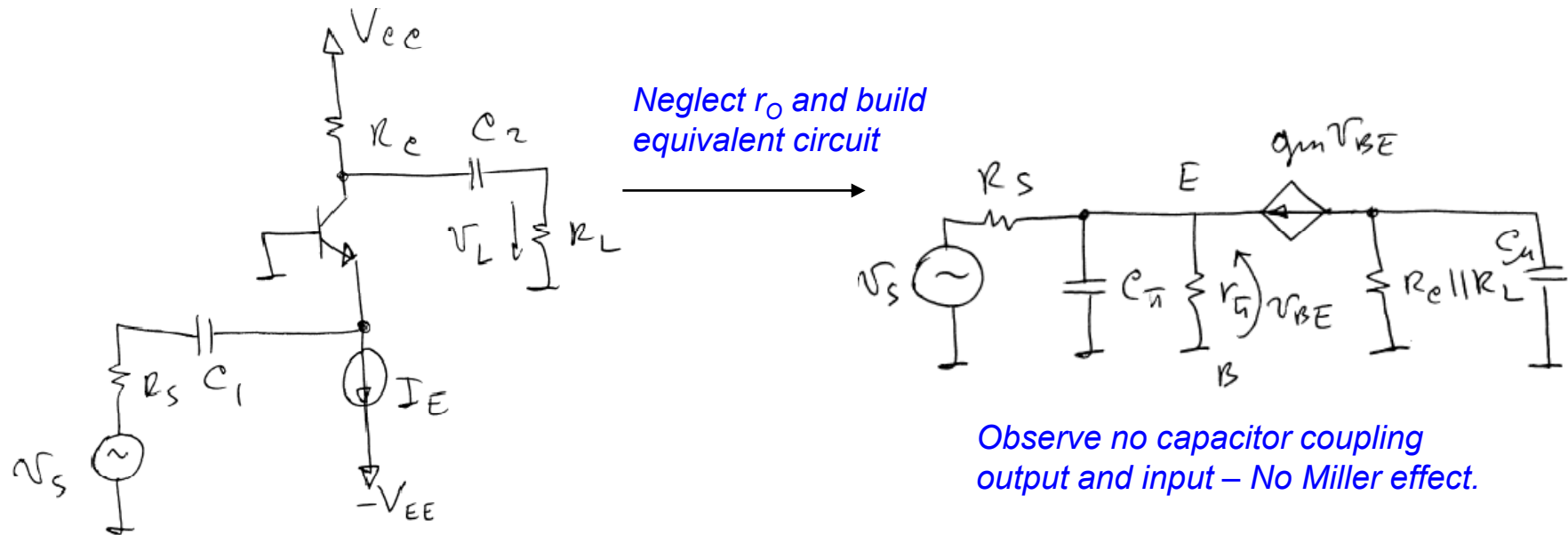CB amplifier does not suffer from Miller effect



$$\frac{v_L(f)}{v_S(f)} = \frac{g_m(R_{eff} || R_L)}{1 + R_S(g_m + \frac{1}{r_{\pi}})} \cdot \frac{1}{1 + j\omega \underbrace{(R_{eff} || R_L) C_m}_{\tau_1}} \cdot \frac{1}{1 + j\omega C_{\pi} \underbrace{\frac{R_S}{1 + R_S(g_m + \frac{1}{r_{\pi}})}}_{\tau_2}}$$

$$f_1 = \frac{1}{2\pi(R_C \parallel R_L)C_M} = \frac{1}{6.28 \cdot 3 \cdot 10^3 \cdot 10^{-12}} = 52 \text{ MHz}$$

$$f_2 = \frac{1}{2\pi C_{\bar{u}} (R_S || V_{\bar{u}} || \frac{1}{g_m})} \approx \frac{g_m}{2\pi C_{\bar{u}}} = \frac{40 \cdot 10^{-3}}{6.28 \cdot 10^{-12} \cdot 7} \approx 910 \text{ MHz}$$